

ECEN 4517/5517

Power Electronics and Photovoltaic Power Systems Laboratory


Lecture 4

Converter Modeling and Simulation

Announcements

- This week's lab: Continue Experiment 3-1
 - You have this and next week to finish Experiment 3-1
 - Get your converter running open-loop and take data outside
 - Next week finish Exp 3-1, including simulations
 - Exp 3-1 Lab Report due by 11:59 pm (MT) on Friday February 24, 2017
- After this: Experiment 3-2
 - Experiment 3-2 has a pre-lab (due 11:59 pm, Friday February 17, 2017)
 - Have 2 weeks to work on Experiment 3-2
 - Exp 3-2 Lab Report due by 11:59 pm (MT) on Friday March 10, 2017
- Following this: Experiment 4
 - Experiment 4 has a pre-lab (due 11:59 pm, Friday March 3, 2017)
 - Have 3 weeks to work on Experiment 4
 - Exp 4 Lab Report due by 11:59 pm (MT) on Friday April 7, 2017
- Quiz 1: Monday, February 27, 2017 (in class)

Experiments

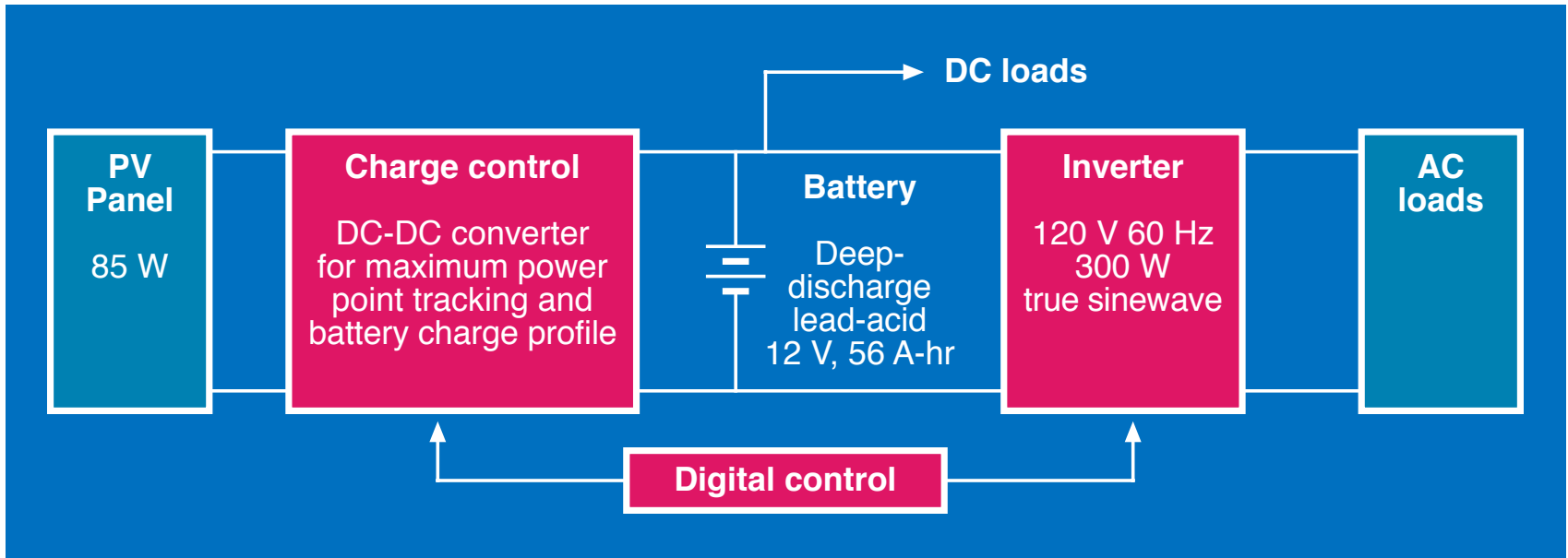


- [Exp 1](#) – PV panel and battery characteristics and direct energy transfer
- [Exp 2](#) – TI MSP430 microcontroller introduction
- [Exp 3-1, 3-2](#) – Buck dc-dc converter for PV MPPT and battery charge control
- [Exp 4](#) – Step-up 12V-200V dc-dc converter
- [Exp 5](#) – Single-phase dc-ac converter (inverter)
- [Expo](#) – Complete system demonstration

Experiments 3-1 and 3-2

- Experiment 3-1

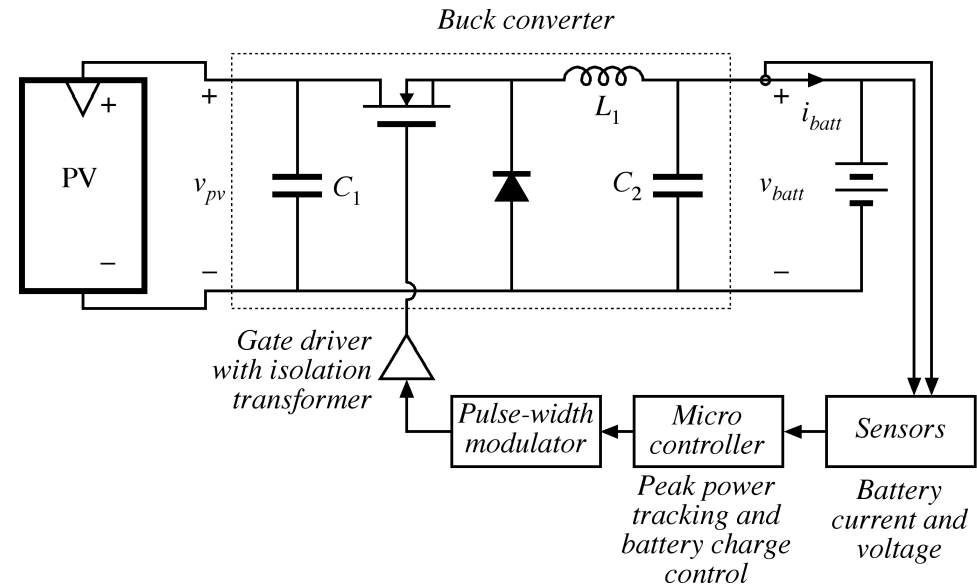- Demonstrate dc-dc converter power stage operating open loop, driven by MSP430 PWM output
- Inside, with input power supply and resistive load
- Outside, between PV panel and battery
- DC system simulation




- Experiment 3-2

- Demonstrate working sensor circuitry, interfaced to microprocessor
- Demonstrate peak power tracker and battery charge controller algorithms, outside with converter connected between PV panel and battery


Experiments 3-1 Week 1

- Demonstrate dc-dc converter power stage inside

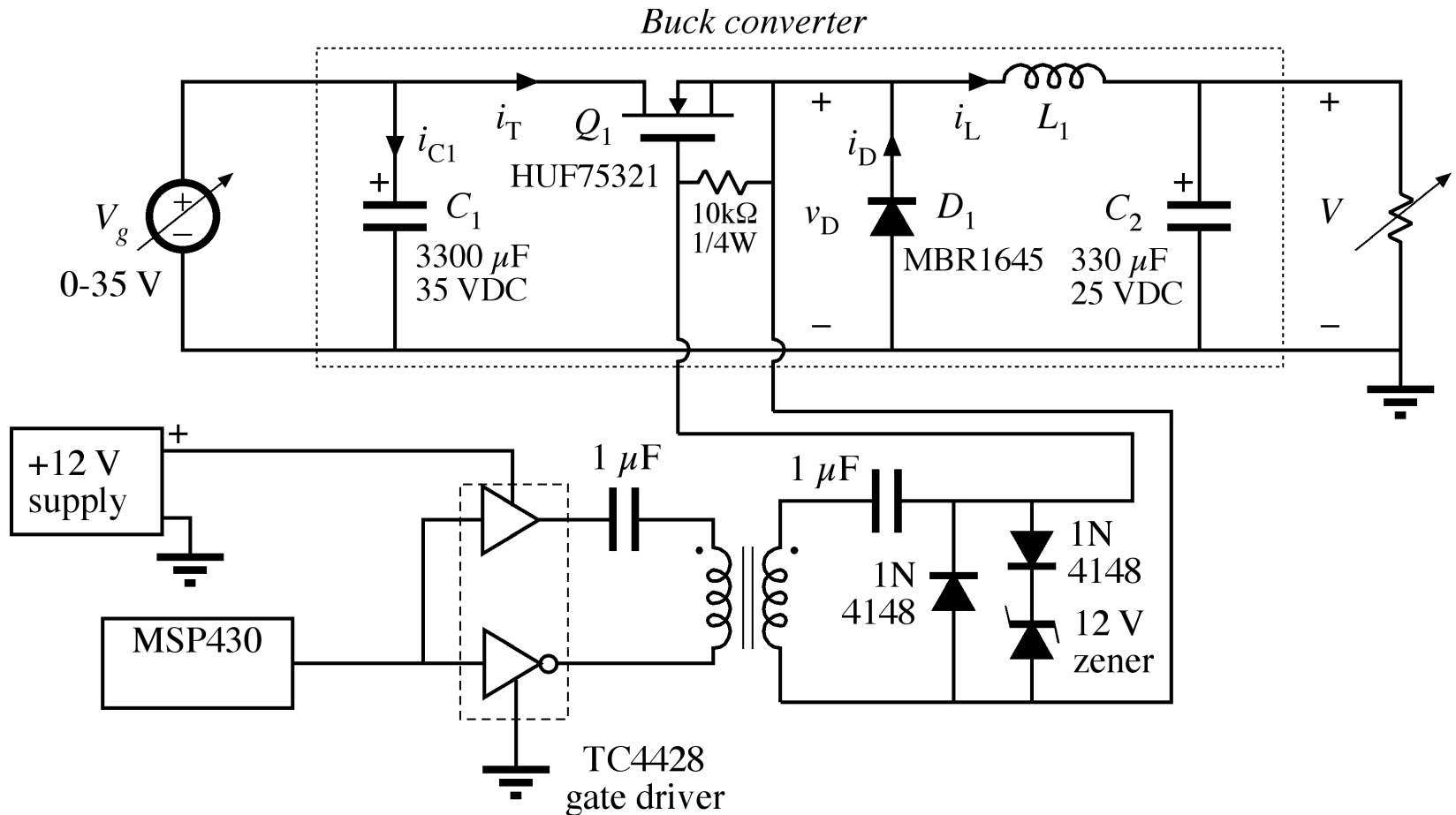



Experiments 3-1 Week 2

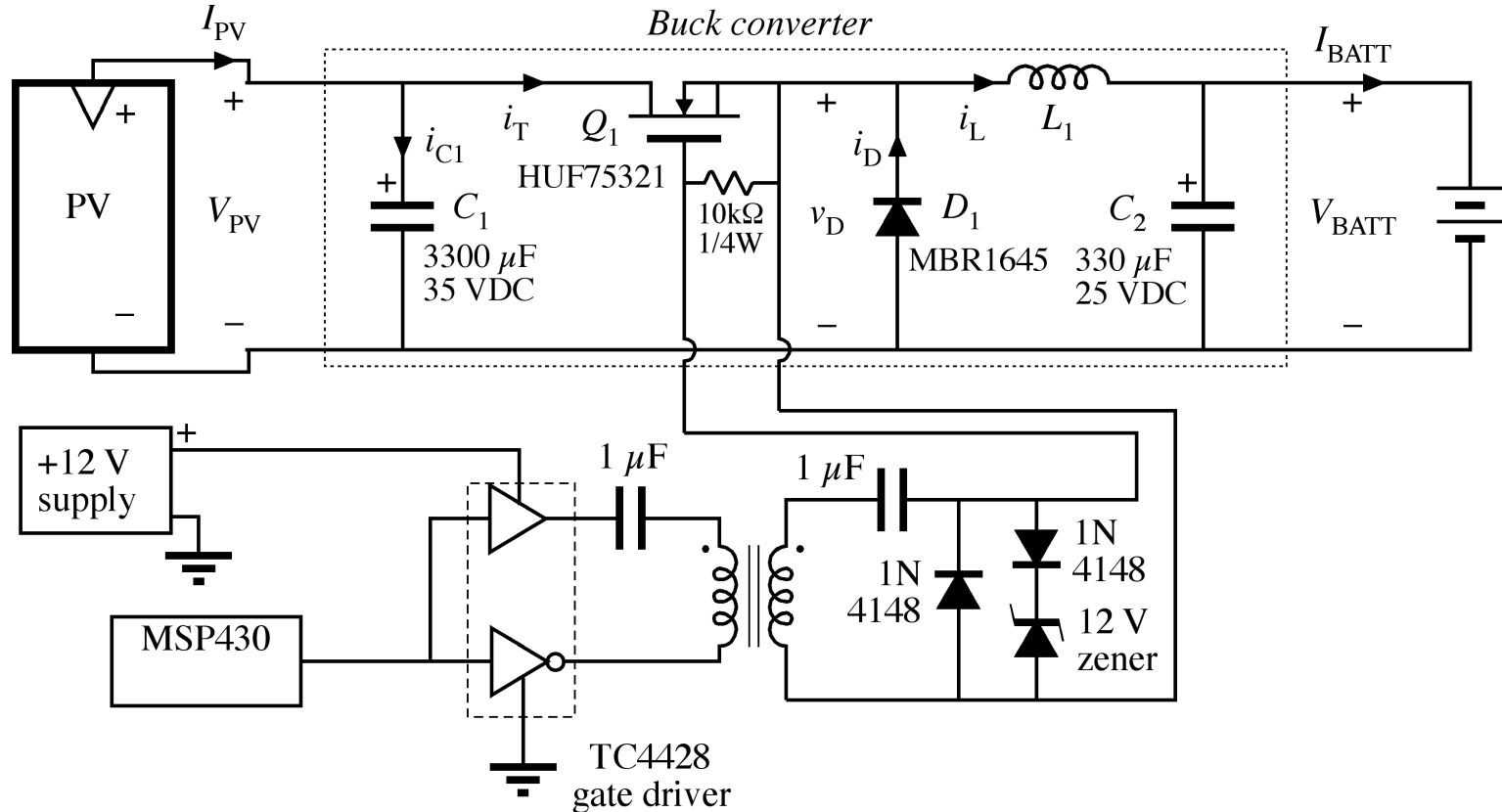- Demonstrate dc-dc converter power stage outside



- Explore how duty ratio controls the PV and battery voltages and currents



Converter Modeling and Simulation

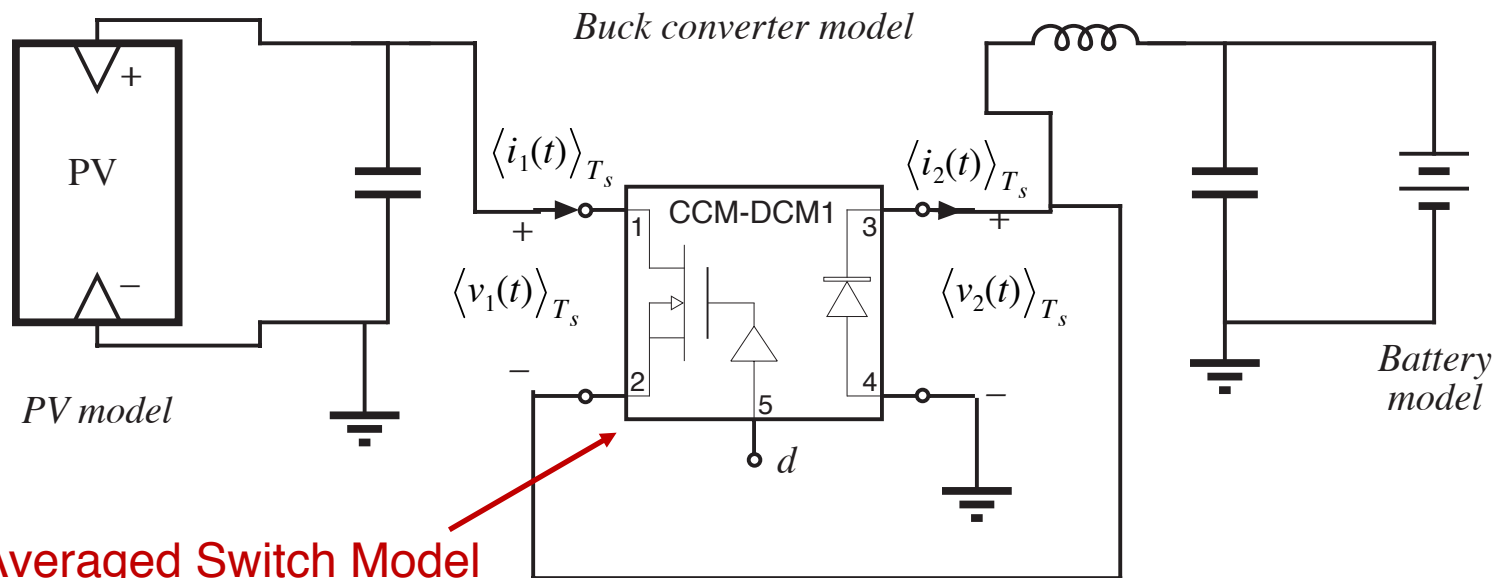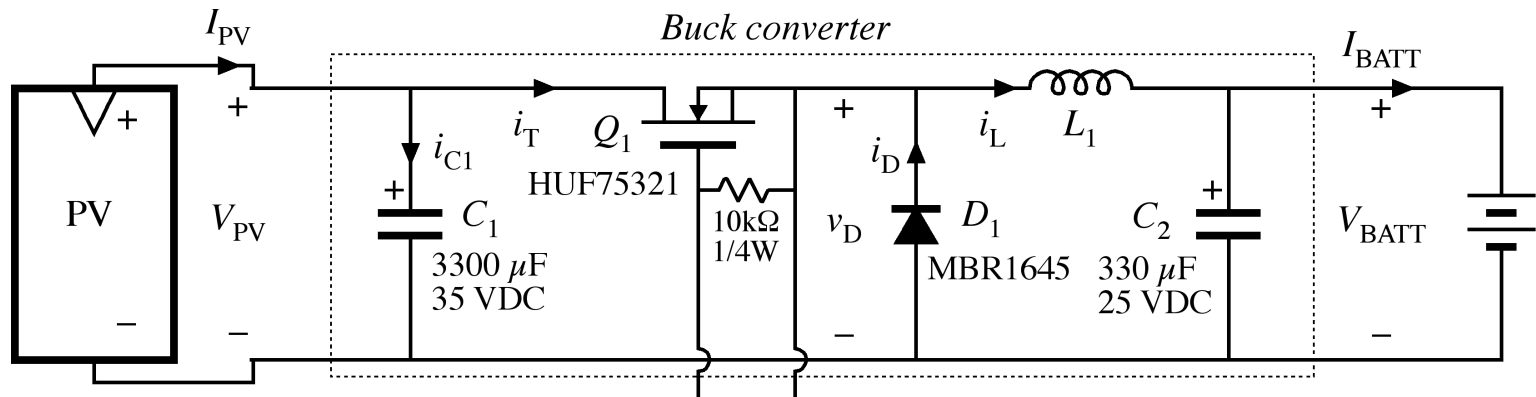


Average Switch Modeling

- Separate the switching elements from the remainder of the converter
- Define the terminal voltages and currents of the two-port switch network
- Derive relationships between the local average values of the switch network terminal voltages and currents

Example: Buck Converter

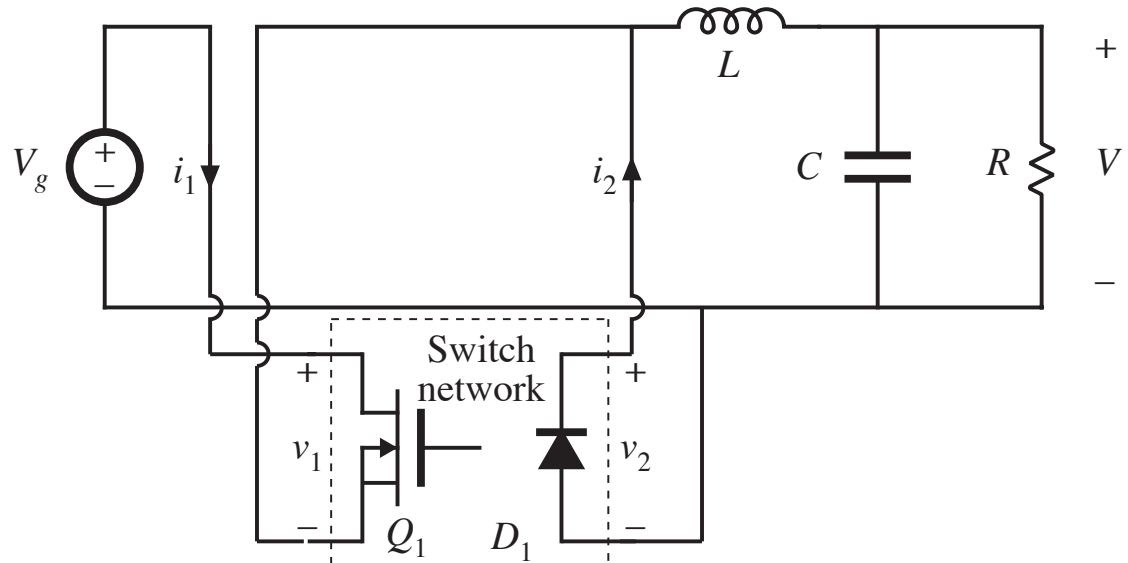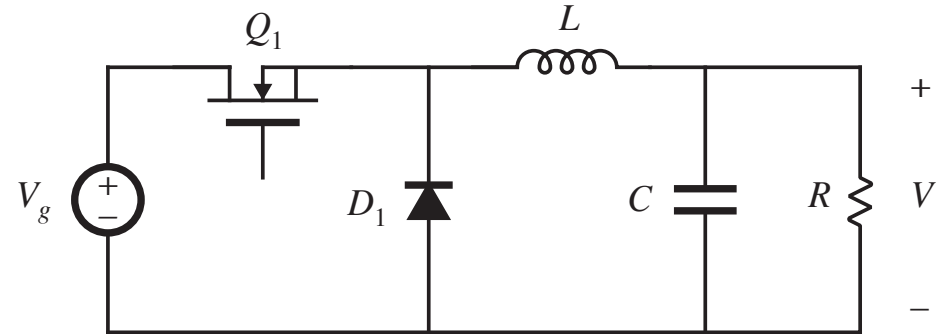

Average Switch Modeling in CCM

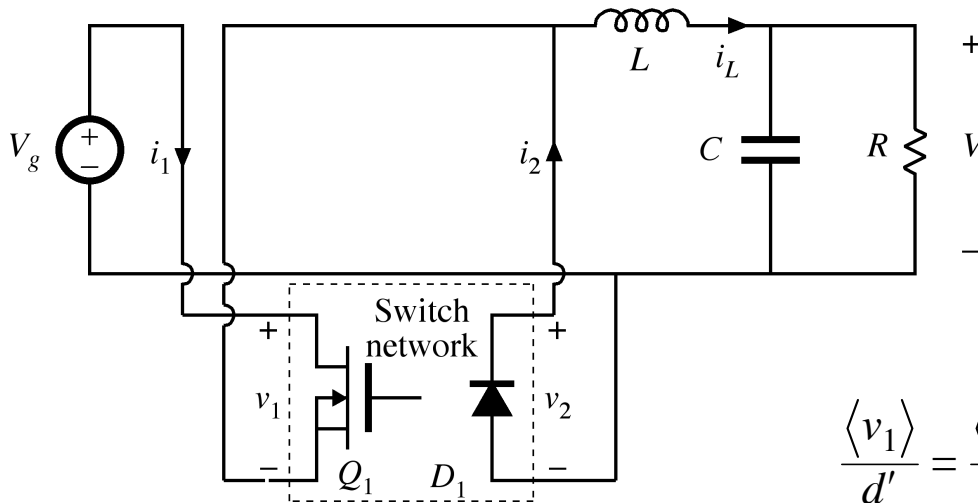

$$\frac{\langle v_1 \rangle}{d'} = \frac{\langle v_2 \rangle}{d} = \langle v_g \rangle$$





$$\frac{\langle i_2 \rangle}{d'} = \frac{\langle i_1 \rangle}{d} = \langle i_L \rangle$$

Relationship between average terminal waveforms:

$$\langle v_1(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle v_2(t) \rangle_{T_s}$$

$$\langle i_2(t) \rangle_{T_s} = \frac{d'(t)}{d(t)} \langle i_1(t) \rangle_{T_s}$$

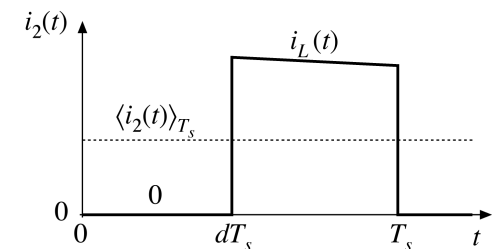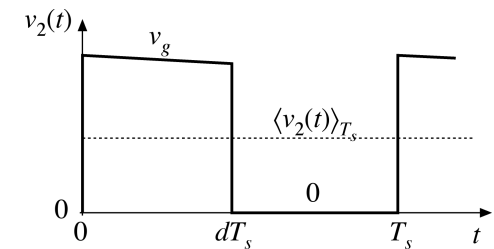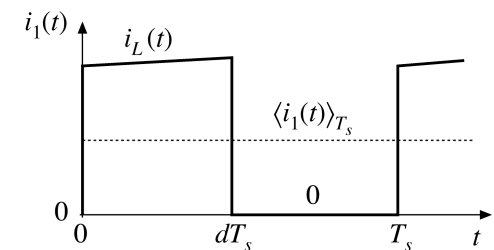
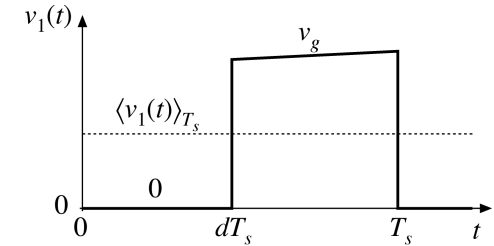
Continuous Conduction Mode (CCM) Operation



Averaged Model of Switch Network under CCM

Can model the switch network via averaged dependent sources
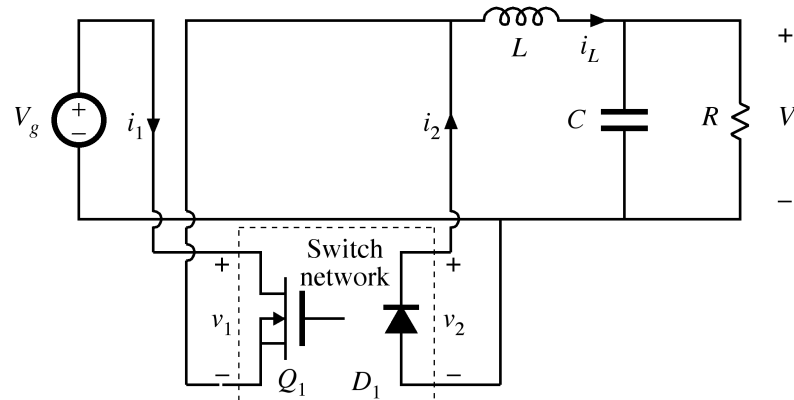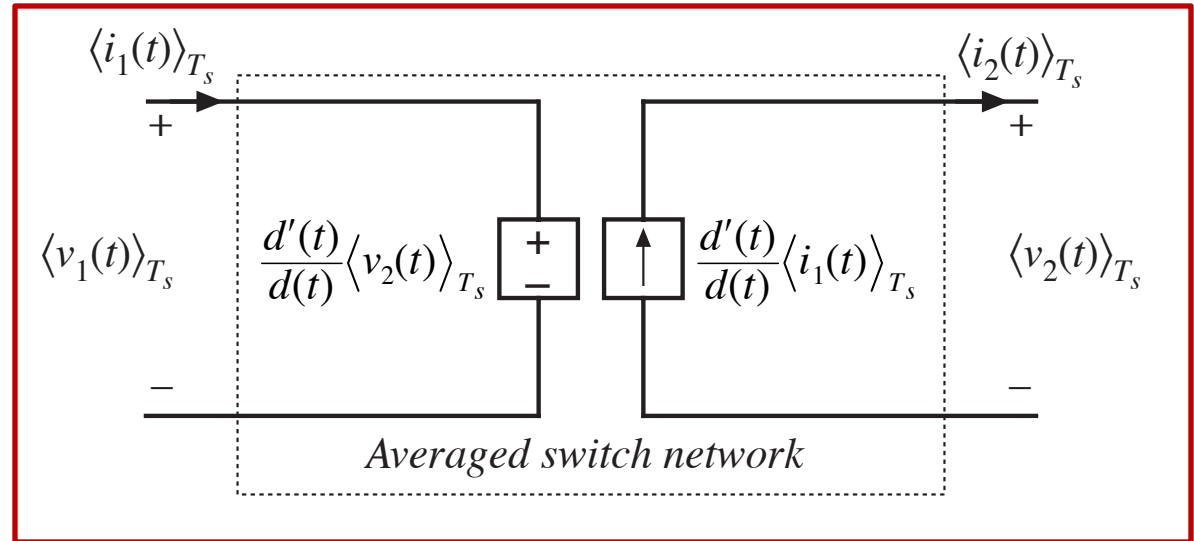
$$\begin{aligned}\langle v_1 \rangle &= \frac{d'}{d} \langle v_2 \rangle \\ \langle i_2 \rangle &= \frac{d'}{d} \langle i_1 \rangle\end{aligned}$$




Averaged Switch Model in SPICE

- We will use LTspice (a free version of SPICE) as the circuit simulator

```
.subckt CCM1 1 2 3 4 5
Et 1 6 value={{(1-v(5))*v(3,4)/v(5)}}
Vdum 6 2 0
Gd 4 3 value={{(1-v(5))*i(Vdum)/v(5)}}
.ends
```


This CCM averaged switch model
is available inside SPICE Library
file `switch.lib`

Symbol

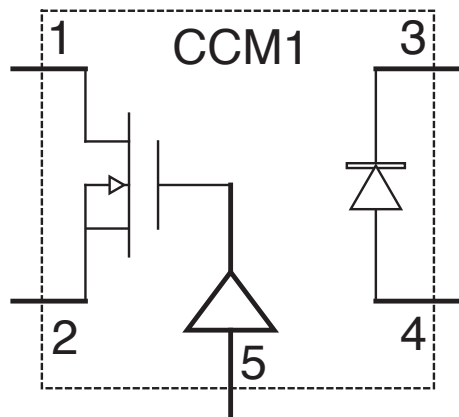


LTspice Symbol

Subcircuit

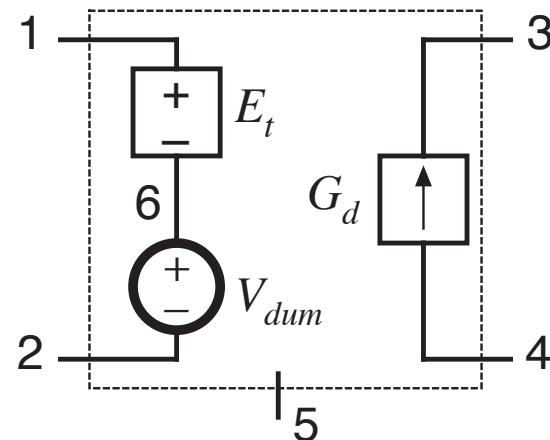


Subcircuit

Average Switch Modeling in DCM

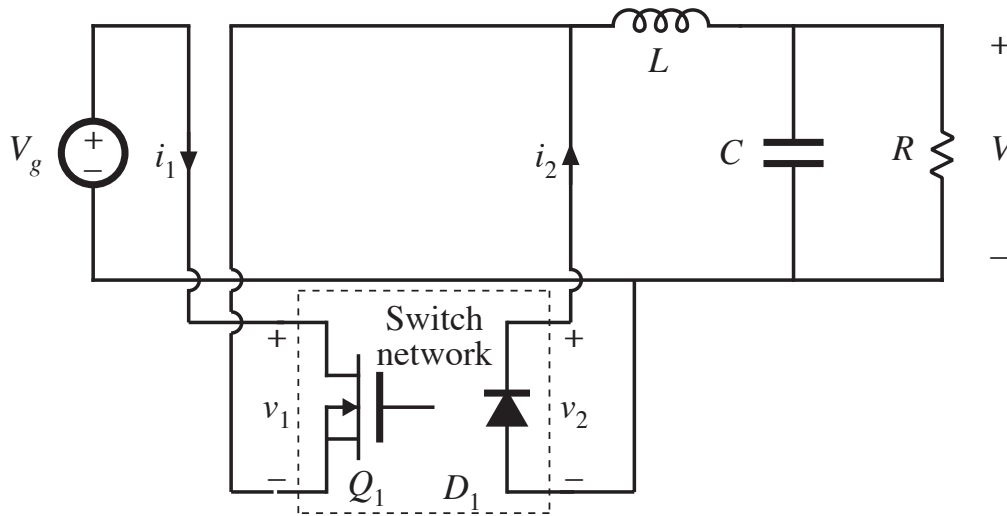


Discontinuous Conduction Mode (DCM) Operation

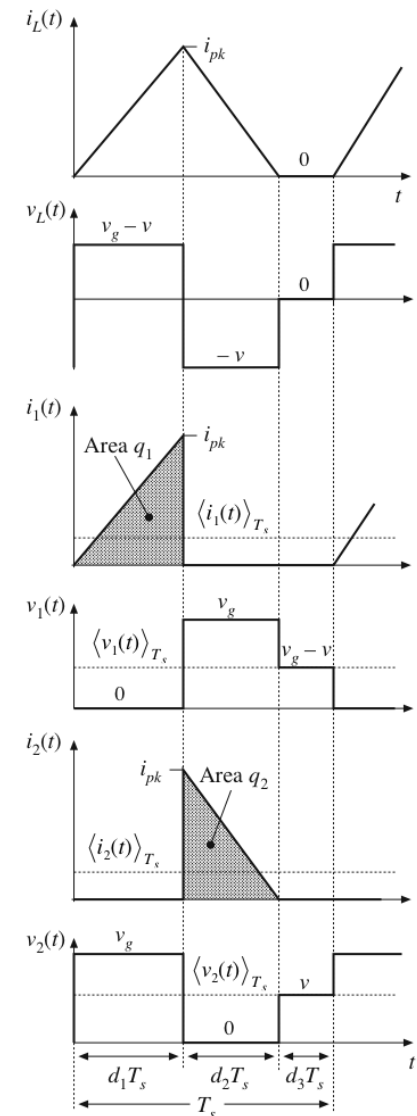- Again find average values of switch network terminal voltages and currents
- Eliminate variables external to the switch network



Average Switch Modeling in DCM

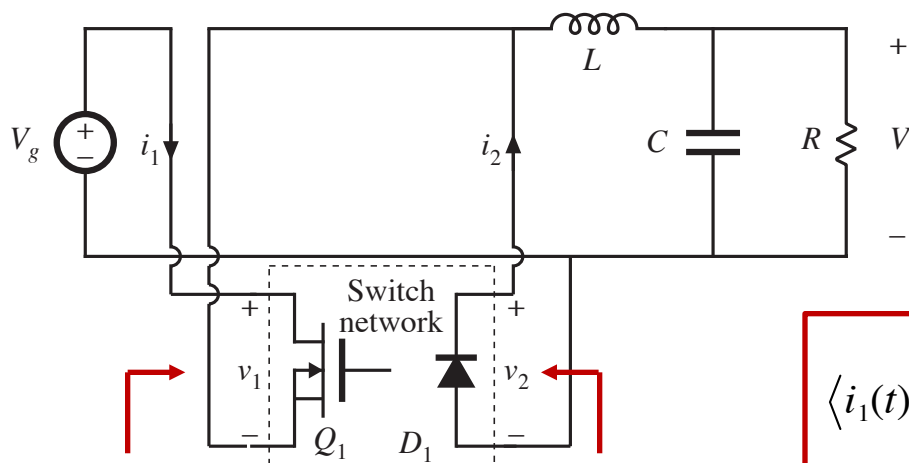

Port 1

Port 2

Port 1


$$\langle i_1(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \langle v_1(t) \rangle_{T_s}$$

$$\langle i_1(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}}{R_e(d_1)}$$

$$R_e(d_1) = \frac{2L}{d_1^2 T_s}$$

Port 2
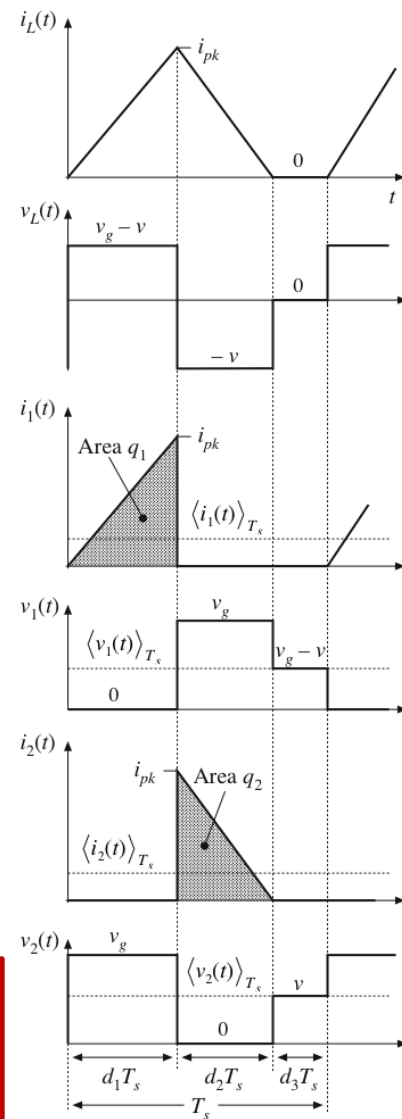
$$\langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}^2}{R_e(d_1)} = \langle p(t) \rangle_{T_s} \Rightarrow \langle i_2(t) \rangle_{T_s} = \frac{d_1^2(t) T_s}{2L} \frac{\langle v_1(t) \rangle_{T_s}^2}{\langle v_2(t) \rangle_{T_s}}$$





Averaged Model of Switch Network under DCM

$$\langle i_1(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}}{R_e(d_1)}$$



$$R_e(d_1) = \frac{2L}{d_1^2 T_s}$$
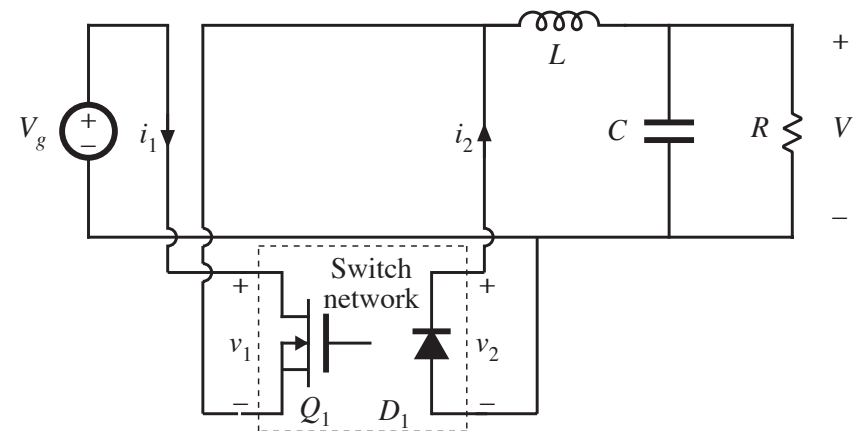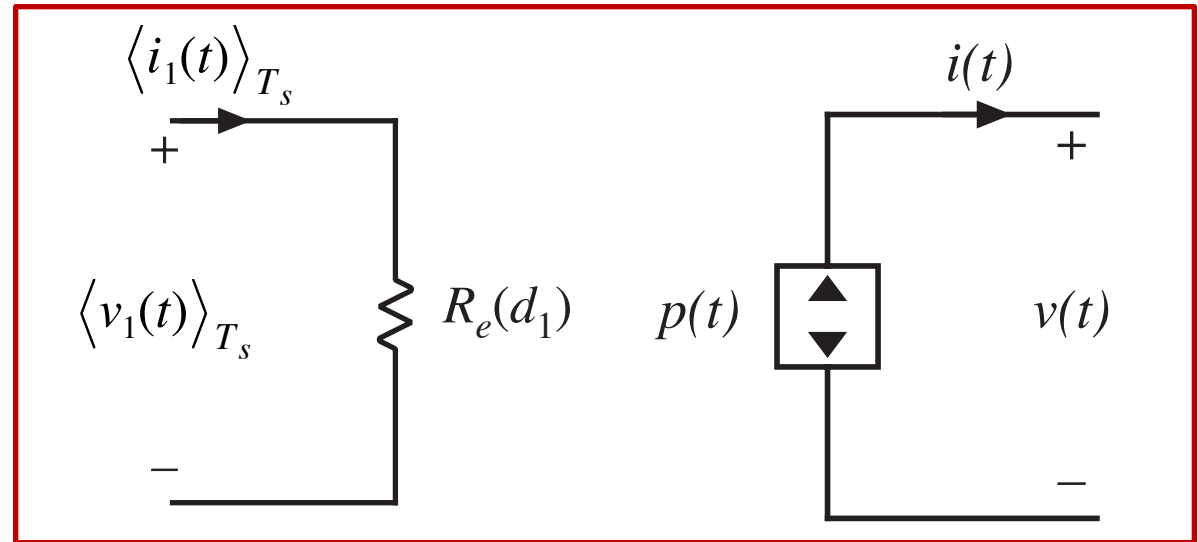
$$\langle i_2(t) \rangle_{T_s} \langle v_2(t) \rangle_{T_s} = \frac{\langle v_1(t) \rangle_{T_s}^2}{R_e(d_1)} = \langle p(t) \rangle_{T_s}$$




Summary of Averaged Switch Models


Switch Network

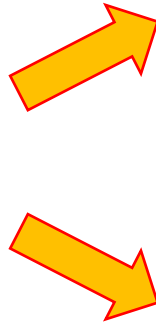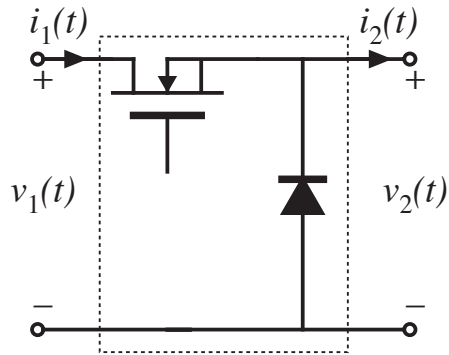

Averaged Switch Models

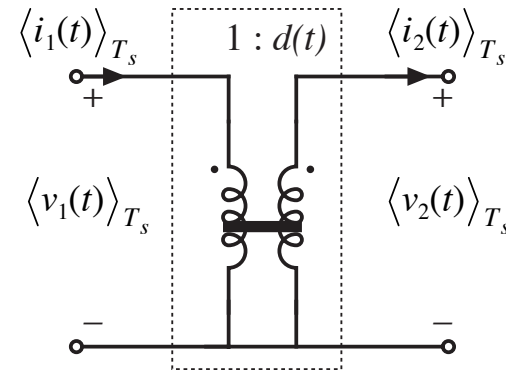

CCM

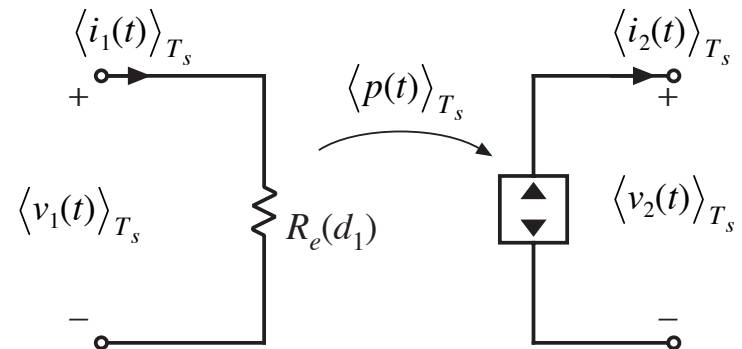


DCM

SPICE Model CCM-DCM1


```
*****
* MODEL: CCM-DCM1
* Application: two-switch PWM converters, CCM or DCM
* Limitations: ideal switches, no transformer
*****
* Parameters:
*   L=equivalent inductance for DCM
*   fs=switching frequency
*****
* Nodes:
* 1: transistor positive (drain of an n-channel MOS)
* 2: transistor negative (source of an n-channel MOS)
* 3: diode cathode
* 4: diode anode
* 5: duty cycle control input
*****
.subckt CCM-DCM1 1 2 3 4 5
+ params: L=100u fs=1E5
Et 1 2 value={MIN((1-v(5))*v(v2)/v(5), i(Va)*2*L/(V(5)*V(5))*fs)}
Gd 4 3 value={MIN((1-v(5))*i(Va)/v(5), i(Va)*i(Va)*2*L*fs/(V(5)*V(5)*V(v2)))}
Ga 0 a value={MAX(i(Et),0)}
Va a b
Ra b 0 10k
Ef v2 0 value={MAX(V(3,4),0)}
Rb v2 0 1k
.ends
*$
*****
```

Combined CCM/DCM switch
model available inside switch.lib

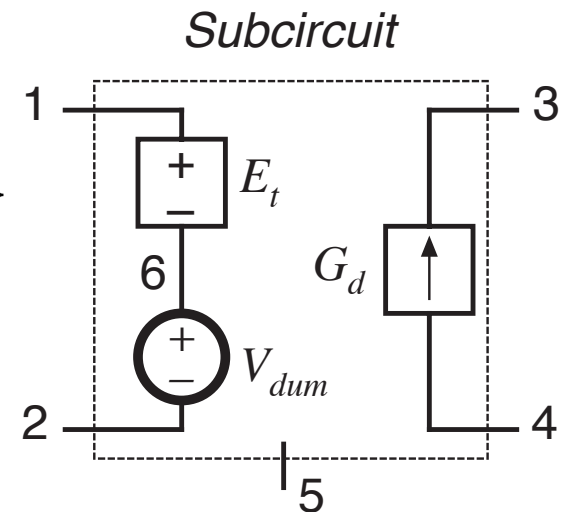This averaged model
automatically switches
between CCM and
DCM as necessary



Simulation of Buck Converter in SPICE

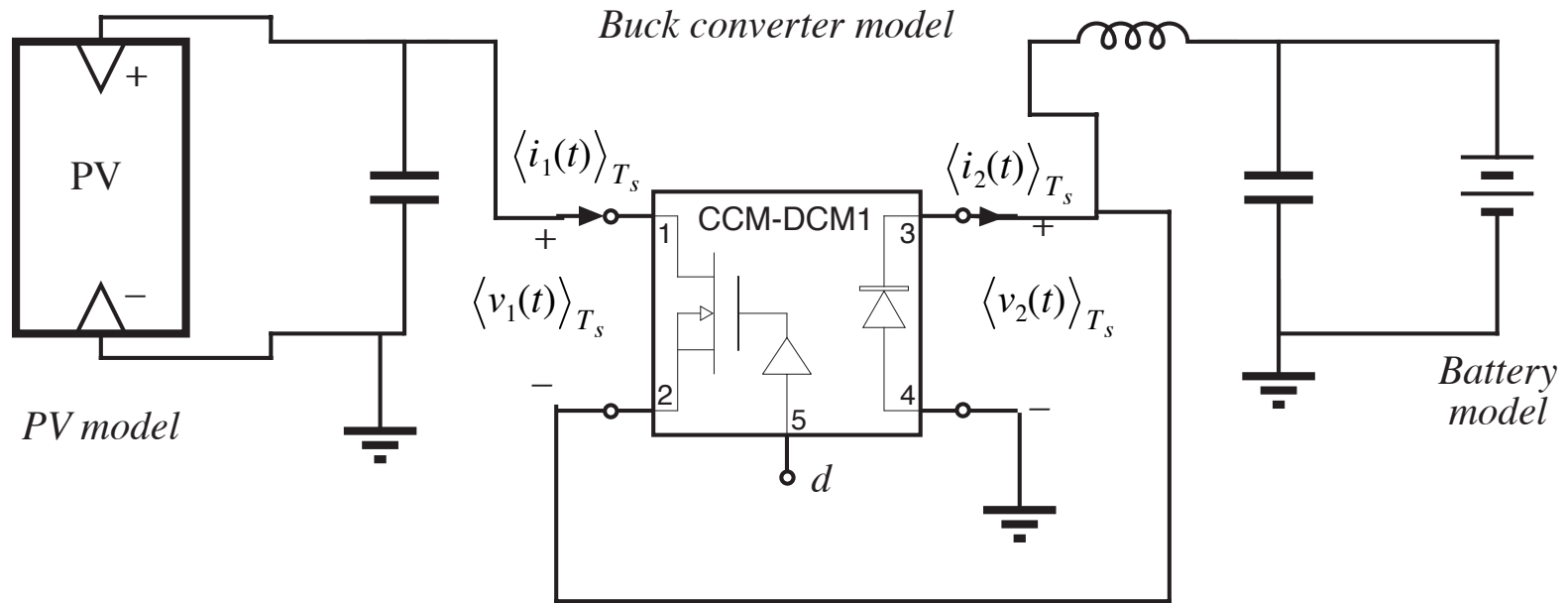

- Replace buck converter switches with averaged switch model CCM-DCM1
- CCM-DCM1 and other SPICE model library elements are available from:
<http://ecee.colorado.edu/ecen4517/pspicelib/index.html>
- Use your PV model from Experiment 1


Frequency Response (AC Analysis) in SPICE

- Given a nonlinear time-invariant circuit, as on the previous slide, SPICE can automatically perturb, linearize, and plot small-signal ac transfer functions
 - Use DC sources to set up the correct quiescent operating conditions
 - Include an AC source having amplitude 1
- When you perform an AC analysis, SPICE will:
 - Do a DC analysis to find the quiescent operating point
 - Linearize all nonlinear elements at this point, to construct a linear model
 - Perform an AC (phasor) analysis at specified frequencies to find the magnitudes and phases of all signals
 - Construct Bode plots of selected signals; with an input amplitude of 1, the signal magnitude and phase plot is the transfer function

SEPIC Frequency Response Example

Ideal SEPIC frequency response
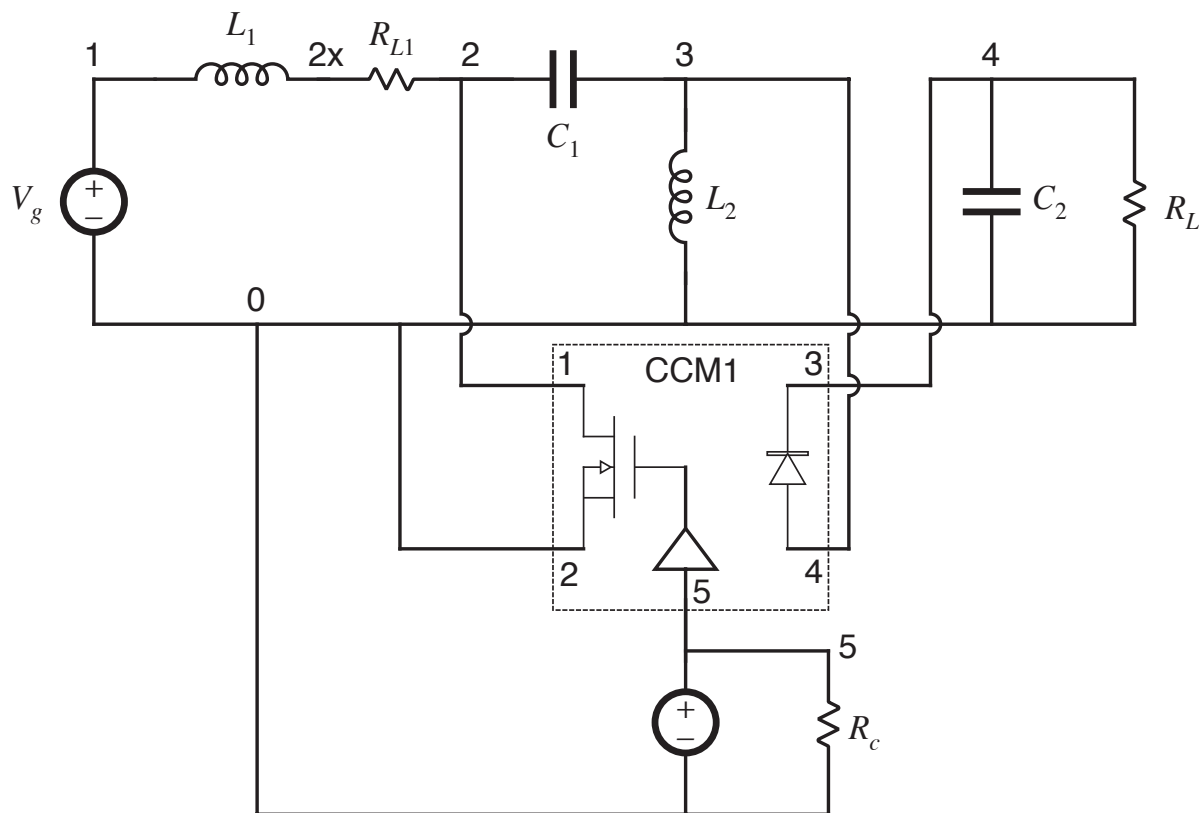
```
.lib switch.lib
Vg 1 0 dc 120V
L1 1 2x 800uH
RL1 2x 2 1U
C1 2 3 100uF
L2 3 0 100uH
C2 4 0 100uF
RL 4 0 40
Vc 5 0 dc 0.4 ac 1
Rc 5 0 1M
Xswitch 2 0 4 3 5 CCM1
.ac DEC 201 10 100kHz
.PROBE
.end
```



AC Analysis of SEPIC in SPICE

