

ECEN 4517/5517

Power Electronics and Photovoltaic Power Systems Laboratory


Lecture 7

**Cascaded Boost Converter using
Analog Pulse Width Modulator**

Announcements


- Exp 3-2 Lab Report due by 11:59 pm (MT) on Friday March 10, 2017
- This week's lab: Start Experiment 4
 - Have 3 weeks to work on Experiment 4
 - Exp 4 Lab Report due by 11:59 pm (MT) on Friday April 7, 2017
- Following this: Experiment 5
 - Experiment 5 has a pre-lab (due 11:59 pm on Friday March 24, 2017)
 - Have 2 weeks to work on Experiment 5 (after Spring Break)
 - Exp 5 Lab Report due by 11:59 pm (MT) on Friday April 21, 2017

Experiments

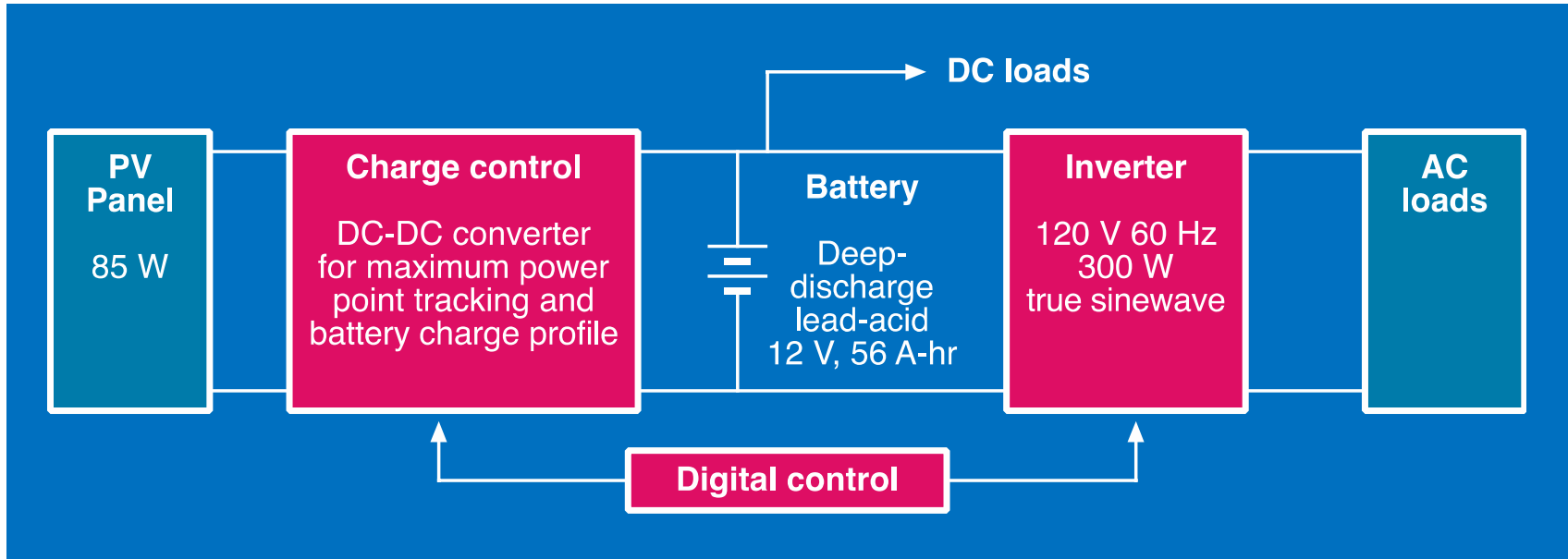


- [Exp 1](#) – PV panel and battery characteristics and direct energy transfer
- [Exp 2](#) – TI MSP430 microcontroller introduction
- [Exp 3-1, 3-2](#) – Buck dc-dc converter for PV MPPT and battery charge control
- [Exp 4](#) – Step-up 12V-200V dc-dc converter
- [Exp 5](#) – Single-phase dc-ac converter (inverter)
- [Expo](#) – Complete system demonstration

Experiment 3-1

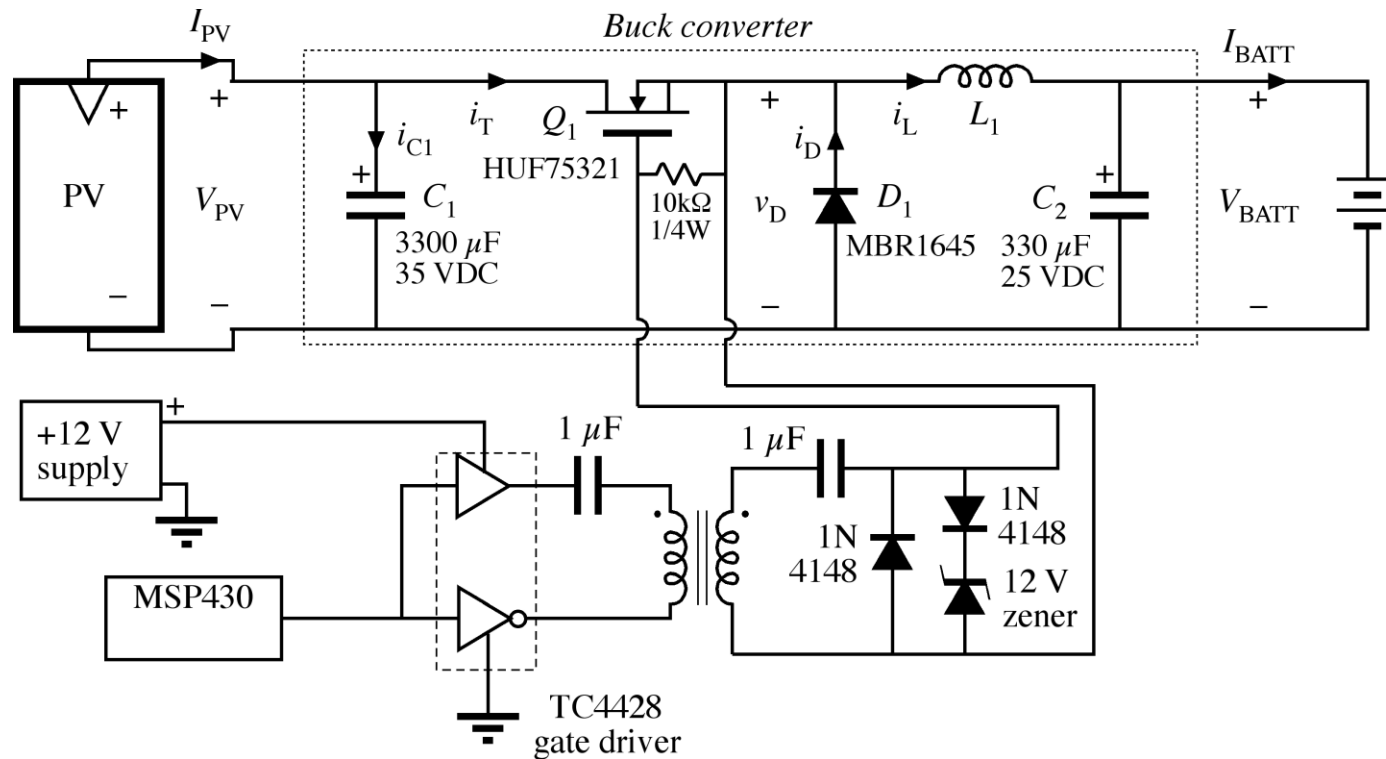


- Demonstrate dc-dc converter power stage operating open loop, driven by MSP430 PWM output:
 - Inside, with input power supply and resistive load
 - Outside, between PV panel and battery
- Compare experimental results with simulation

Experiment 3-2

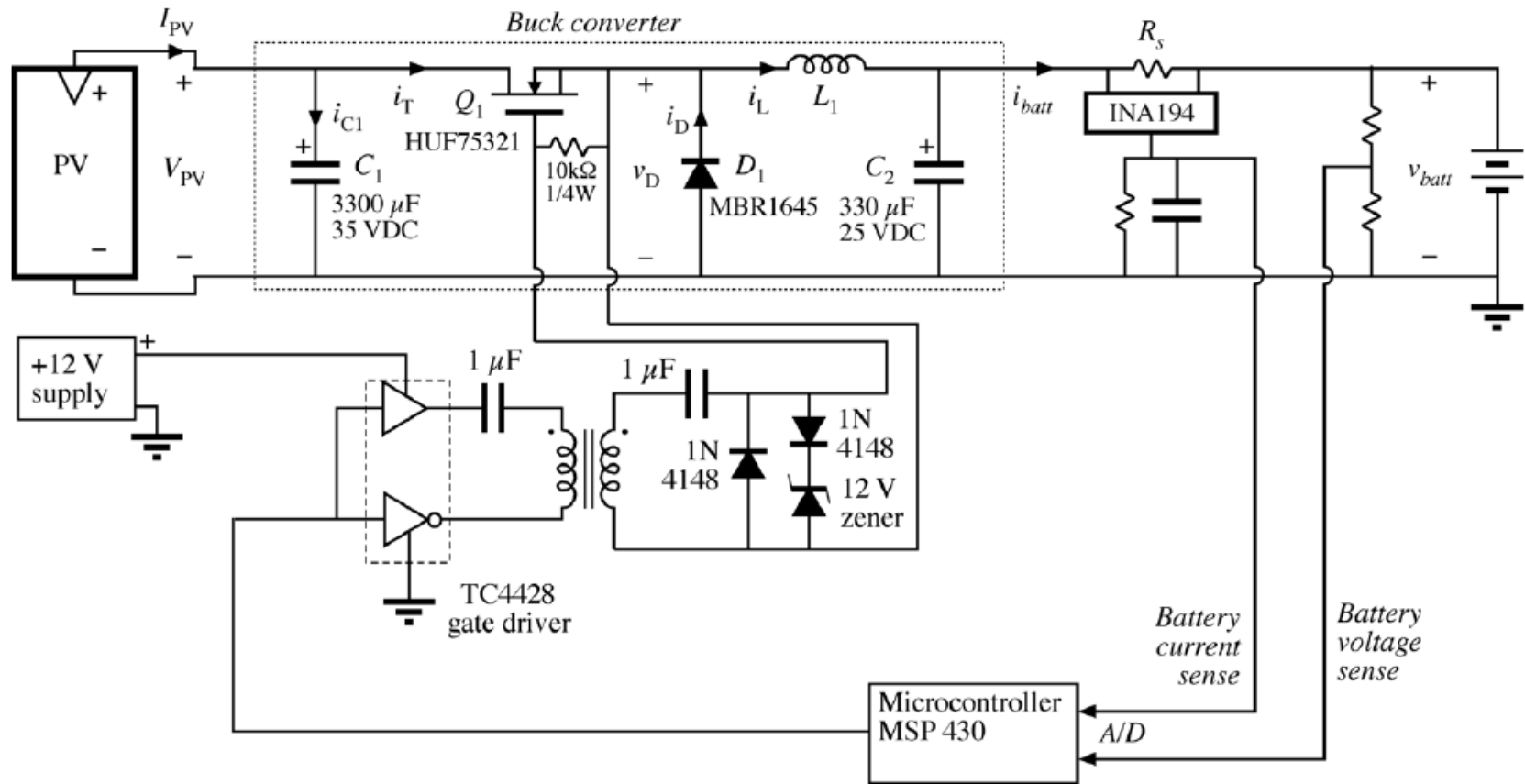

- Demonstrate working sensor circuitry, interfaced to microcontroller
- Demonstrate maximum power point tracking algorithm, outside with converter connected between PV panel and battery

Experiments 4 and 5

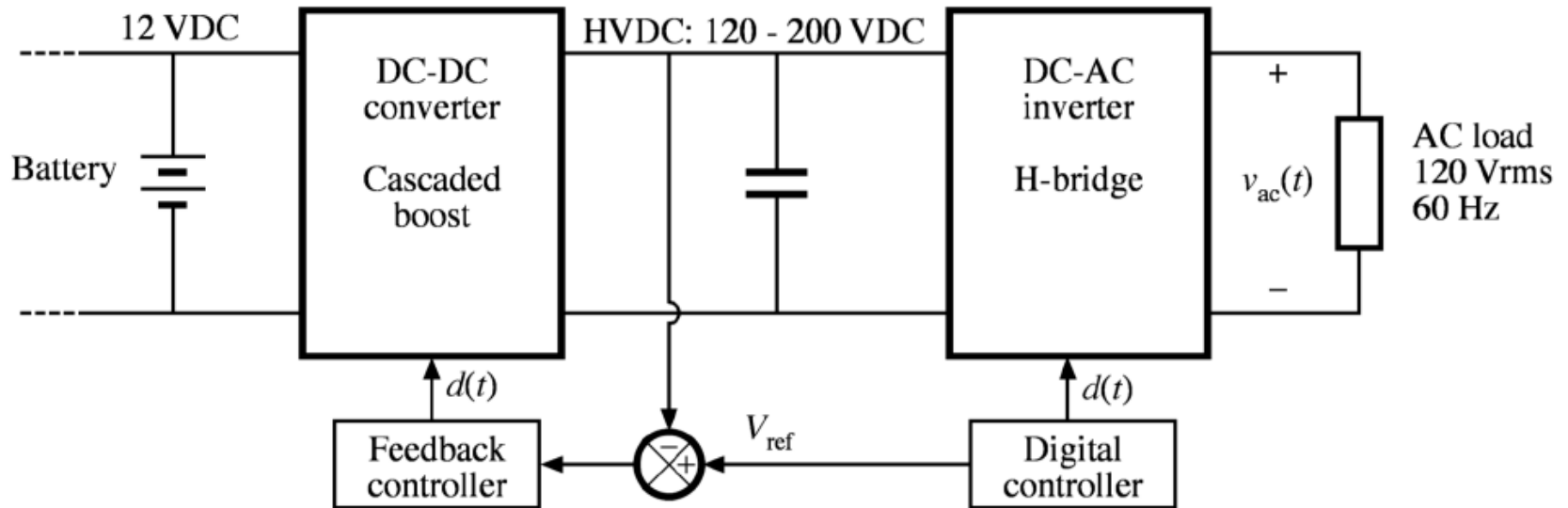

- **Exp 4:** Cascaded boost step-up dc-dc converter (using analog PWM and feedback controller to regulate HVDC)
- **Exp 5:** H-bridge dc-ac inverter


Experiment 4 - Cascaded Boost Converters



- **Controller IC:** Demonstrate operating PWM controller IC (UC 3525)
- **Power Stage:** Demonstrate operating cascaded boost power converters
- **Closed-Loop Analog Control:** Demonstrate analog feedback system that regulates the dc output voltage; and measure and document loop gain and compensator design
- **Additional Analysis [ECEN 5517 Only]:** Develop and verify system loss budget; and analytical model of control-to-output transfer function

Experiment 4 Pre-lab Assignment

- Step up 12 V battery voltage to HVDC (120-200V)
- Will use this for inverter capable of producing same rated power as PV panel (85W)
- Need to choose: duty cycles, switching frequency, inductances
- Design inductors
- Must insure that all components operate within their specified limits
- How much power can you get using the parts in your kit?
- How efficient can your design be?
- Key limitations:
 - MOSFET on-resistances, rated voltages
 - Capacitor rms current ratings, rated working voltages
 - Switching losses
 - Inductor (core & winding) losses, saturation current

 



Example Converter Loss Budget

Operating point: $V_{in} = 13\text{ V}$, $V_{out} = 200\text{ V}$, $P_{out} = 85\text{ W}$

MOSFET conduction loss	2.2 W
Diode conduction loss	1.5 W
Switching loss	3.5 W
Inductor loss (core + dc copper + proximity)	<u>4.3 W</u>
Total loss:	11.5 W
Predicted efficiency:	88%

(must document calculations to support above values)

Analog Pulse Width Modulator Operation

 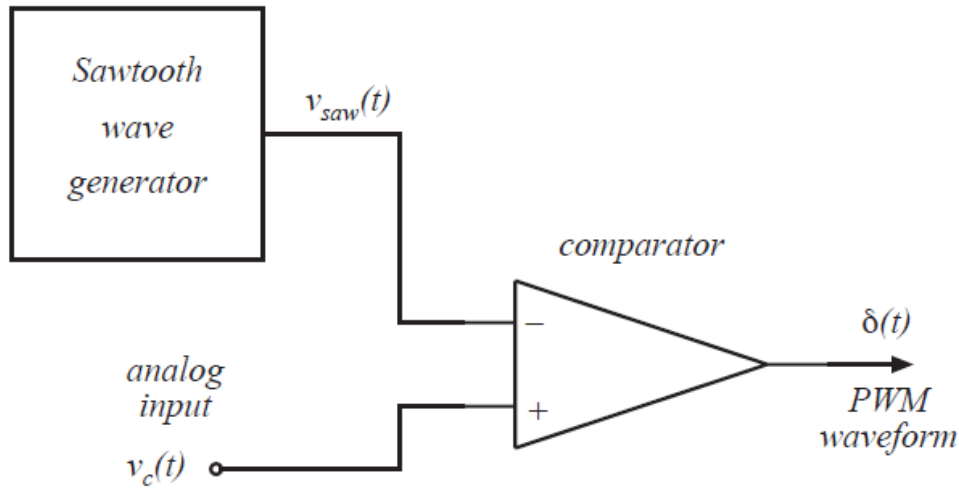

For a linear sawtooth waveform:


$$d(t) = \frac{v_c(t)}{V_M} \quad \text{for } 0 \leq v_c(t) \leq V_M$$

So $d(t)$ is a linear function of $v_c(t)$.


UC3525A Pulse Width Modulator (PWM) IC

Key Functions

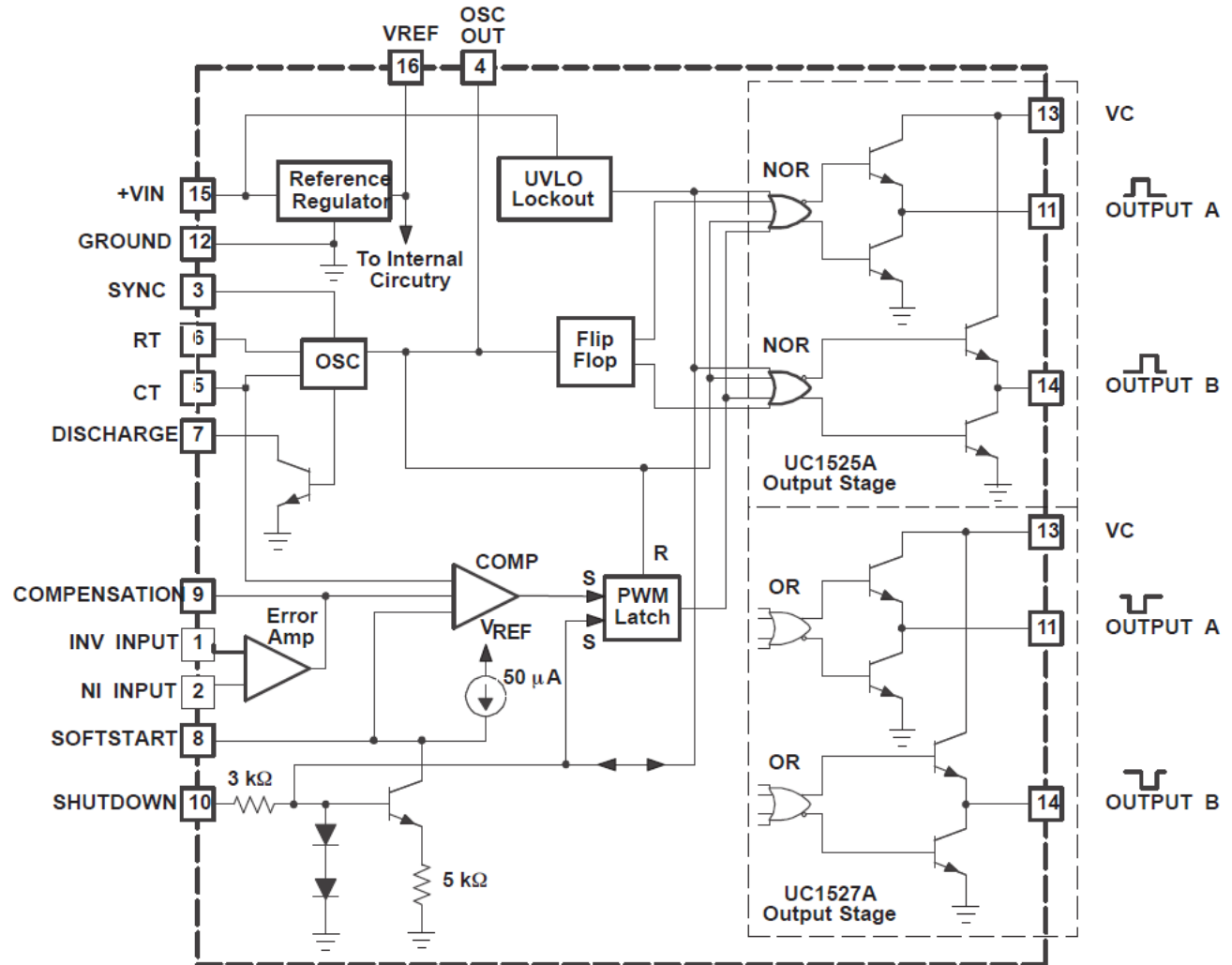
- Sawtooth wave generator (oscillator)
- PWM comparator and latch
- Error amplifier
- 5.1 V reference
- Output drivers
- Shutdown and soft-start circuitry




Sawtooth (Ramp) Oscillator Schematic

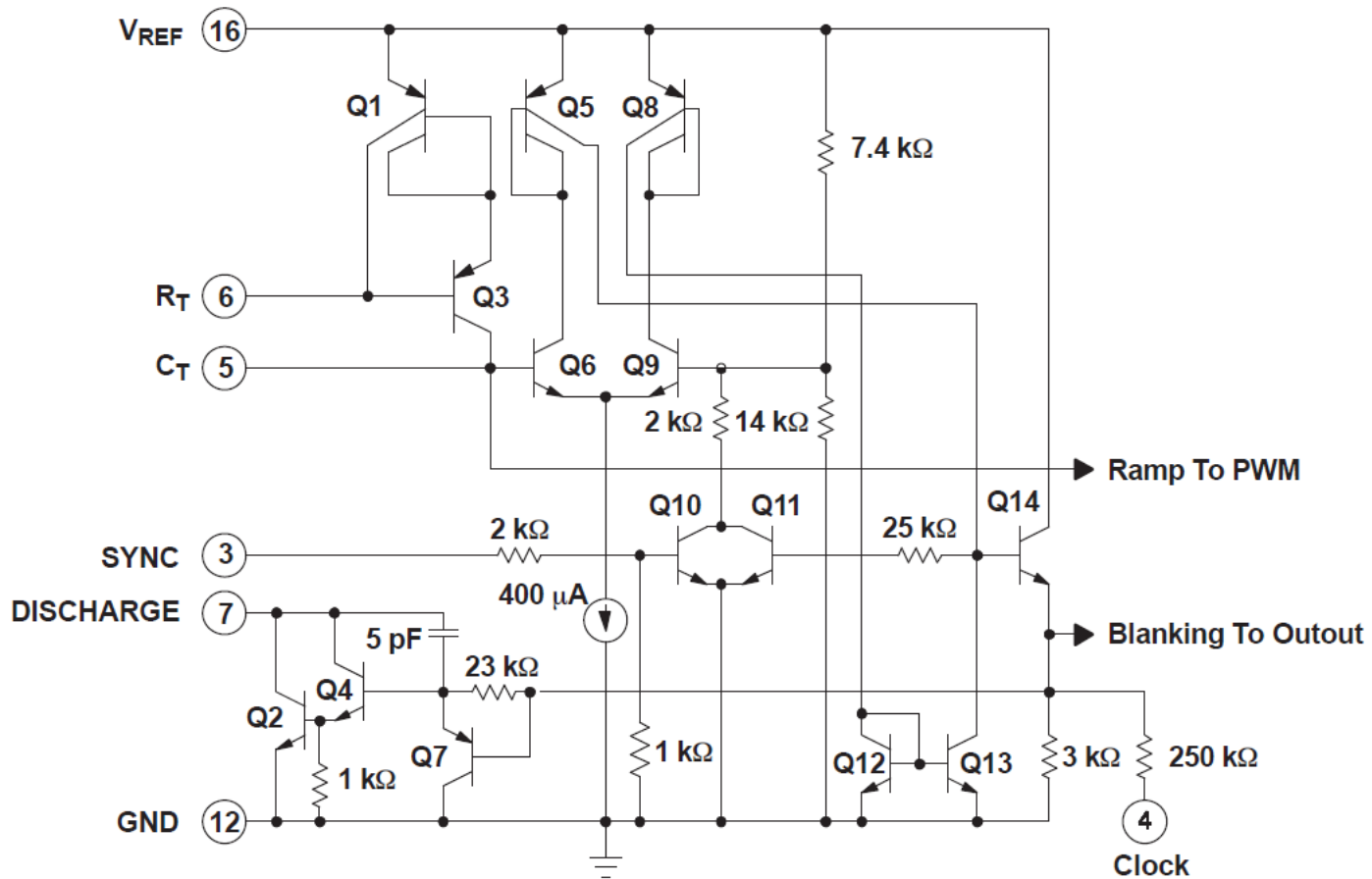

Sawtooth (Ramp) Oscillator Operation

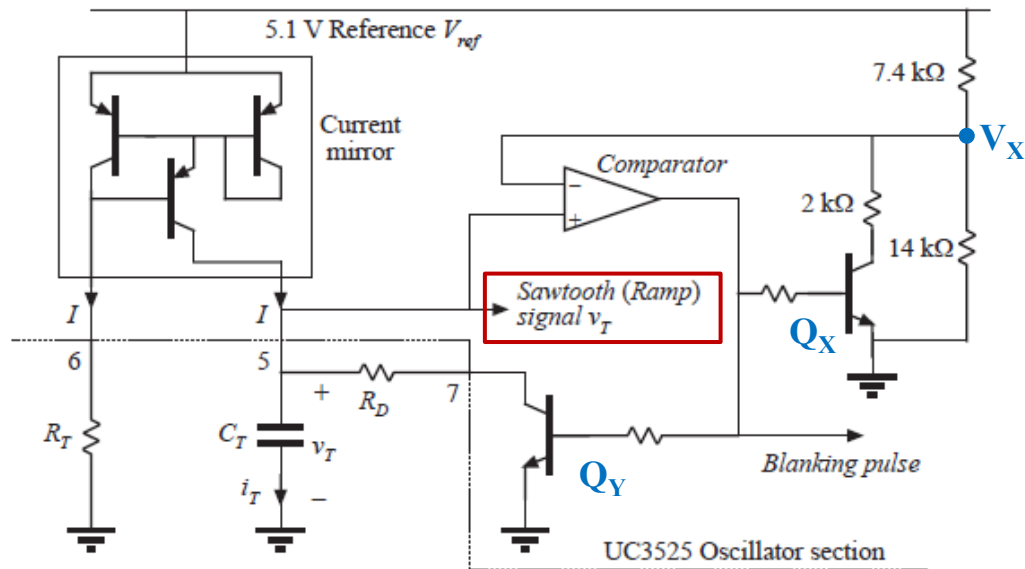
 
$$i_T = C_T \frac{dv_T}{dt} \quad \text{hence} \quad \frac{dv_T}{dt} = \frac{i_T}{C_T}$$



$$I = \frac{(5.1 \text{ V}) - 2(0.7 \text{ V})}{R_T}$$

$$V_{max} = (5.1 \text{ V}) \frac{14 \text{ k}\Omega}{14 \text{ k}\Omega + 7.4 \text{ k}\Omega} = 3.3 \text{ V}$$





$$V_{min} = (5.1 \text{ V}) \frac{(2 \text{ k}\Omega \parallel 14 \text{ k}\Omega)}{(2 \text{ k}\Omega \parallel 14 \text{ k}\Omega) + 7.4 \text{ k}\Omega} = 1.0 \text{ V}$$

Blanking pulse causes driver outputs to be low, so that $dT_s \leq t_c$

Increasing R_D reduces maximum allowed duty cycle D_{max}

- R_T must be greater than 2kΩ; otherwise the UC3525 oscillator will not work
- R_D must be substantially smaller than R_T ; R_D is usually a few hundred Ohms


Error Amplifier

 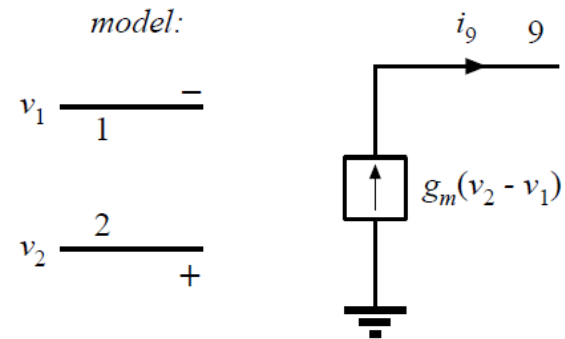 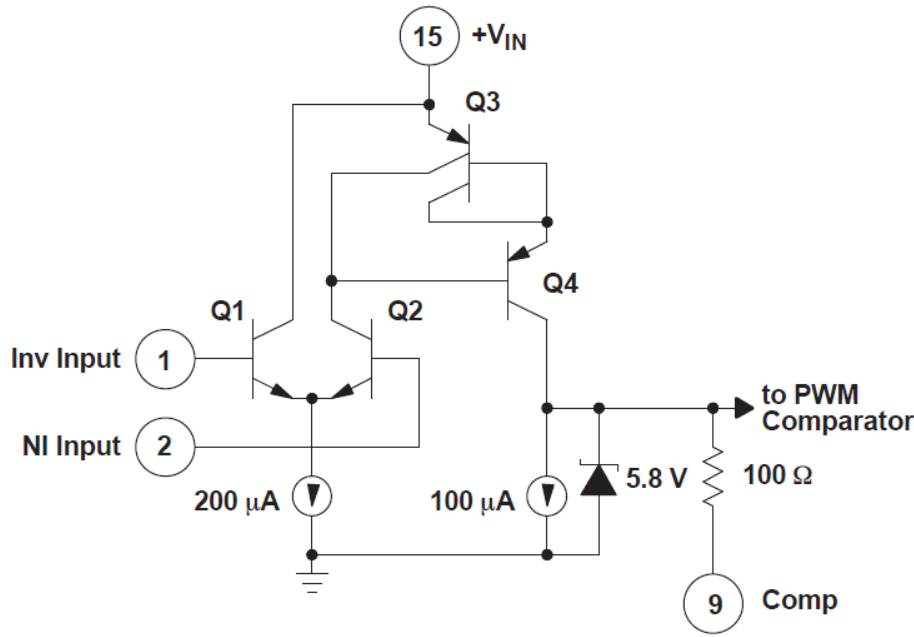

$$v_9 = g_m Z(s)(v_2 - v_1)$$

- The differential voltage gain is: $g_m Z(s)$
- With large $Z(s)$, the differential voltage gain is large; the data sheet specifies a low-frequency differential voltage gain of at least 1000 (60 dB)

 
Adjustable Duty Ratio using Error Amplifier



The error amplifier is connected as a unity-gain stage: $v_{comp} = v_{in}$


The duty cycle D can be adjusted by the external pot.

PWM Function Implementation

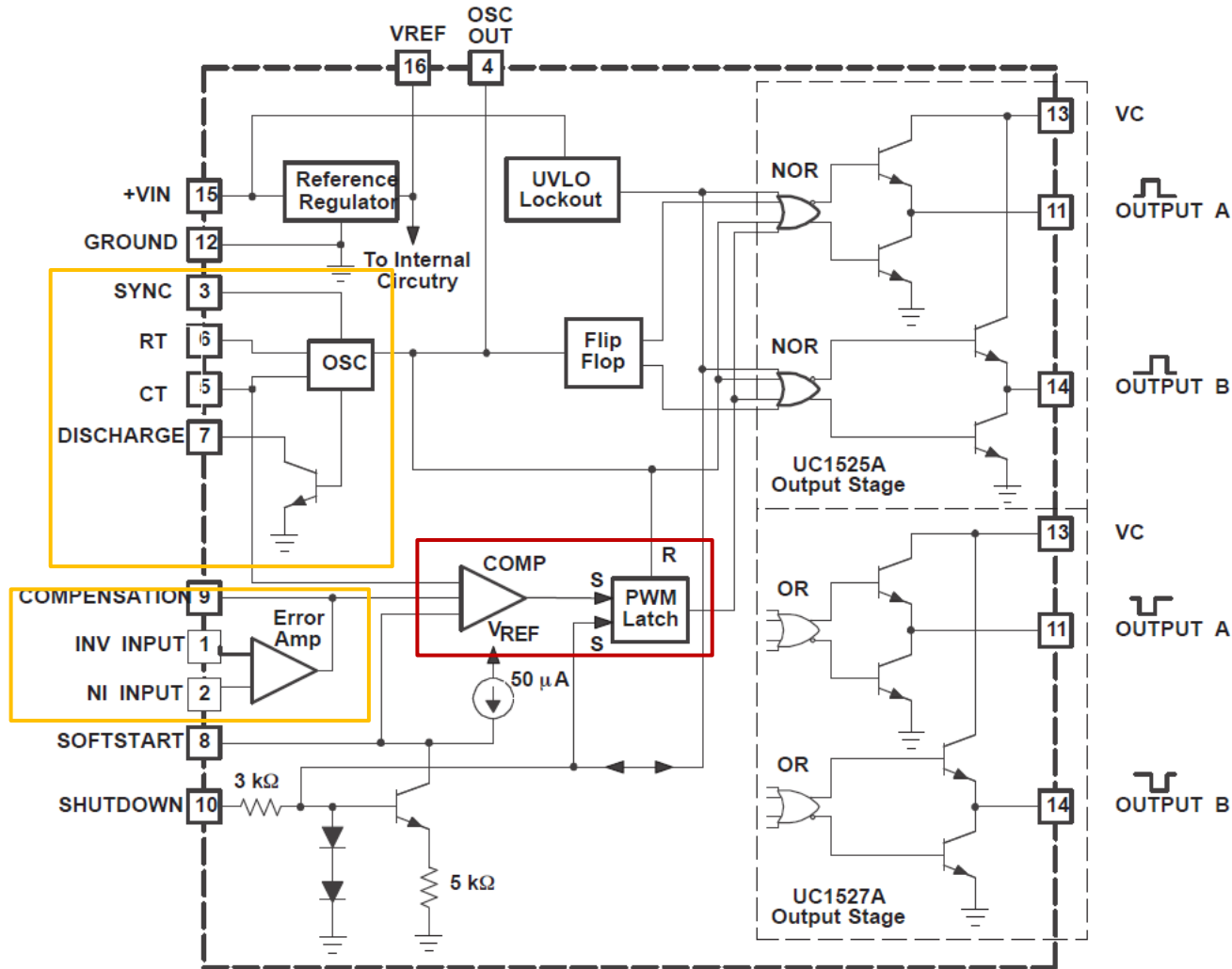


- PWM latch prevents from having multiple pulses in a switching period

Outputs of UC3525A

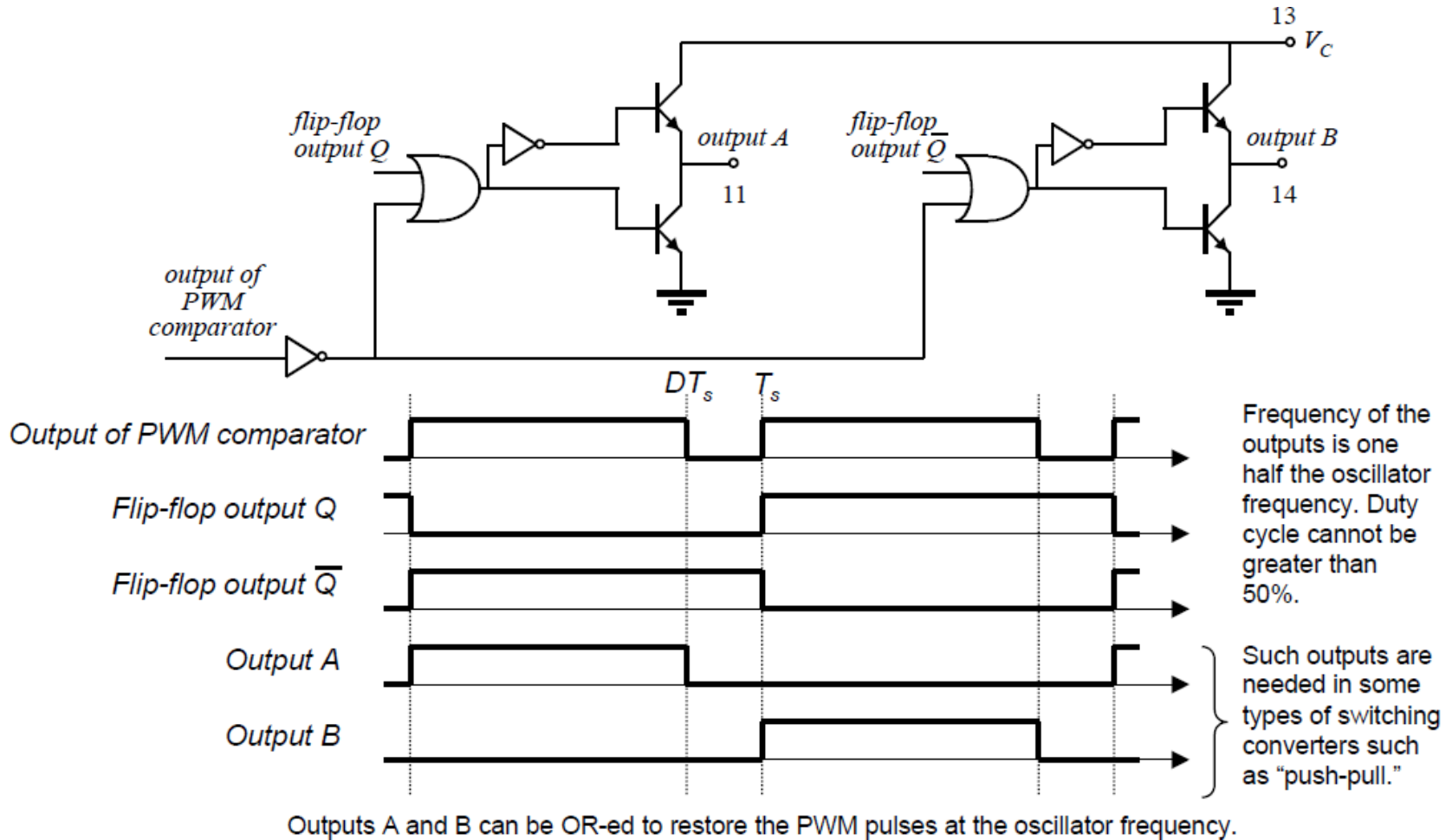

OR-ing the Outputs of UC3525A

 

- A simple way to OR the outputs is using two diodes and a resistor

More Tips

The + 5 V can be obtained from the 5 V reference of the UC3525

Bypass the + 5 V so that the switching EMI of this circuit does not disrupt the internal control circuitry of the UC3525, which also uses the + 5 V.

Soft Start and Shutdown

Soft Start

- A capacitor can be connected to the soft start pin (8); the voltage on this pin limits the maximum duty ratio
- At turn on, the capacitor will start at 0V, and then will charge from the 50 μ A current source; this overrides the feedback loop and starts the converter gently

Shutdown

- The shutdown pin (10) turns off the chip outputs; ground this pin to ensure that the outputs are not shut down

