

# **ECEN 4517/5517**

## **Power Electronics and Photovoltaic Power Systems Laboratory**

### **Lecture 9**


#### **Compensator Design and Modified Sine Wave Inverter**

# Announcements

---


- This week's lab: Finish Experiment 4
  - Exp 4 Lab Report due by 11:59 pm (MT) on Friday April 7, 2017
- Following this: Experiment 5
  - Experiment 5 has a pre-lab (due 11:59 pm on Friday March 24, 2017)
  - Have 2 weeks to work on Experiment 5 (after Spring Break)
  - Exp 5 Lab Report due by 11:59 pm (MT) on Friday April 21, 2017
- Quiz 2 on Monday April 24, 2017
  - In-class 40-minute quiz administered during lecture time
  - Closed book/notes, calculator allowed
  - Will cover Experiment 4 and 5 material
- Expo (Final Demo) on Thursday May 4, 2017

# Experiments

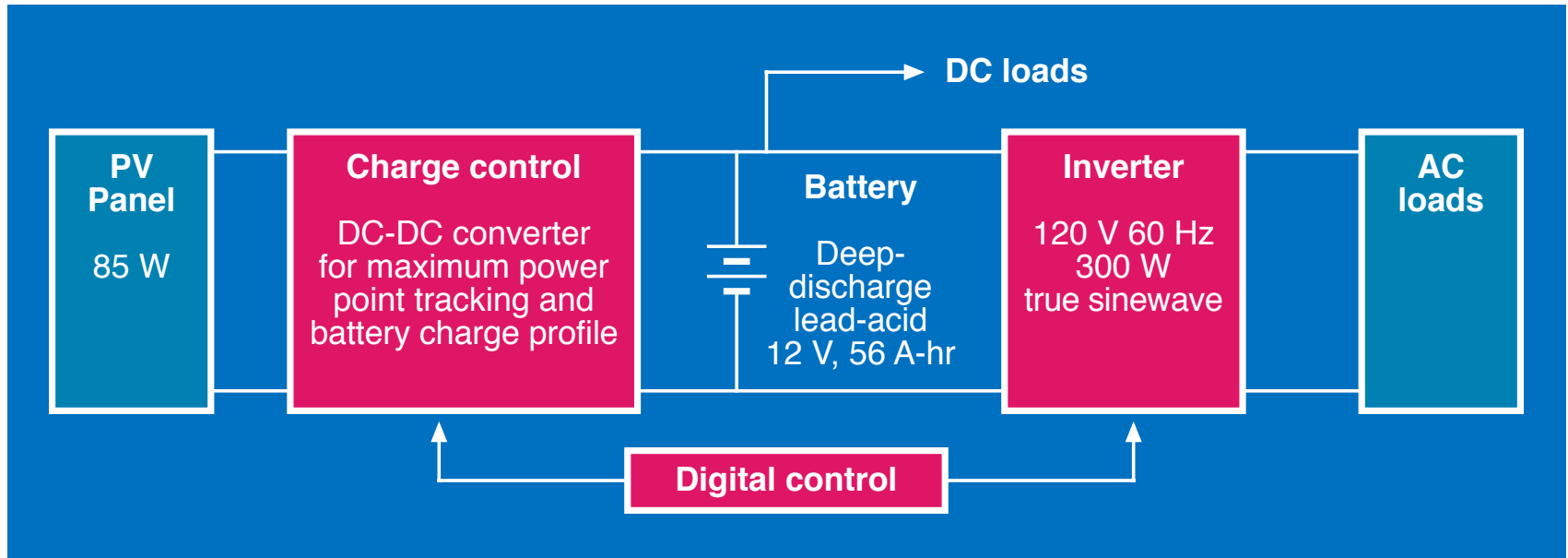


- [Exp 1](#) – PV panel and battery characteristics and direct energy transfer
- [Exp 2](#) – TI MSP430 microcontroller introduction
- [Exp 3-1, 3-2](#) – Buck dc-dc converter for PV MPPT and battery charge control
- [Exp 4](#) – Step-up 12V-200V dc-dc converter
- [Exp 5](#) – Single-phase dc-ac converter (inverter)
- [Expo](#) – Complete system demonstration

# Experiments 4 and 5

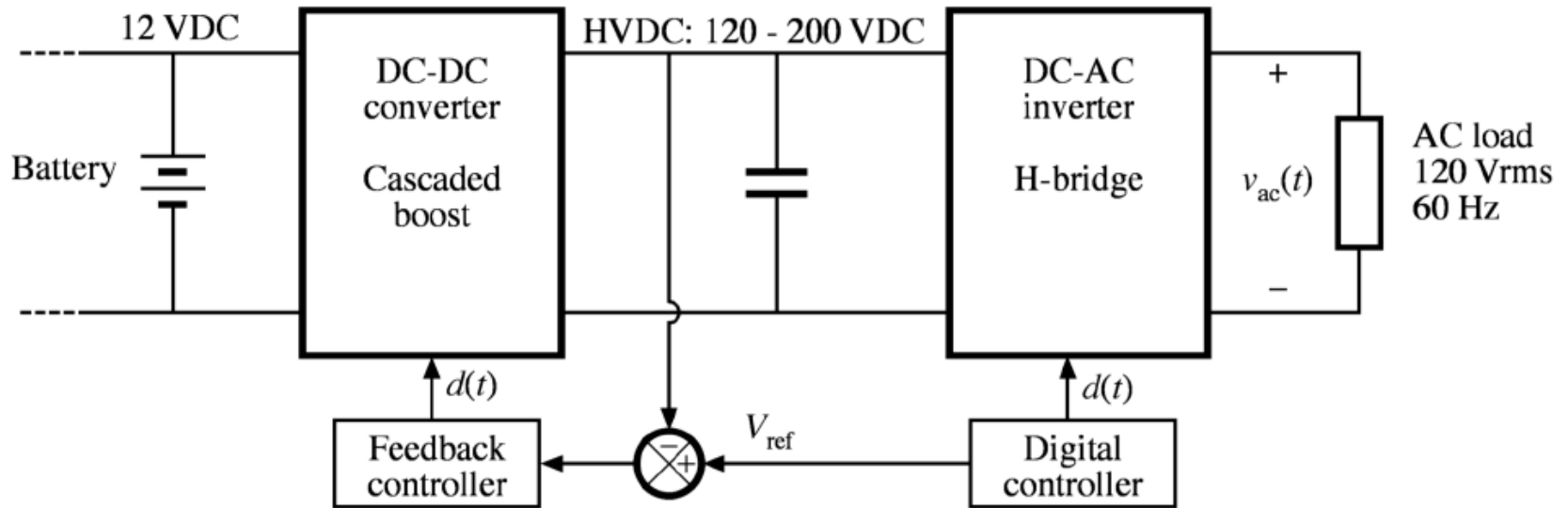

- **Exp 4:** Cascaded boost step-up dc-dc converter (using analog PWM and feedback controller to regulate HVDC)
- **Exp 5:** H-bridge dc-ac inverter

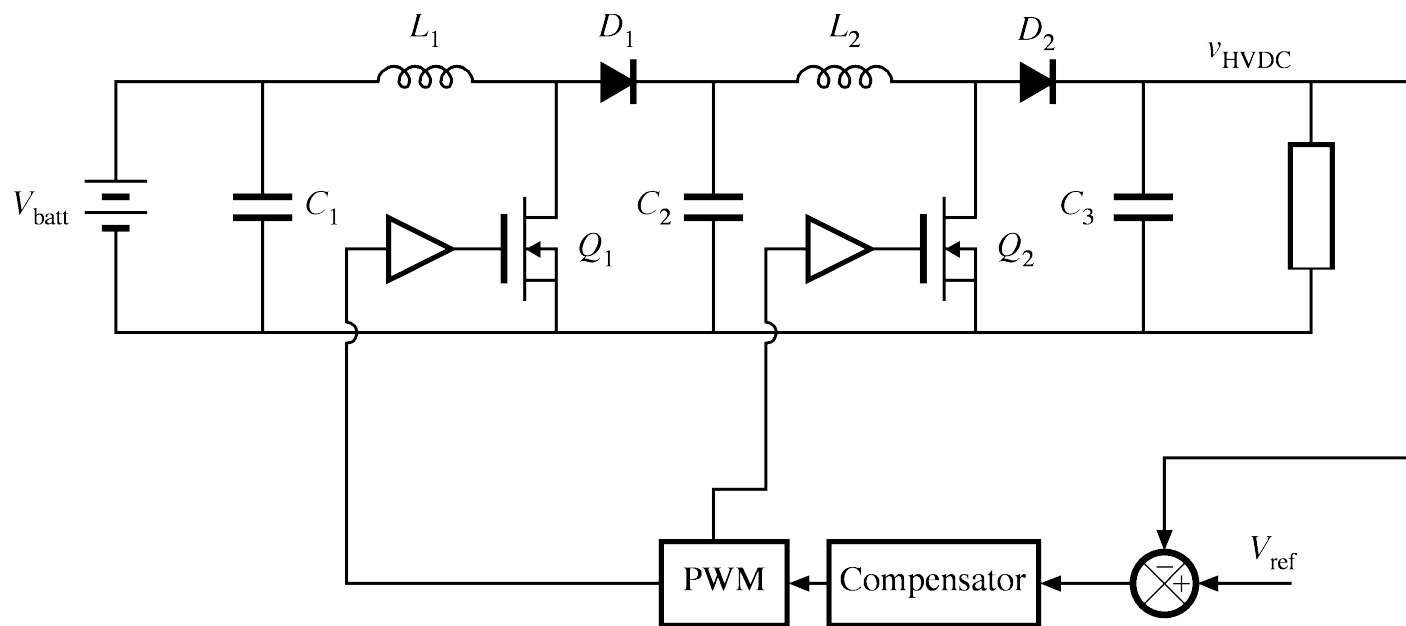
# Experiment 4 - Cascaded Boost Converters



- **Controller IC:** Demonstrate operating PWM controller IC (UC 3525)
- **Power Stage:** Demonstrate operating cascaded boost power converters
- **Closed-Loop Analog Control:** Demonstrate analog feedback system that regulates the dc output voltage; and measure and document loop gain and compensator design
- **Additional Analysis [ECEN 5517 Only]:** Develop and verify system loss budget; and analytical model of control-to-output transfer function
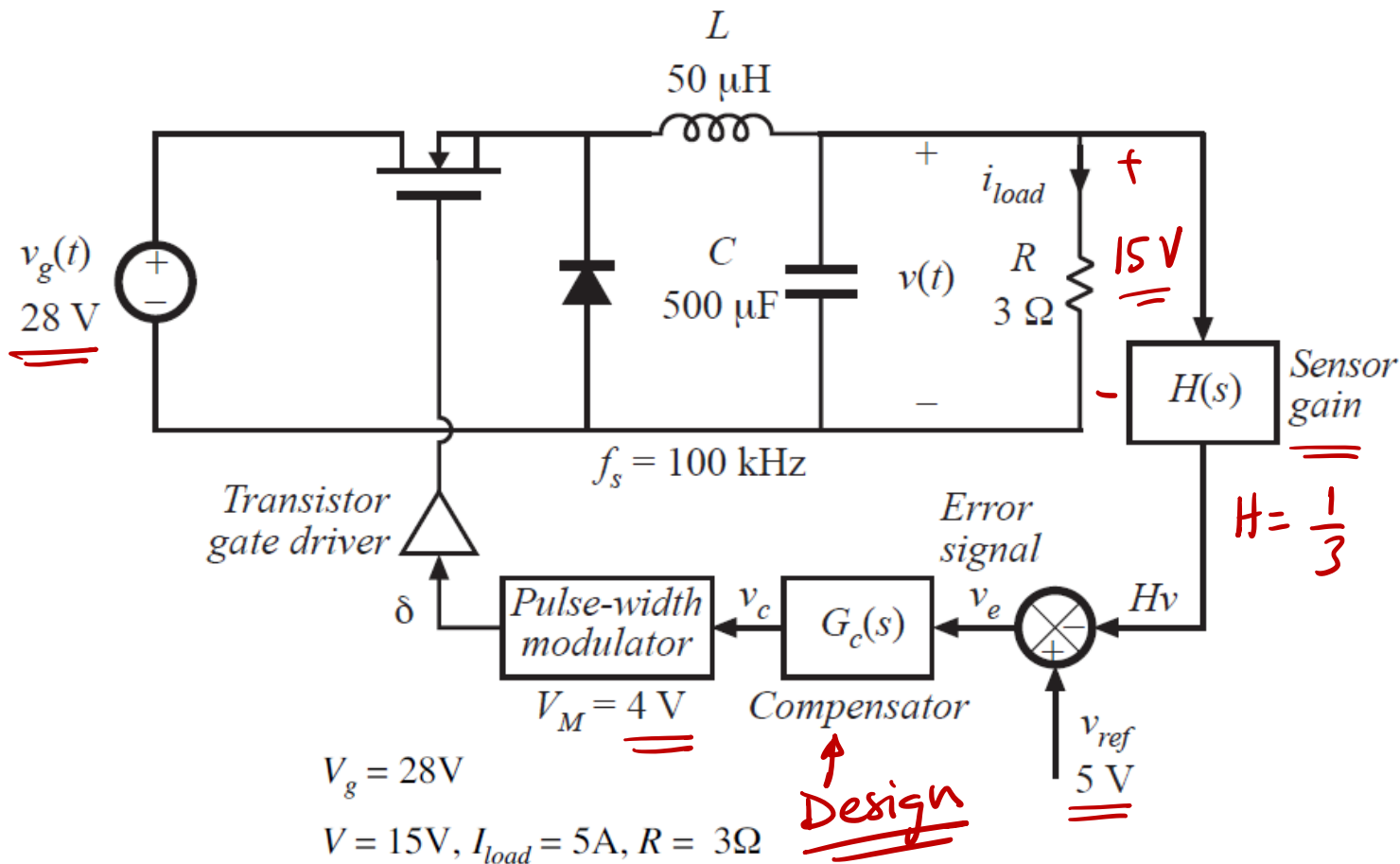
# Compensator Design Example

Also see  
Compensator  
Design  
Example  
notes under  
Experiment 4  
folder on D2L



Input voltage

Output

Quiescent duty cycle

Reference voltage

Quiescent value of control voltage

Gain  $H(s)$

$$V_g = 28\text{ V}$$

$$V = 15\text{ V}, I_{load} = 5\text{ A}, R = 3\ \Omega$$

$$D = 15/28 = 0.536$$

$$V_{ref} = 5\text{ V}$$

$$V_c = DV_M = 2.14\text{ V}$$

$$H = V_{ref}/V = 5/15 = 1/3$$

Design Specifications

$$f_c = 5\text{ kHz}$$

$$\phi_m = 52^\circ$$

# Transfer Functions for Basic CCM Converters

Open-loop control-to-output transfer function:  $G_{vd}(s) = G_{d0} \frac{\left(1 - \frac{s}{\omega_z}\right)}{\left(1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2\right)}$

Open-loop line-to-output transfer function:  $G_{vg}(s) = G_{g0} \frac{1}{1 + \frac{s}{Q\omega_0} + \left(\frac{s}{\omega_0}\right)^2}$


Converter	$G_{g0}$	$G_{d0}$	$\omega_0$	$Q$	$\omega_z$
buck	$D$	$\frac{V}{D}$	$\frac{1}{\sqrt{LC}}$	$R \sqrt{\frac{C}{L}}$	$\infty$
boost	$\frac{1}{D'}$	$\frac{V}{D'}$	$\frac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{L}$
buck-boost	$-\frac{D}{D'}$	$\frac{V}{D D'^2}$	$\frac{D'}{\sqrt{LC}}$	$D'R \sqrt{\frac{C}{L}}$	$\frac{D'^2 R}{D L}$

# Uncompensated Loop Gain

$$T(s) = \frac{G_c(s) H(s)}{V_M} \underbrace{\left( \frac{V}{D} \right)}_{G_{vd}} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left( \frac{s}{\omega_0} \right)^2} \Rightarrow \underline{\underline{T_u(s) = T_{u0} \frac{1}{1 + \frac{s}{Q_0 \omega_0} + \left( \frac{s}{\omega_0} \right)^2}}}$$

$T_{u0} = \frac{H V}{D V_M} = 2.33 \Rightarrow \underline{\underline{7.4 \text{ dB}}}$

$\frac{28}{12} = 2.33$

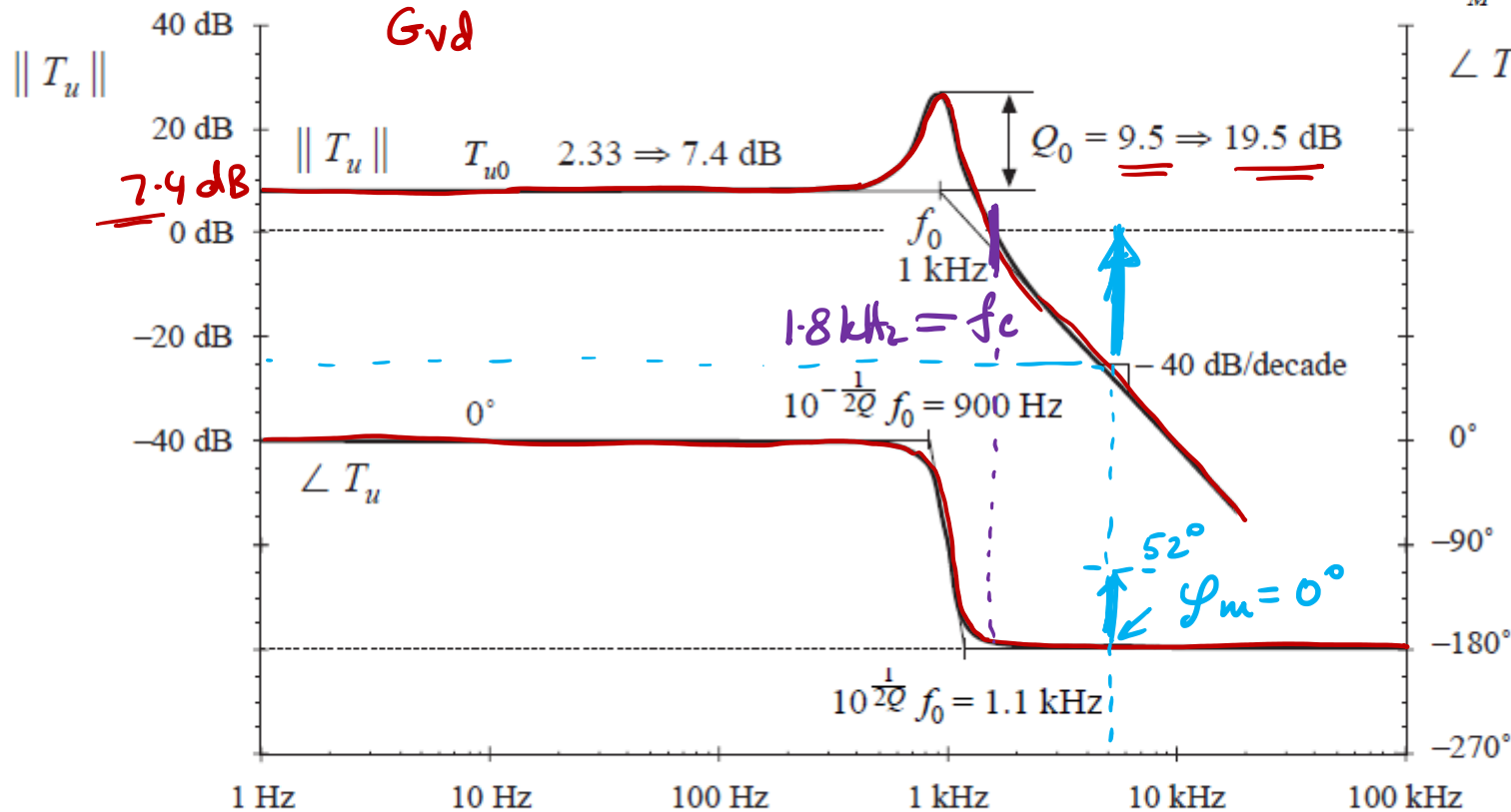

Want

$f_c = 5 \text{ kHz}$

$\phi_m = 52^\circ$

$f_c = 1.8 \text{ kHz}$ ,  $\phi_m = 5^\circ$

$T_u$  has magnitude of  $-20.6 \text{ dB}$  at  $5 \text{ kHz}$   
 $T_u$  has phase of approximately  $-180^\circ$  at  $5 \text{ kHz}$




# Improved Compensator (PID)

PD


$$G_c(s) = G_{cm} \frac{\left(1 + \frac{s}{\omega_z}\right) \left(1 + \frac{\omega_L}{s}\right)}{\left(1 + \frac{s}{\omega_p}\right)}$$

PI

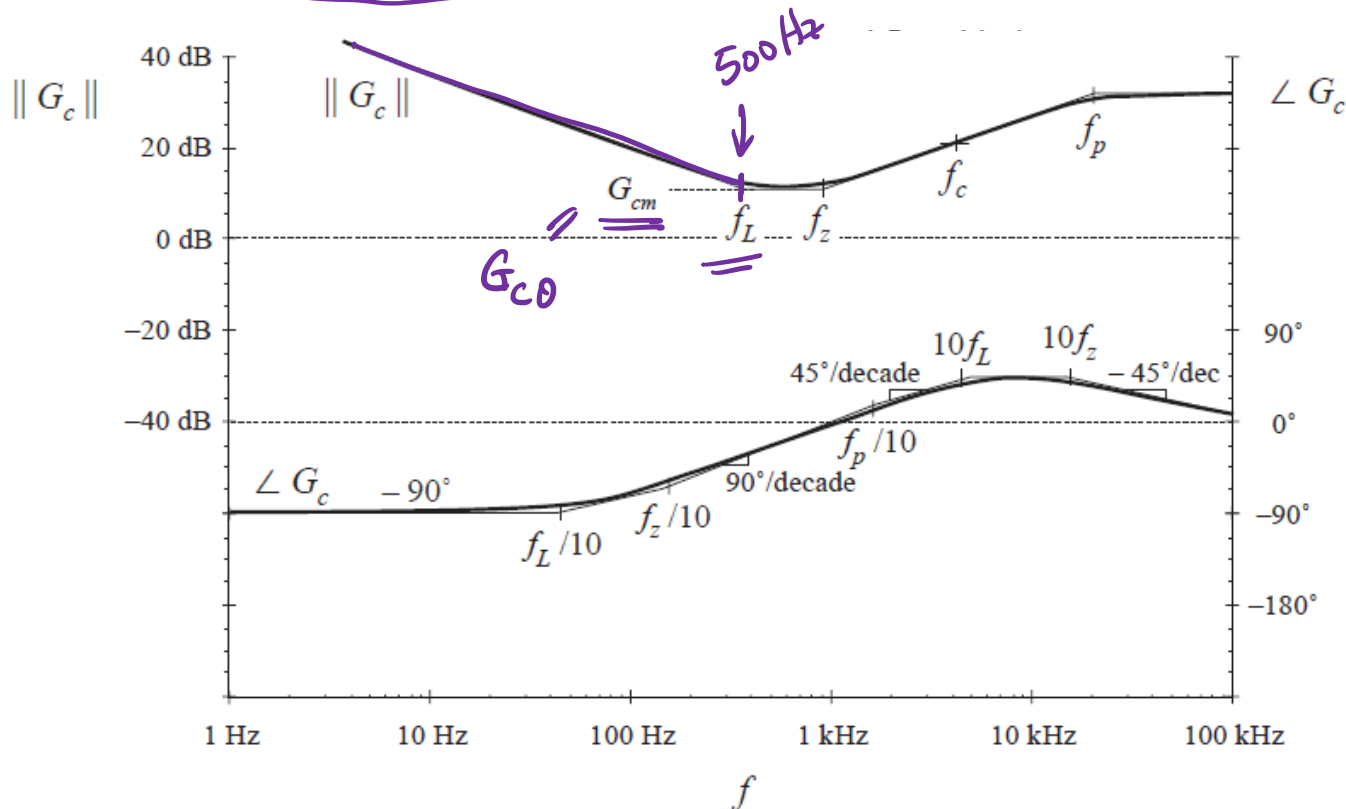



- add inverted zero to PD compensator, without changing dc gain or corner frequencies
- choose  $f_L$  to be  $f_c/10$ , so that phase margin is unchanged
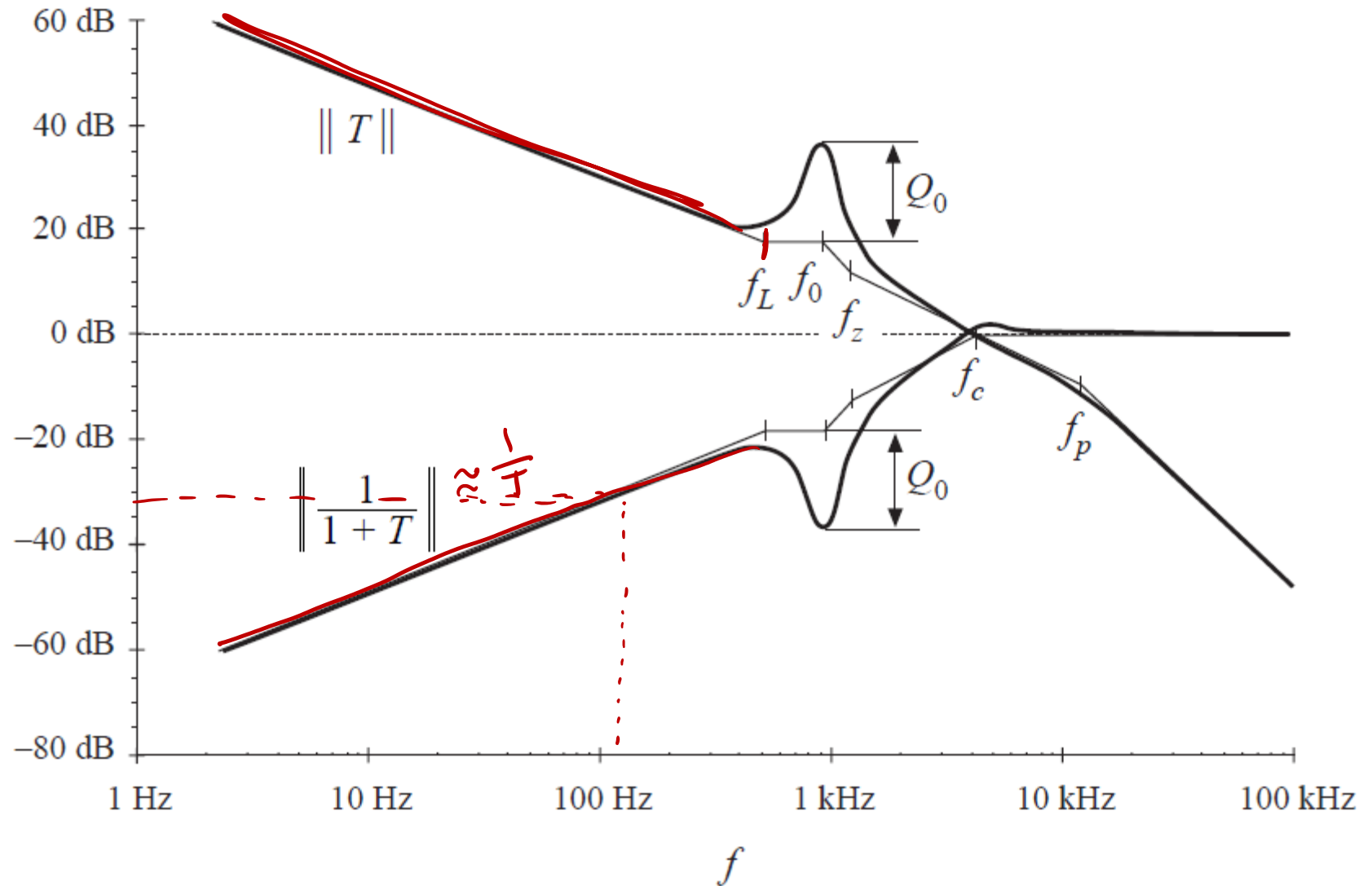
# Loop Gain and $1/(1+T)$ with PID Compensator



# Compensator Implementation

$$v_c = G_c(v_{ref} - Hv)$$

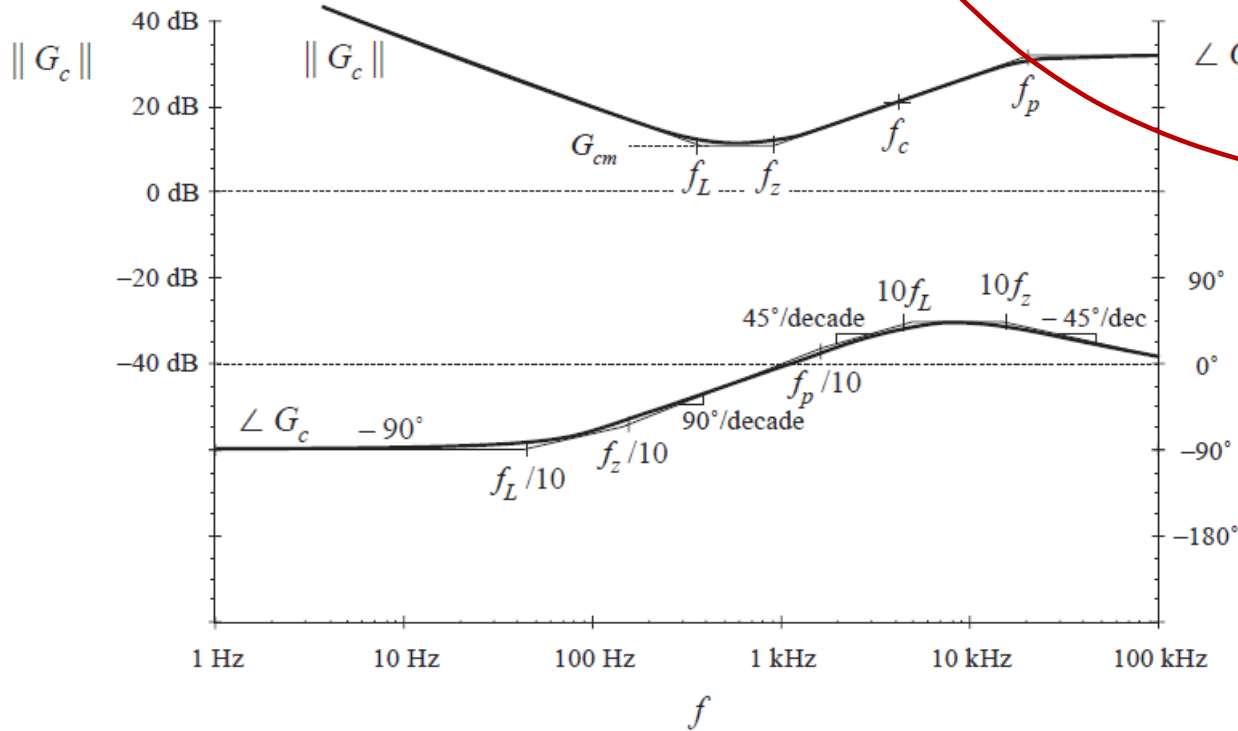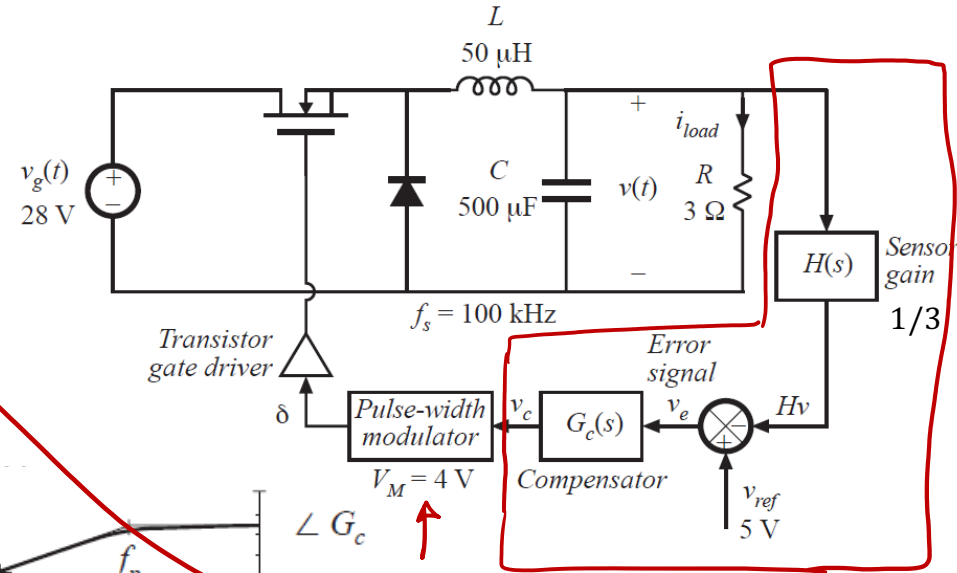


Today's Focus

$$H = \frac{1}{3}$$

$$v_{ref} = 5 \text{ V}$$

# Divider and OpAmp Subtractor

$$v_c = G_c(v_{ref} - Hv)$$

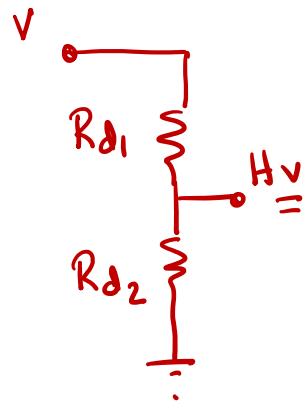


$$v^+ = \frac{z_2}{z_1 + z_2} v_A$$

$$v_o = v^- + z_2 i \quad \& \quad i = \frac{v^- - v_B}{z_1}$$

$$\Rightarrow v_o = v^- + \frac{z_2}{z_1} (v^- - v_B) = v^- \left( \frac{z_1 + z_2}{z_1} \right) - \frac{z_2}{z_1} v_B$$
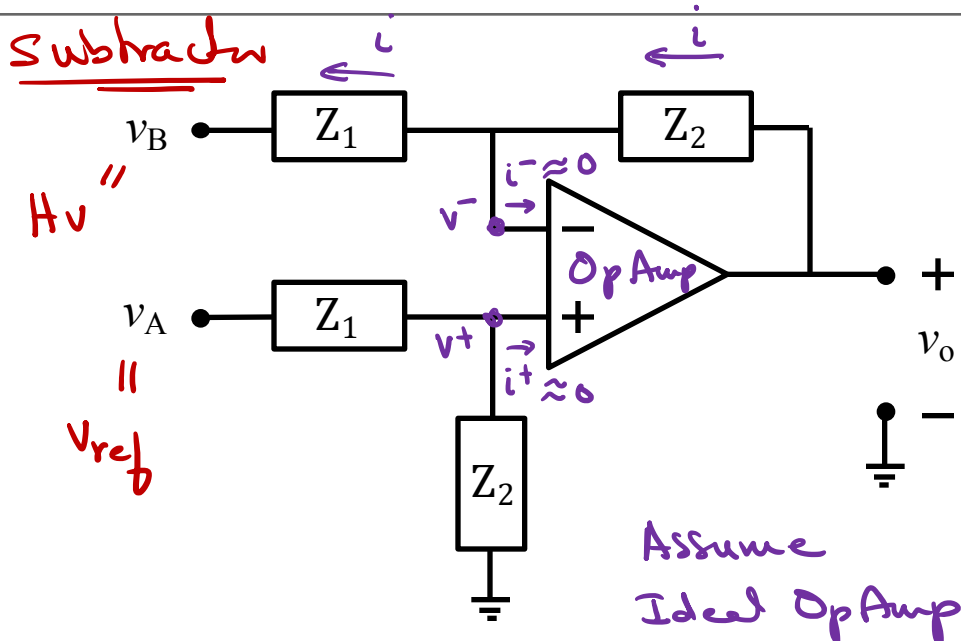
$$\Rightarrow v_o = \frac{z_2}{z_1 + z_2} \left( \frac{z_1 + z_2}{z_1} \right) - \frac{z_2}{z_1} v_B \Rightarrow \boxed{v_o = \frac{z_2}{z_1} (v_A - v_B)}$$



Because of negative feedback in OpAmp  
 $v^+ \approx v^-$



$$v_o = \frac{z_2}{z_1} (v_{ref} - Hv) = v_c$$

$\underbrace{\frac{z_2}{z_1}}_{G_c(s)}$



$$v_o = \frac{Z_2}{Z_1} (v_A - v_B)$$

# Implementing $Z_1$ and $Z_2$

$$G_c(s) = \frac{Z_2(s)}{Z_1(s)}$$

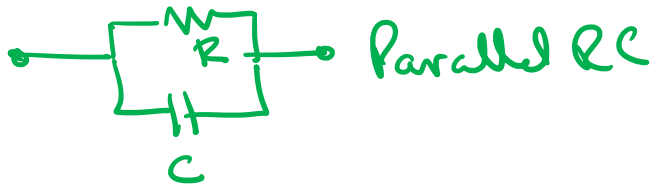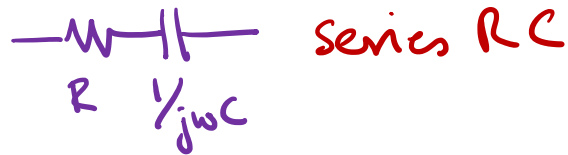

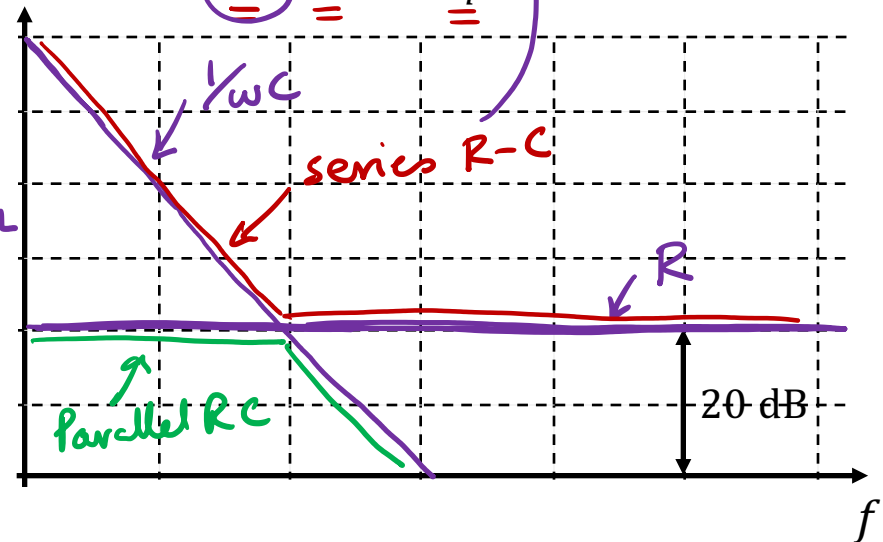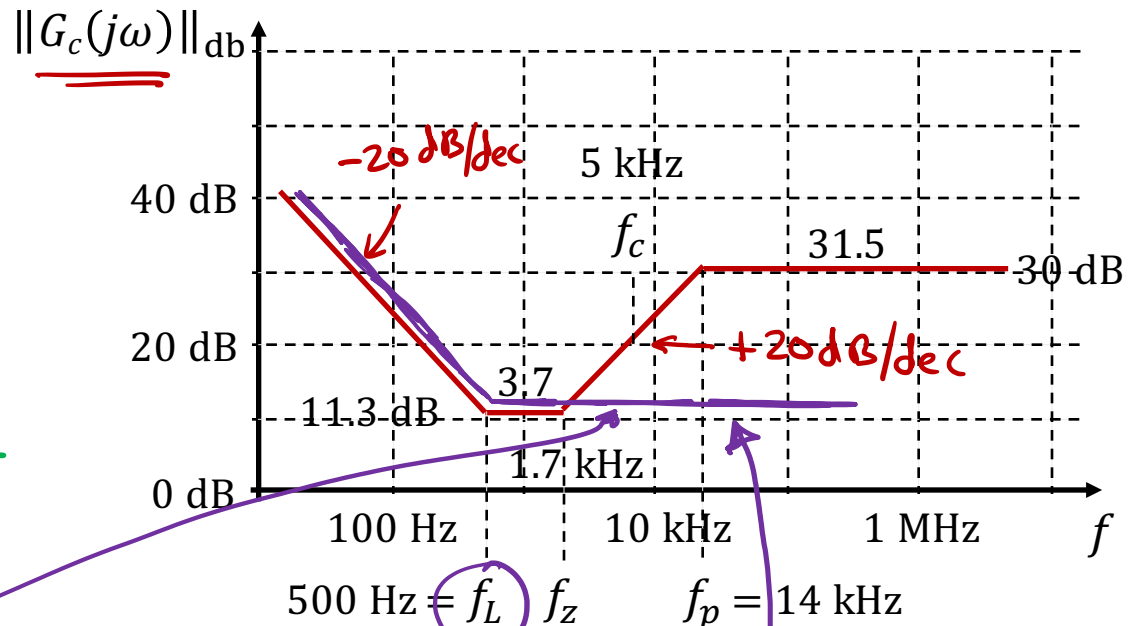
$$R_2 = \frac{1}{\omega C_2} \Rightarrow \omega = \frac{1}{R_2 C_2} \Rightarrow f = \frac{1}{2\pi R_2 C_2} = f_L$$




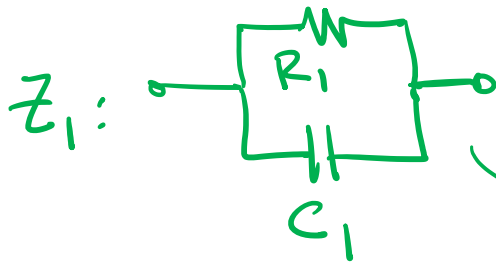
# Implementing $Z_1$ and $Z_2$ (Cont.)





$$G_c(s) = \frac{Z_2}{Z_1} = Z_2 \cdot \frac{1}{Z_1}$$




$$f = \frac{1}{2\pi R_1 C_1} = f_z$$

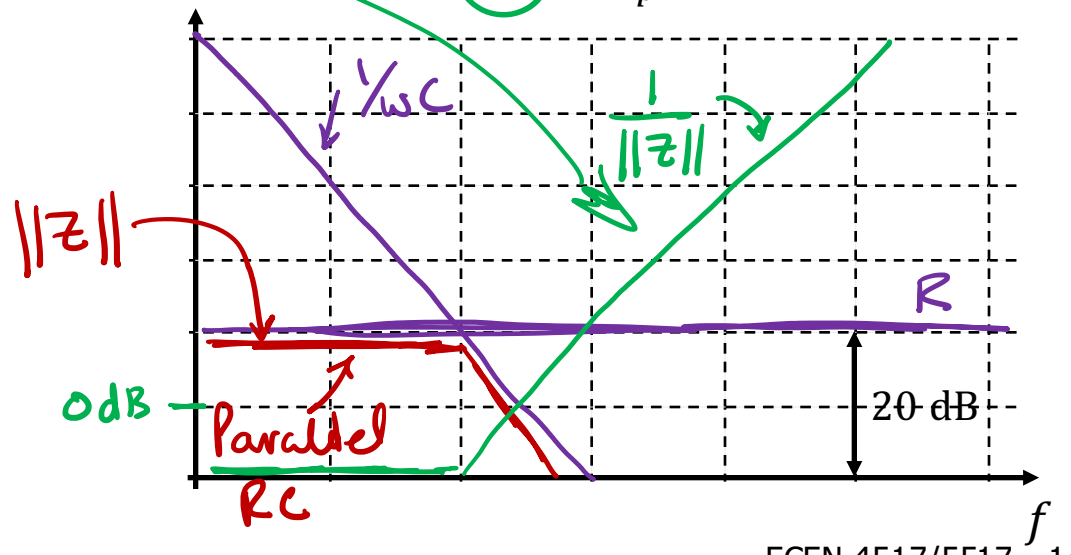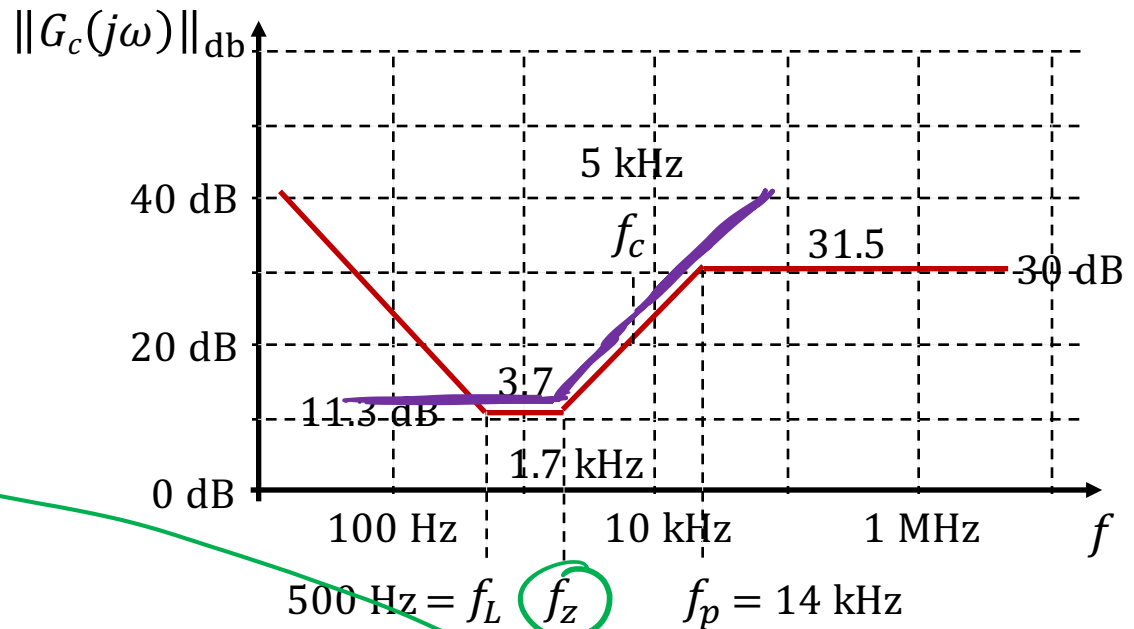

# $Z_2/Z_1$ Bode Plot

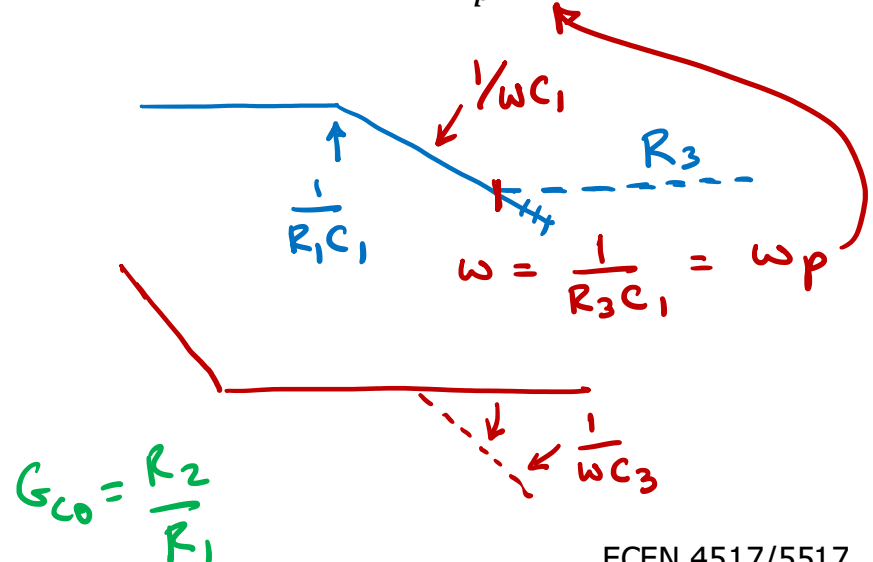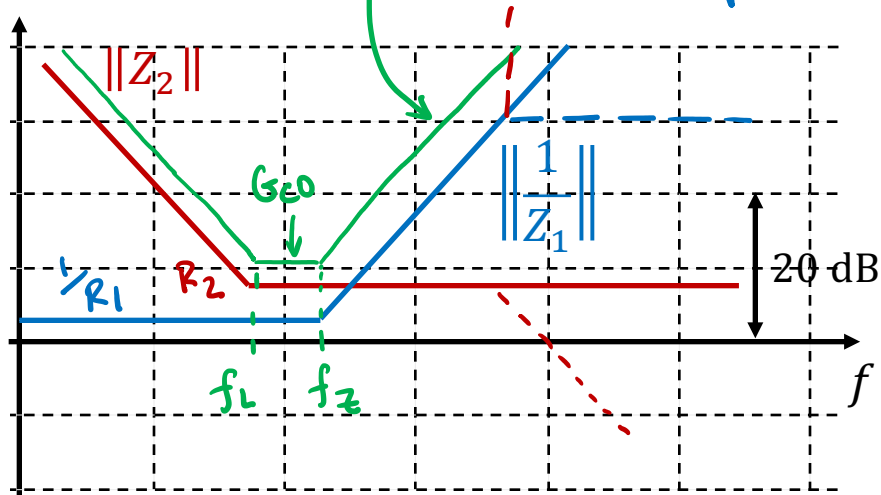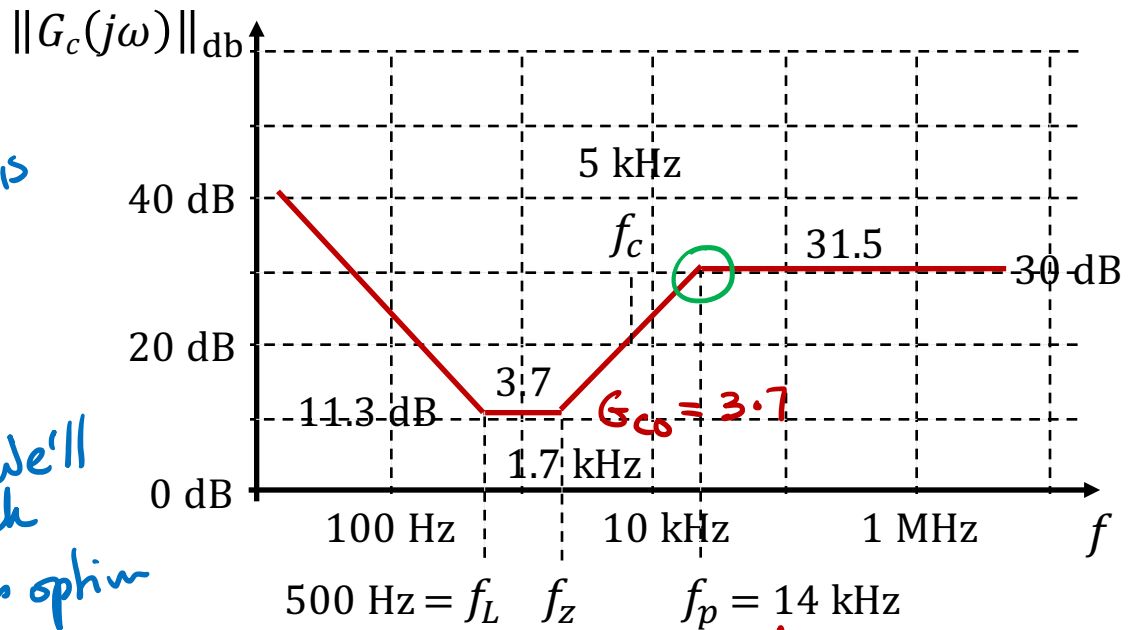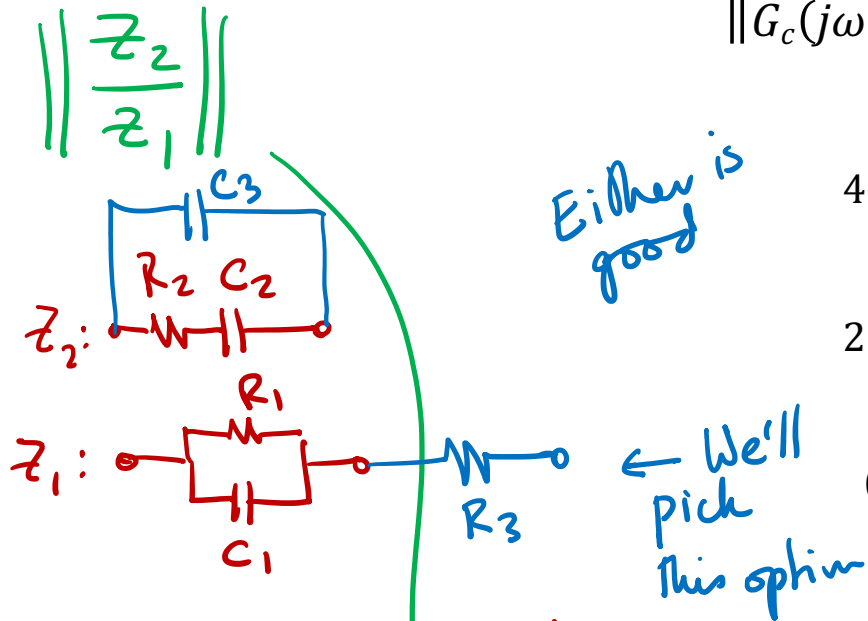

# OpAmp Based Compensator

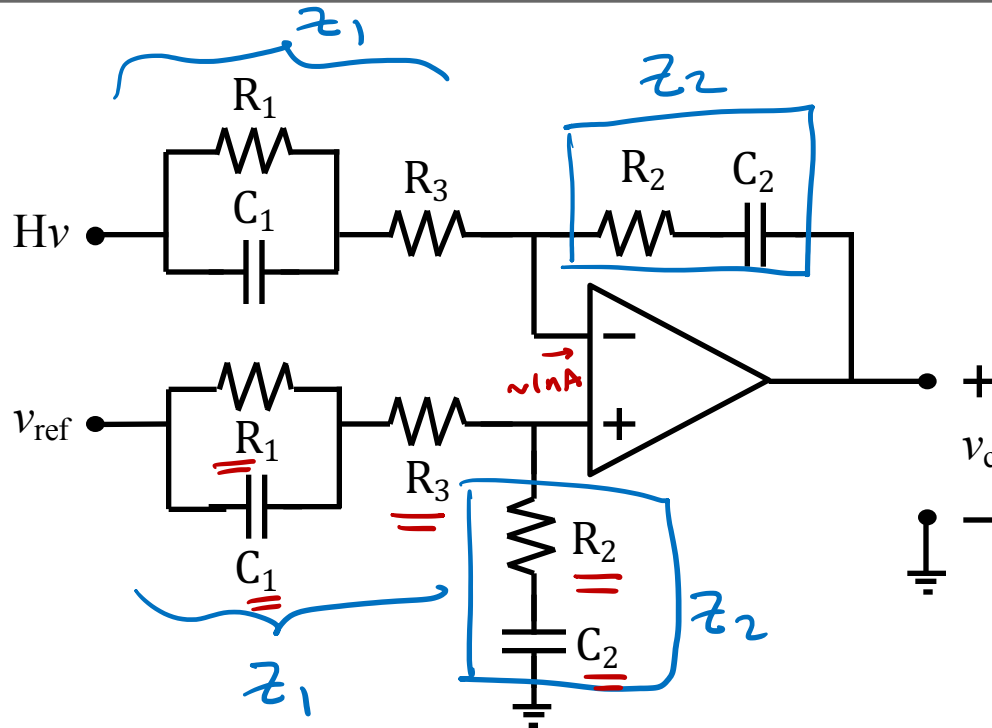

## Design Equations

$$\underline{G_{c0}} = \frac{R_2}{R_1} \quad \checkmark$$

$$\underline{f_L} = \frac{1}{2\pi R_2 C_2} \quad \checkmark$$


$$\underline{f_z} = \frac{1}{2\pi R_1 C_1} \quad \checkmark$$

$$\underline{f_p} = \frac{1}{2\pi R_3 C_1} \quad \checkmark$$


$$\underline{R_2 = 100 \text{ k}\Omega}$$




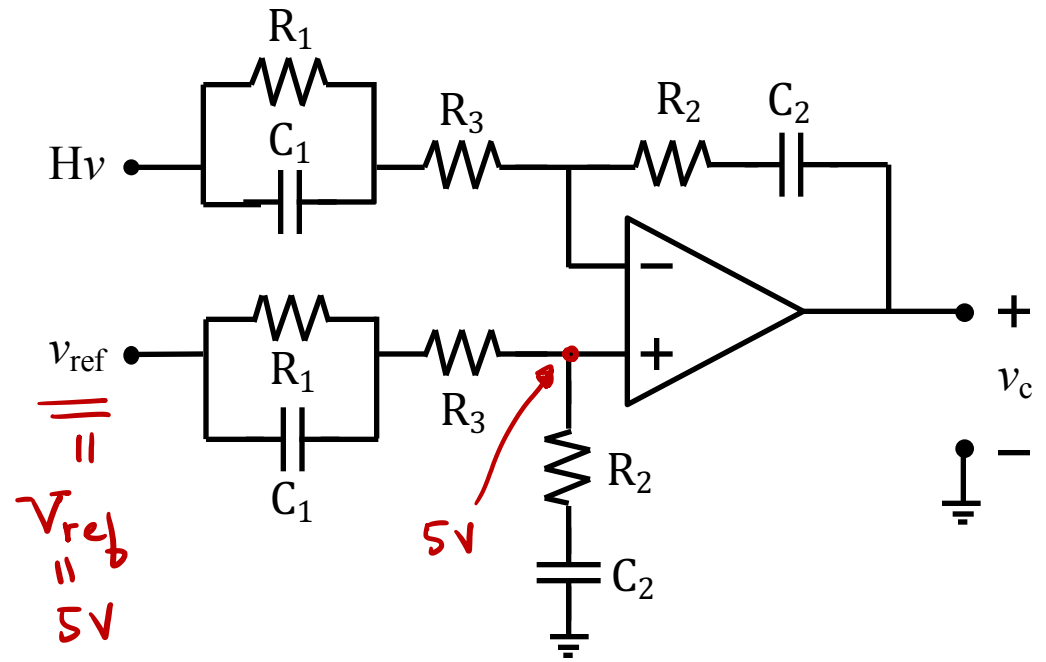
# Possible Simplification for Fixed Reference Voltage



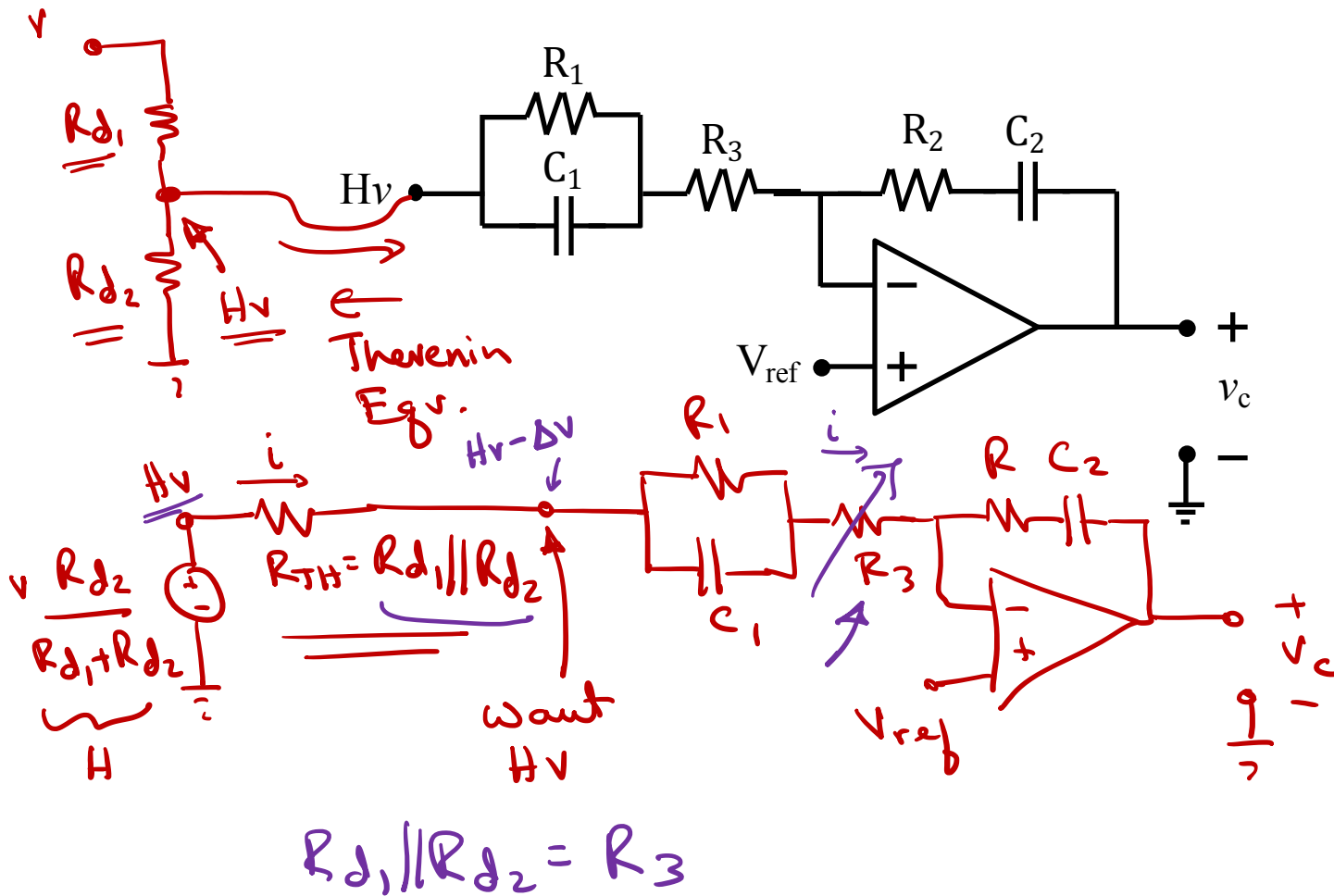
# Incorporating the Divider and Loading Effect





# Final Design

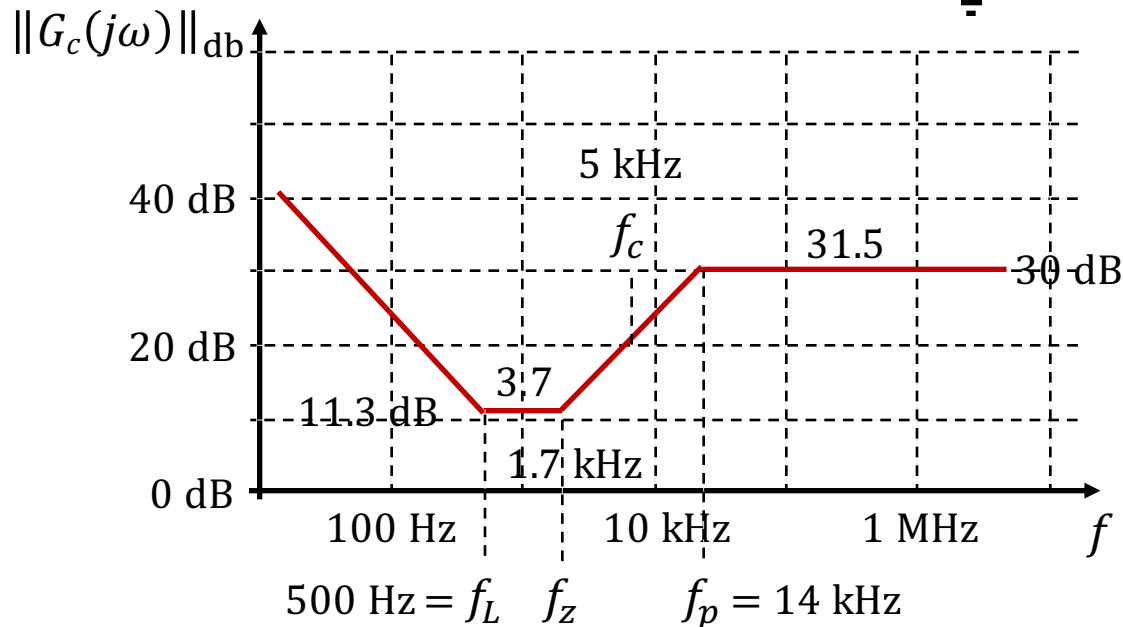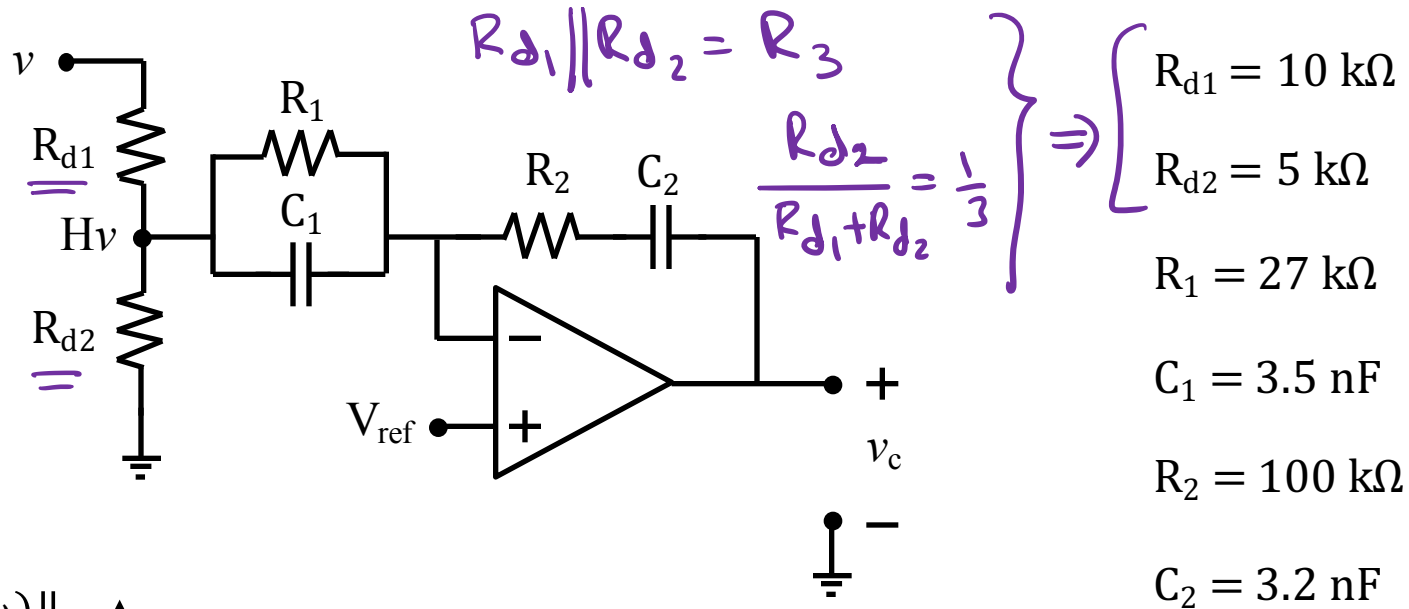

# Performance with Real OpAmp

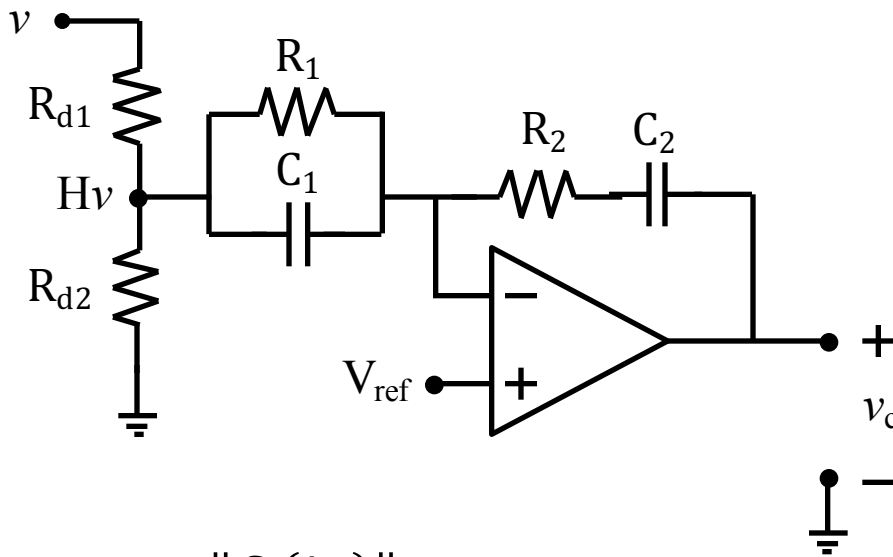


## Real OpAmp Gain

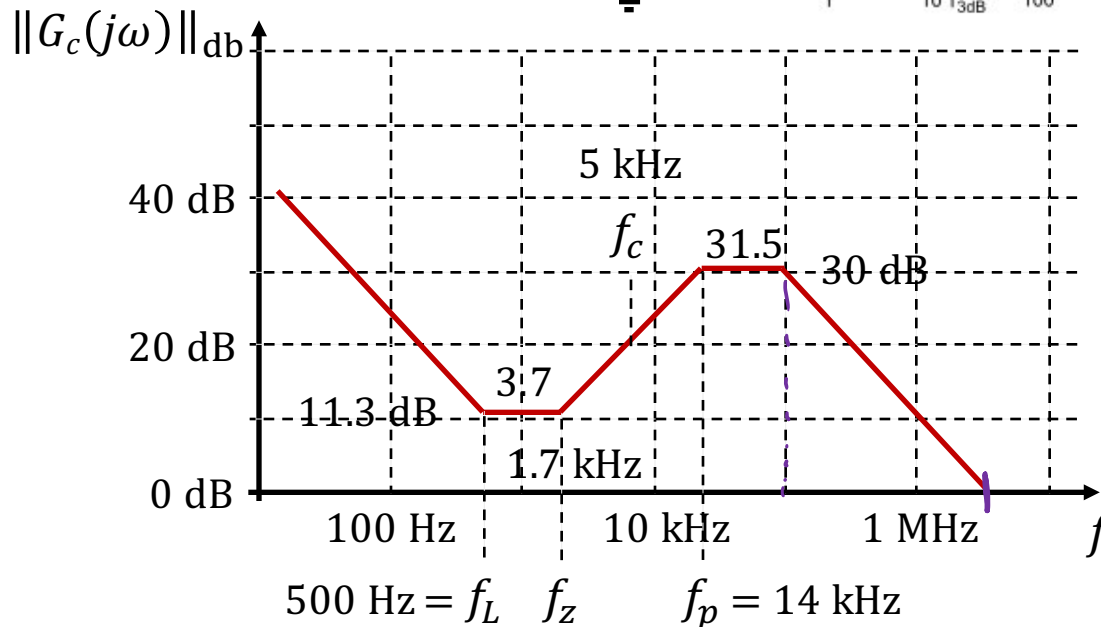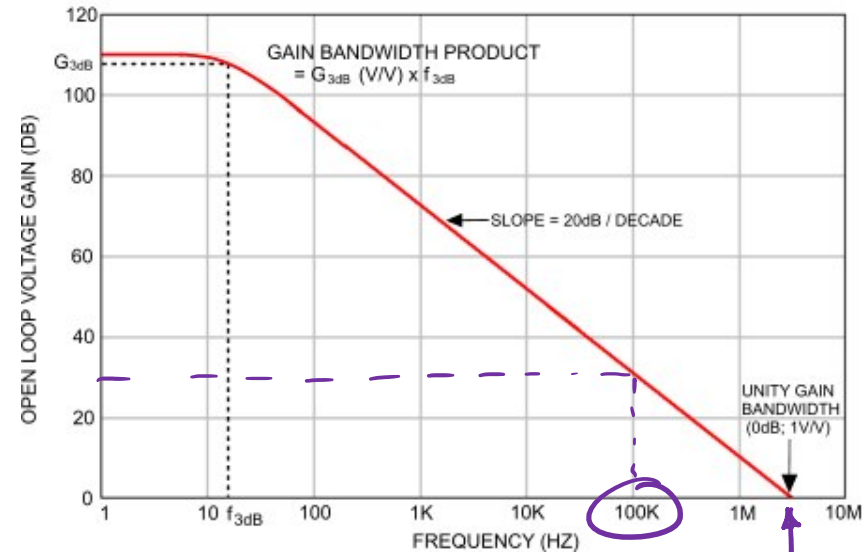


3 MHz  
Gain-Bandwidth

# Experiment 5 – Off-Grid Inverter

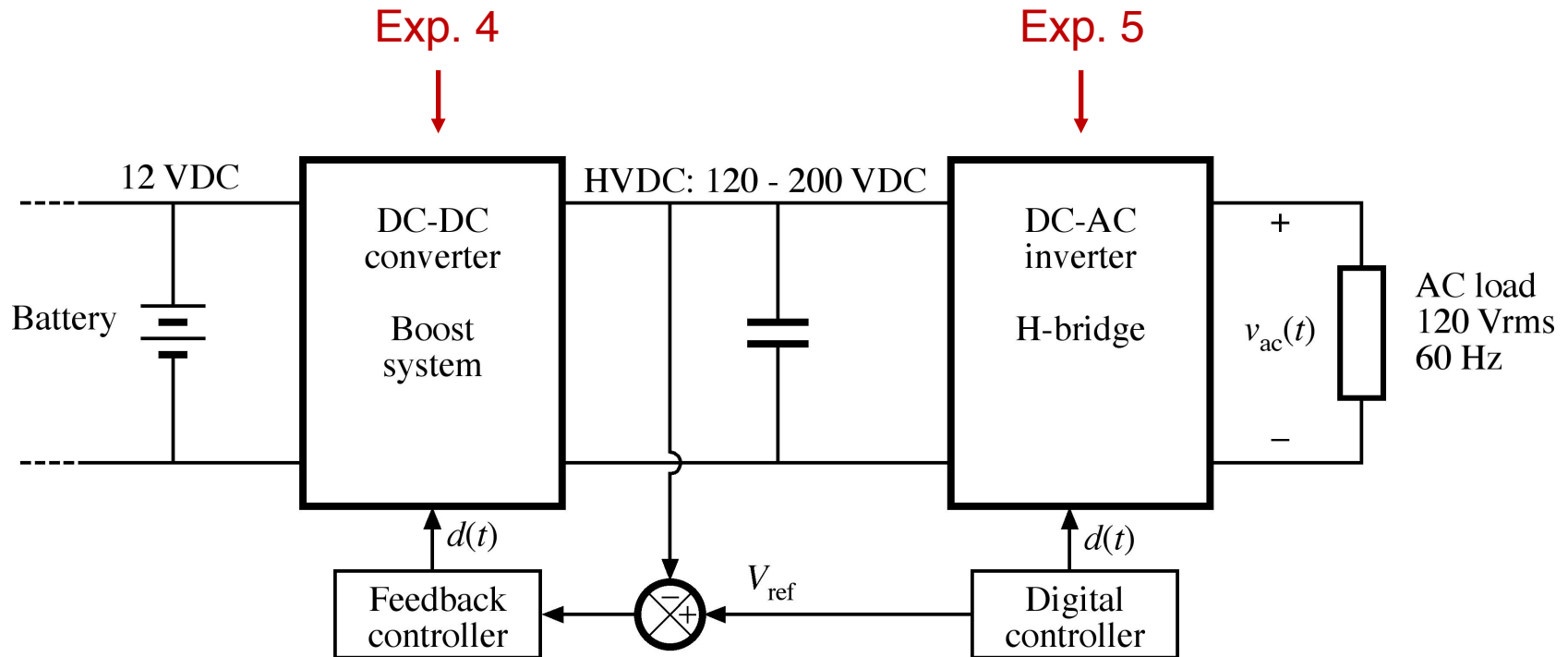

- **Required:** Demonstrate modified sine-wave inverter
- **Extra Credit:** Demonstrate PWM inverter

# Off-Grid H-Bridge Inverter

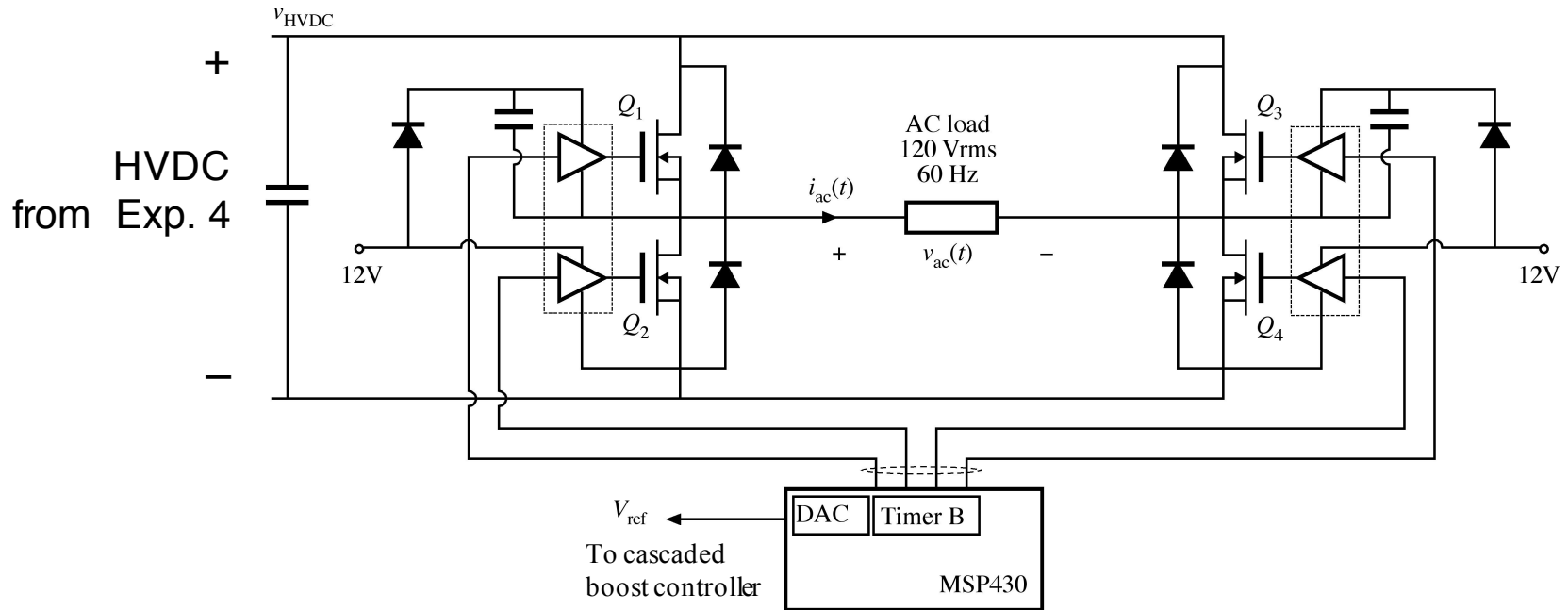


- Need MOSFETs and half-bridge gate drivers
- Filtering of ac output not explicitly shown
- Grid-tied: control  $i_{ac}(t)$
- Off-grid: control  $v_{ac}(t)$
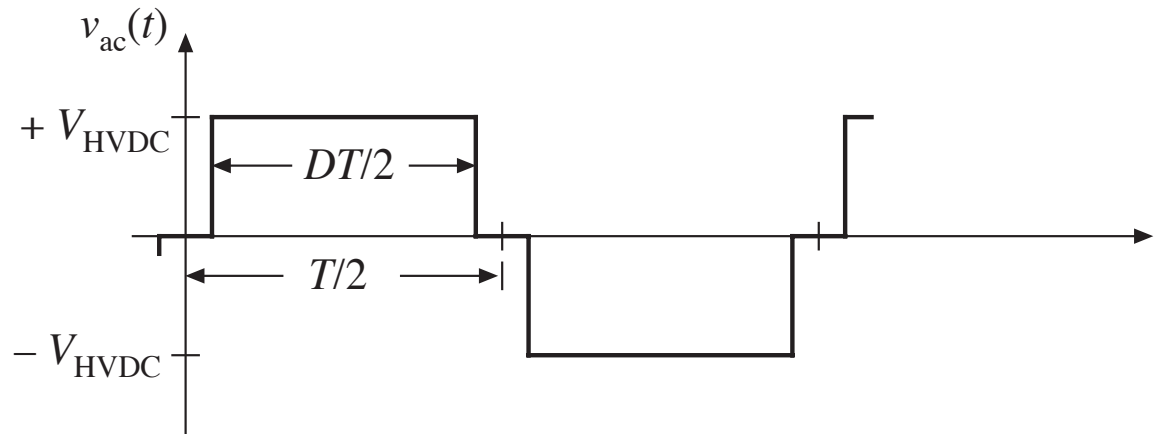
# “Modified Sine Wave” Inverter

$v_{ac}(t)$  has a rectangular waveform

Inverter transistors switch at 60 Hz,  
 $T = 16.66$  msec




RMS value of  $v_{ac}(t)$  is:

$$V_{ac,RMS} = \sqrt{\frac{1}{T} \int_0^T v_{ac}^2(t) dt} = \sqrt{D} V_{HVDC}$$

- Choose  $V_{HVDC}$  larger than desired  $V_{ac,RMS}$
- Can regulate value of  $V_{ac,RMS}$  by variation of  $D$
- Waveform is highly nonsinusoidal, with significant harmonics
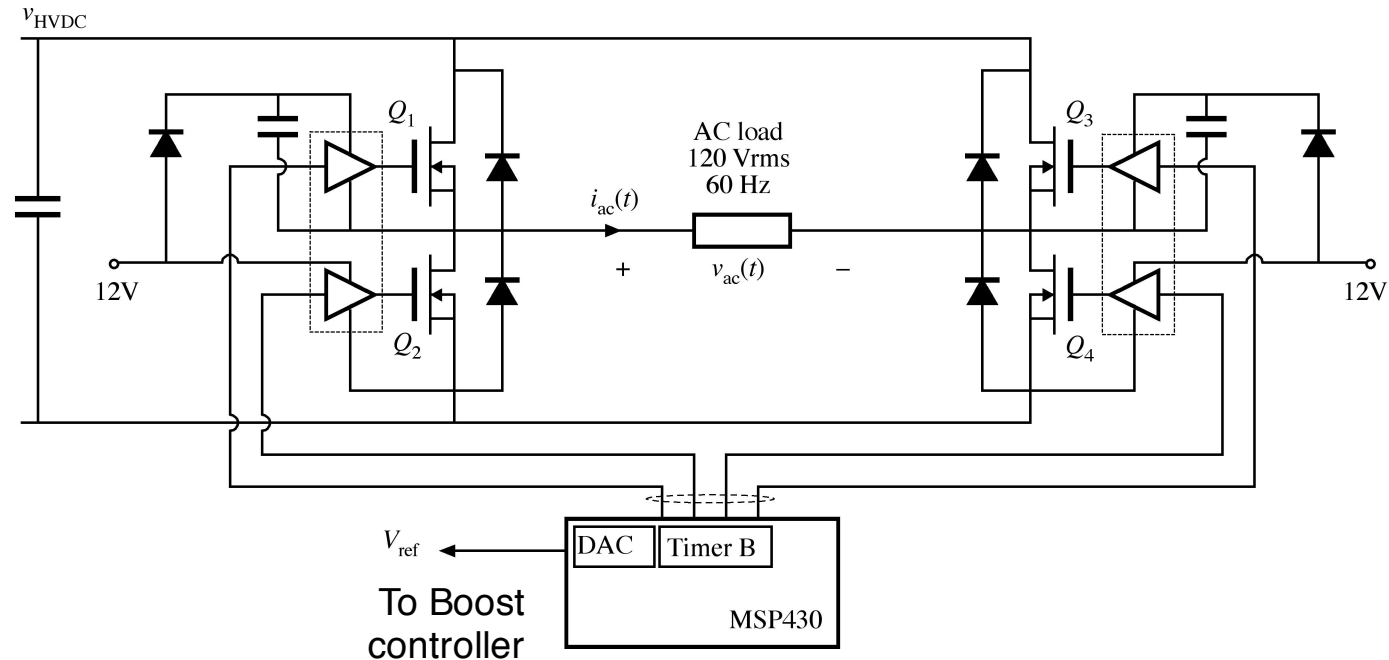
# Inverter Control


- Use MSP430 to control the MOSFET gate drivers
  - Can use Timer A (or logic outputs) to generate drive signals



- Your goal: adjust  $V_{ref}$  and inverter duty cycle to obtain  $V_{ac} = 120 \text{ V rms}$




# Gate Drive Timing

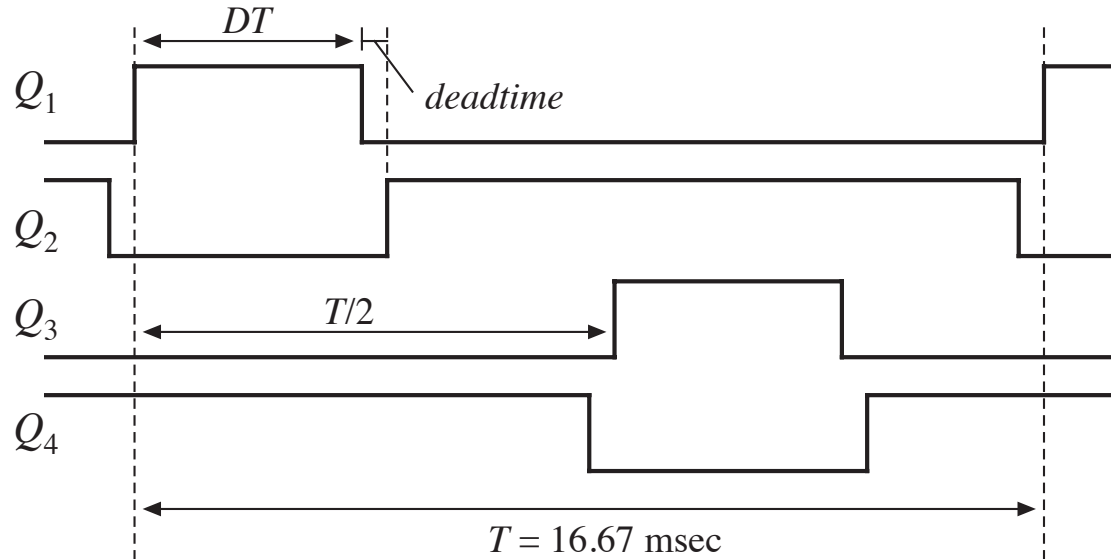

- For modified sine wave inverter: switch once per ac half cycle
- Adjust duty cycle to control rms voltage
- Require deadtime  $>$  (switching/delay times of MOSFETs plus gate drivers); otherwise, simultaneous conduction of  $Q_1$  and  $Q_2$  causes “shoot-through” current that can damage MOSFETs

# Half-Bridge Gate Drivers

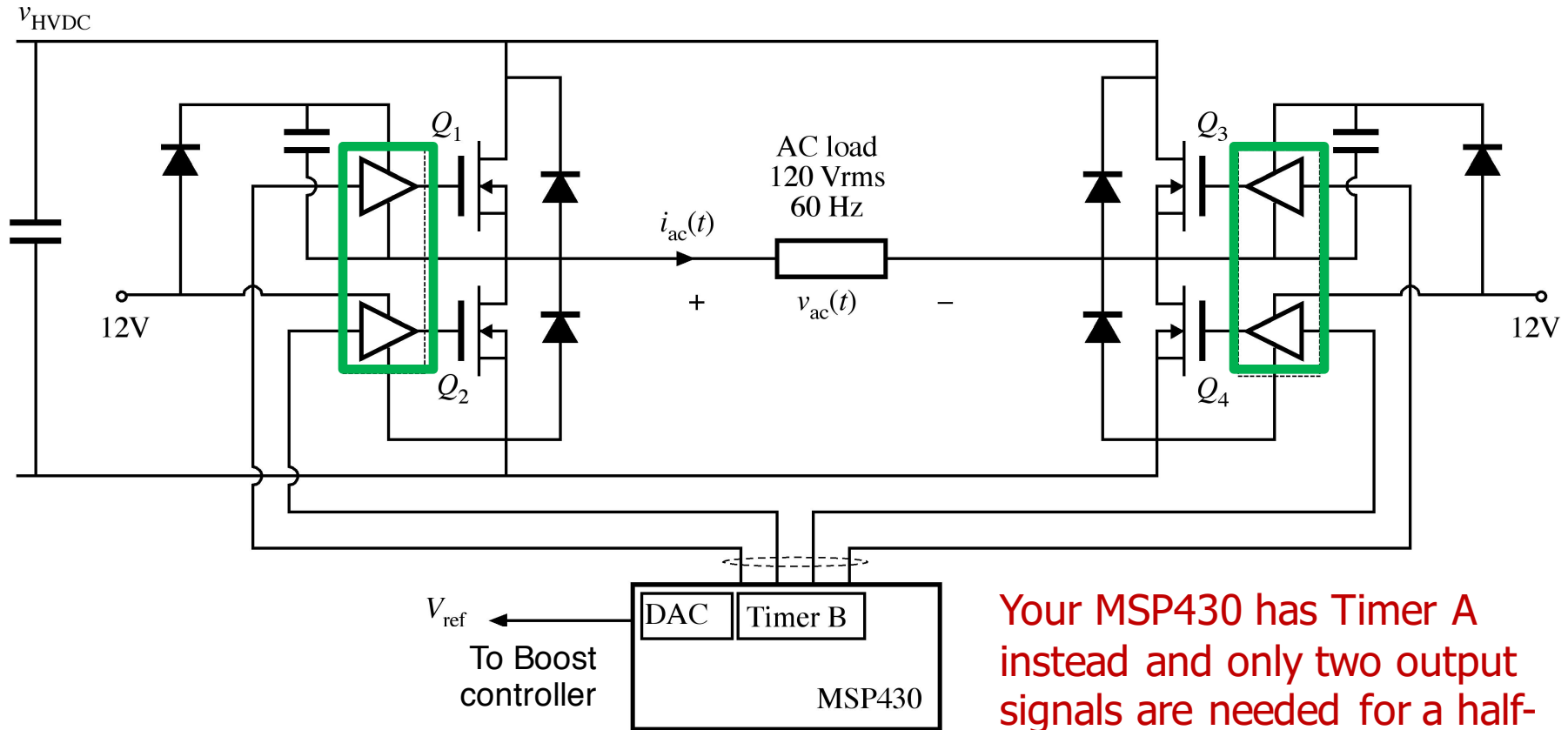

Your MSP430 has Timer A instead and only two output signals are needed for a half-bridge driver

Half-bridge gate driver examples: IR21094 and FAN 73832  
(your parts kit has IR21094)


# Half-Bridge Gate Driver Functionality

Contains two MOSFET drivers:

- Low side driver
- High side driver

High side driver includes

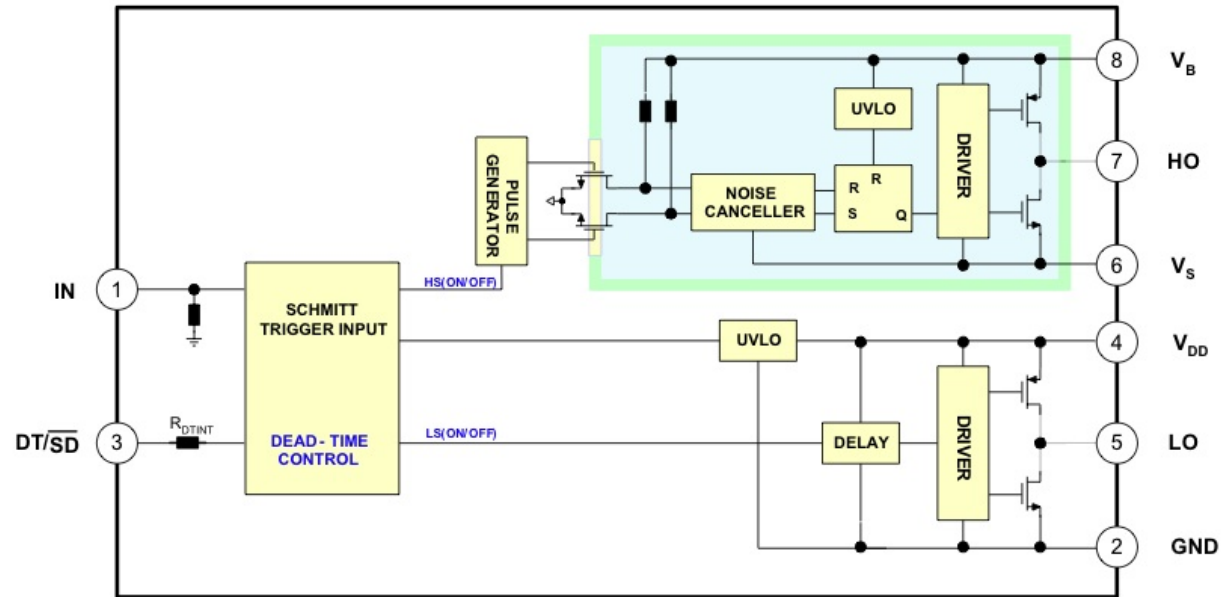- Level-shifting circuitry
- Provisions for bootstrap power supply




FAN73832 Rev:00


Figure 3. Functional Block Diagram of FAN73832

Undervoltage lockout circuitry holds MOSFETs off when driver power supply is below threshold

# Half-Bridge Gate Driver - IR21094

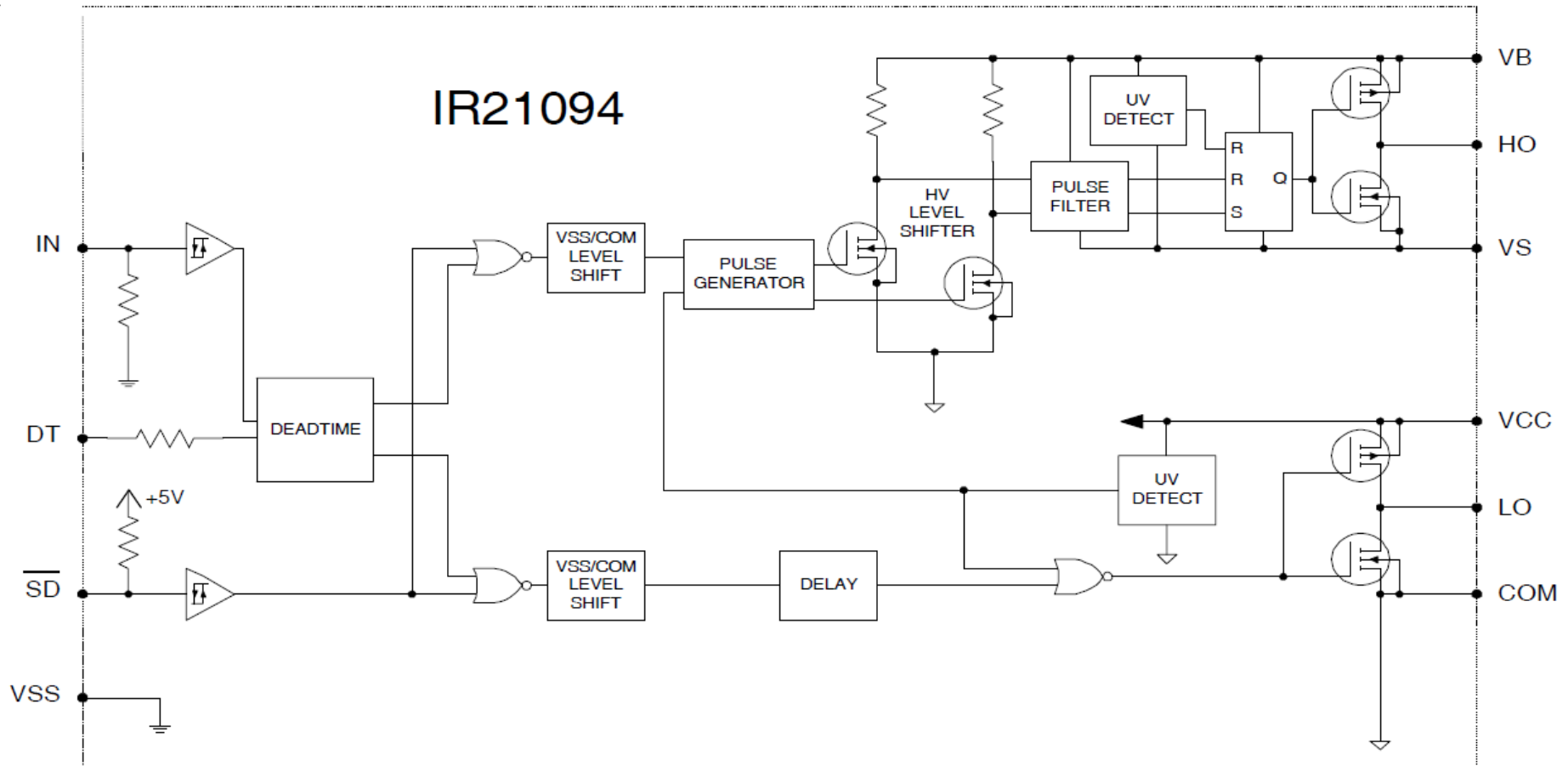
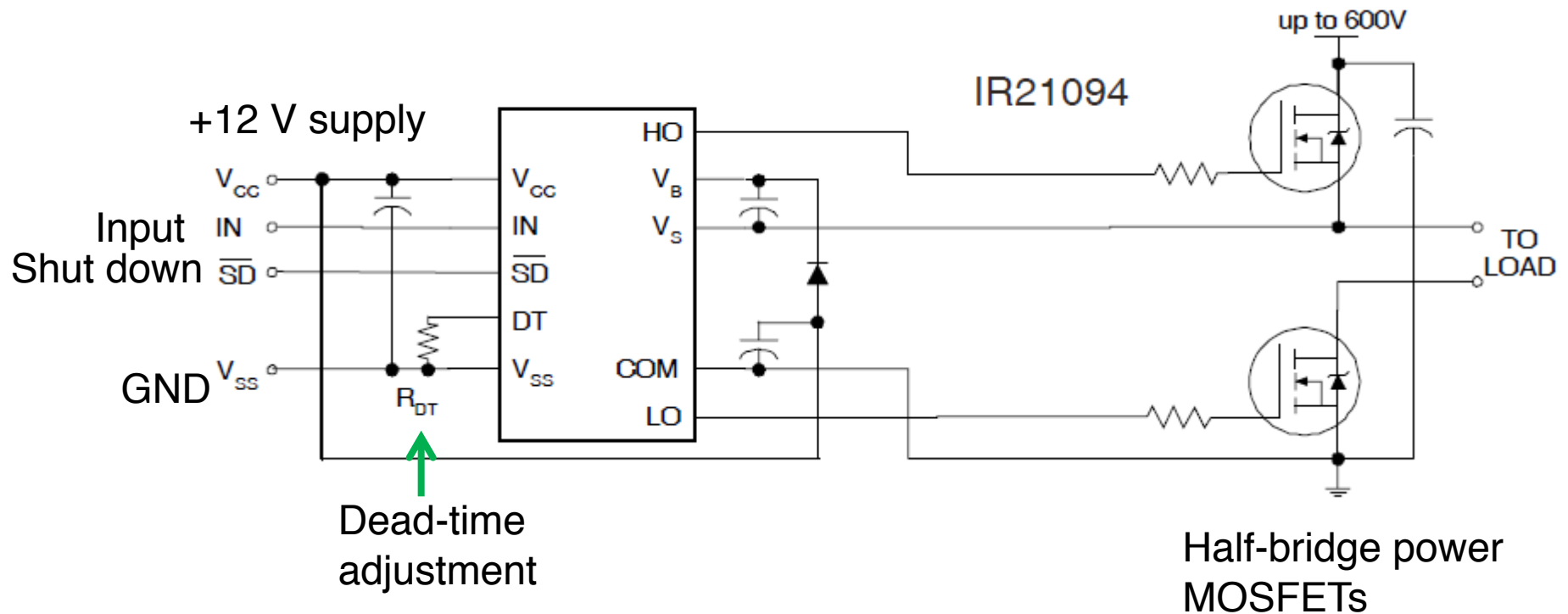
# Half-Bridge Gate Driver Circuit Example



# Half-Bridge Gate Driver Circuit Example

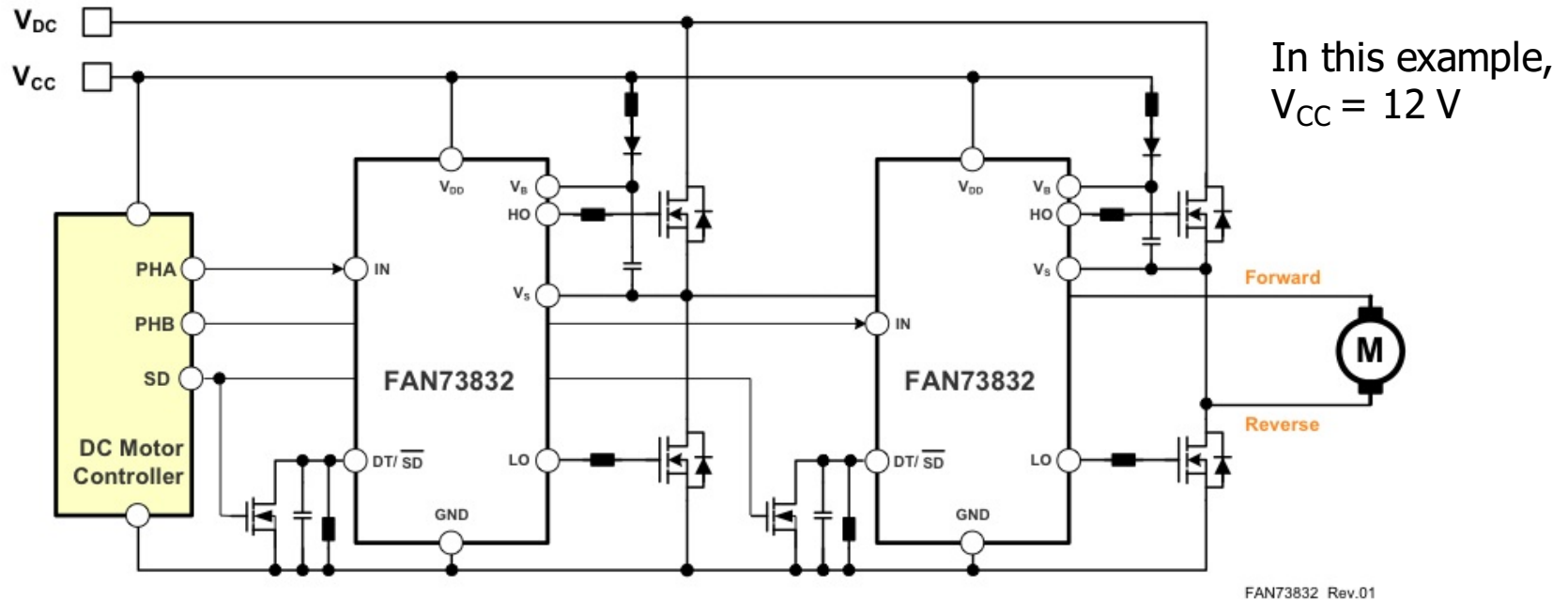


Figure 2. Application Circuit for Full-Bridge DC Motor Driver

- High side circuitry includes external diode and capacitor for bootstrap power supply
- To charge bootstrap capacitor, low side MOSFET must conduct