



ECEN 4517/5517 Power Electronics and PV Lab

Course Home Content Research Assessments Communication Edit Course Logout

Edit Rubric - Exp 4 final report: ECEN5517 ▼

Properties	Levels a	and C	riteria						
+ Add Crit	terion	ф	Add Level	Add C	Criteria Group	ĵļ	Reord	er Criteria	
Criter	ia	~	Full cı	redit 🔻	Partial cre	dit	~	No credit	▼
	Document PWM controller circuit diagram		3 points		2 points			0 points	
Measured waveforms of all 16 pins of UC3525		₩	8 points		4 points			0 points	
Document power stage schematic		~	6 points		3 points			0 points	
Document indicates the design and modern and		~	3 р	ooints	2 poin	ts		0 points	
Open loop measured waveforms and meter readings: vds, Vg, Ig, V, I, efficiency, at 200V and 85 W		, I,	10 points		5 points			0 points	
Updated loss measurement calculations, s for improvement	s and suggestion	ns	13 ן	points	7 poin	ts		0 points	
Measured da magnitude an		~	5 p	ooints	2 poin	ts		0 points	
Fit magnitude asymptotes to measured Gvd that follow Bode plot rules		• OW	3 points		2 points			0 points	
Fit phase asymptotes to measured Gvd that follow Bode plot rules		~	3 points		2 points			0 points	
Analytical exp for measured		~	2 points		1 point			0 points	

with numerical values of parameters			
Simulation of Gvd: schematic and output plots	5 points	2 points	0 points
Fit magnitude asymptotes to simulated Gvd that follow Bode plot rules	3 points	2 points	0 points
Fit phase asymptotes to simulated Gvd that follow Bode plot rules	3 points	2 points	0 points
Analytical expression for simulated Gvd(s) with numerical values of parameters	2 points	1 point	0 points
Compare measured and simulated Gvd(s)	2 points	1 point	0 points
Analytical derivation of Gvd(s); compare with measured and simulated	5 points	3 points	0 points
Optional extra credit: add damping network. Document calculations, element values, and implementation.	10 points	5 points	0 points
Feedback: proposed compensated T(s) mag and phase asymptotes	5 points	2 points	0 points
Feedback: proposed op amp compensator Gc(s) mag and phase asymptotes, and op amp circuit	5 points	2 points	0 points
Expected crossover frequency and phase margin, with supporting calculations	3 points	2 points	0 points
Load test: Vg, V, Ig, I, D, efficiency at the two extreme points of load range. Calculate regulation.	3 points	2 points	0 points
Line test: Vg, V, Ig, I, D, efficiency at the two extreme points of Vg range. Calculate regulation.	3 points	2 points	0 points
Soft start: document circuit and value used.	5 points	2 points	0 points

Uscilloscope output voltage waveform of turn-on transient.					
Overall Score	Level 3 74 or more	Level 2 49 or more	~	Level 1 0 or more	~
Close					