

# **ECEN 4517/5517**

## **Power Electronics and Photovoltaic Power Systems Laboratory**

### **Lecture 10**


#### **True Sine Wave Inverter And Other Inverter Modulation Techniques**

# Announcements

---


- Exp 4 Lab Report due by 11:59 pm (MT) on Friday April 7, 2017
- This week's lab: Experiment 5
  - Have 2 weeks to work on Experiment 5
  - Exp 5 Lab Report due by 11:59 pm (MT) on Friday April 21, 2017
- After that: Assemble Complete System
- Quiz 2 on Monday April 24, 2017
  - In-class 40-minute quiz administered during lecture time
  - Closed book/notes, calculator allowed
  - Will cover Experiment 4 and 5 material
- Expo (Final Demo) on Thursday May 4, 2017

# Experiments

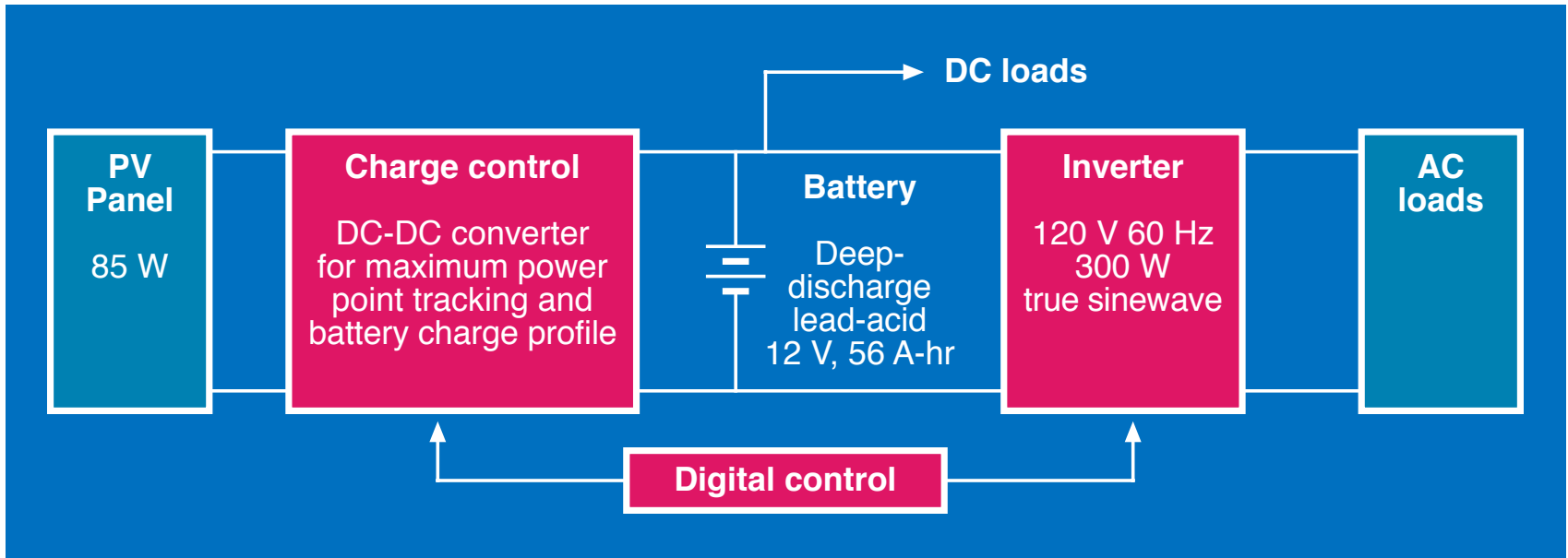


- [Exp 1](#) – PV panel and battery characteristics and direct energy transfer
- [Exp 2](#) – TI MSP430 microcontroller introduction
- [Exp 3-1, 3-2](#) – Buck dc-dc converter for PV MPPT and battery charge control
- [Exp 4](#) – Step-up 12V-200V dc-dc converter
- [Exp 5](#) – Single-phase dc-ac converter (inverter)
- [Expo](#) – Complete system demonstration

# Experiment 5 – Off-Grid Inverter

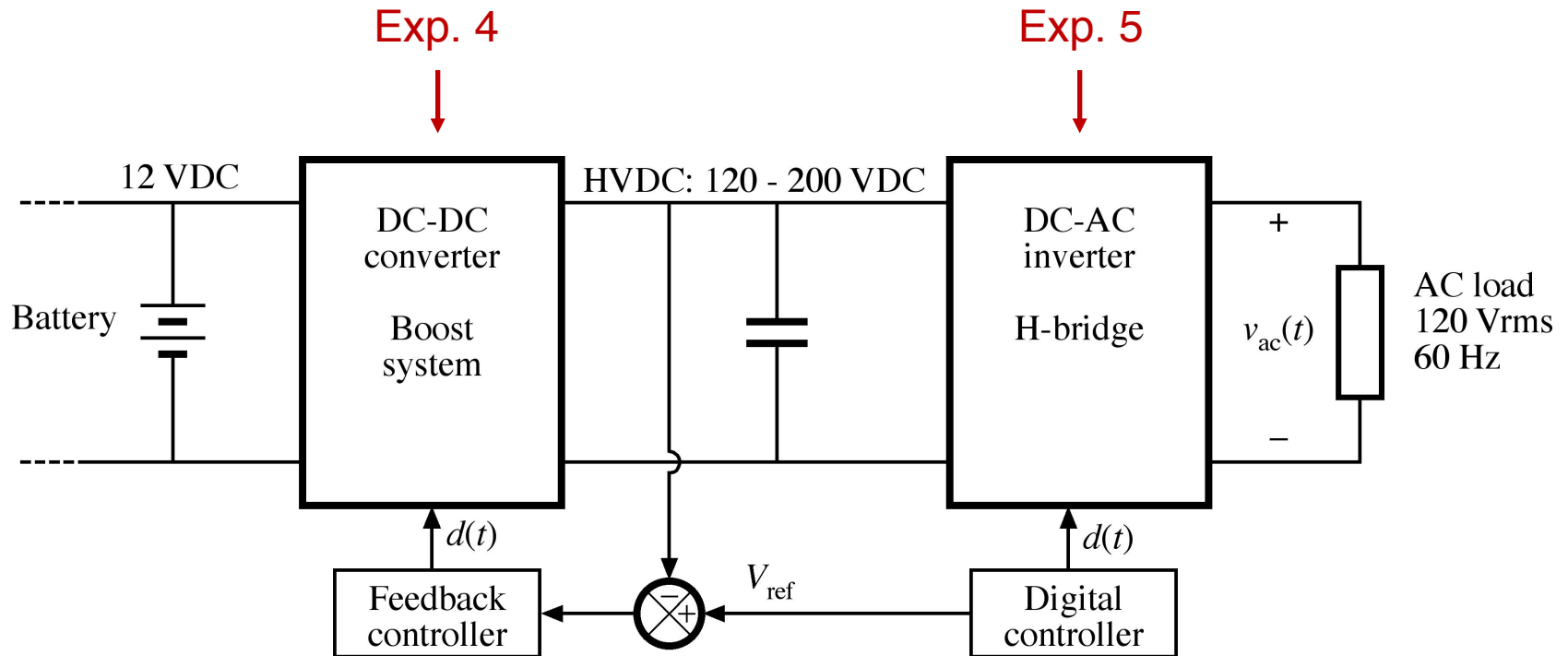

- **Required:** Demonstrate modified sine-wave inverter
- **Extra Credit:** Demonstrate PWM inverter

# Off-Grid H-Bridge Inverter

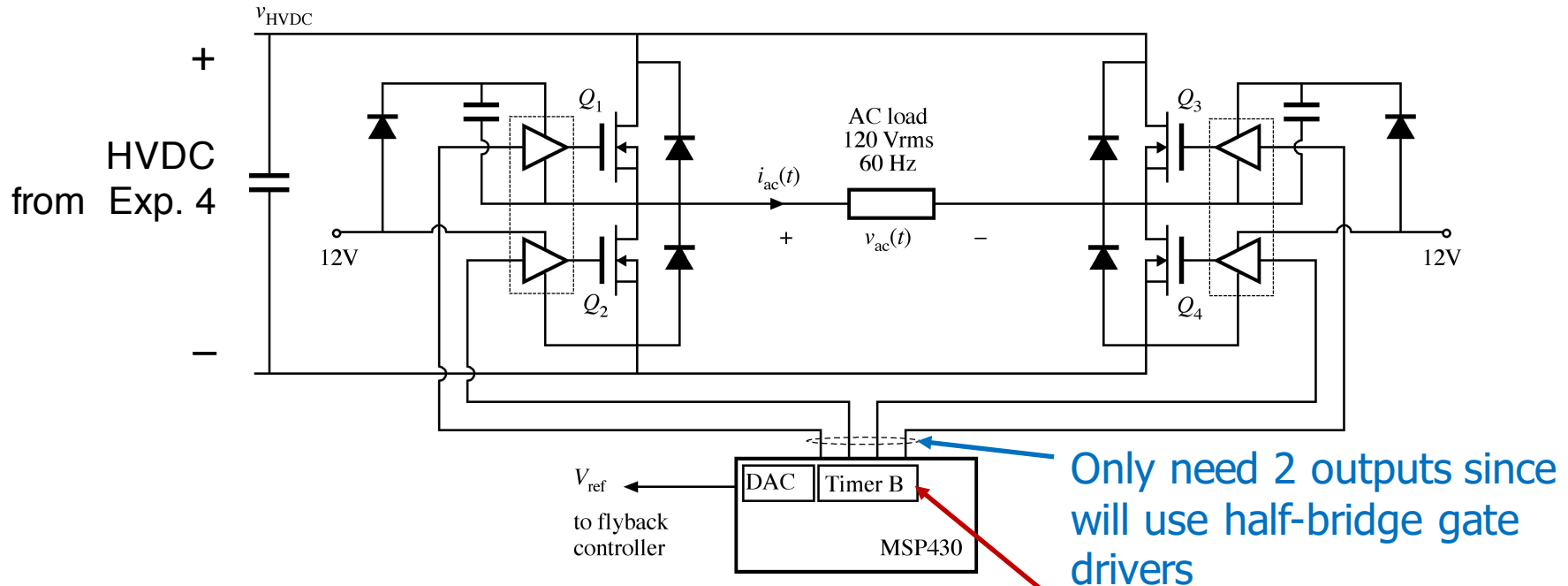


- Need MOSFETs and half-bridge gate drivers
- Filtering of ac output not explicitly shown
- Grid-tied: control  $i_{ac}(t)$
- Off-grid: control  $v_{ac}(t)$

Timer A instead
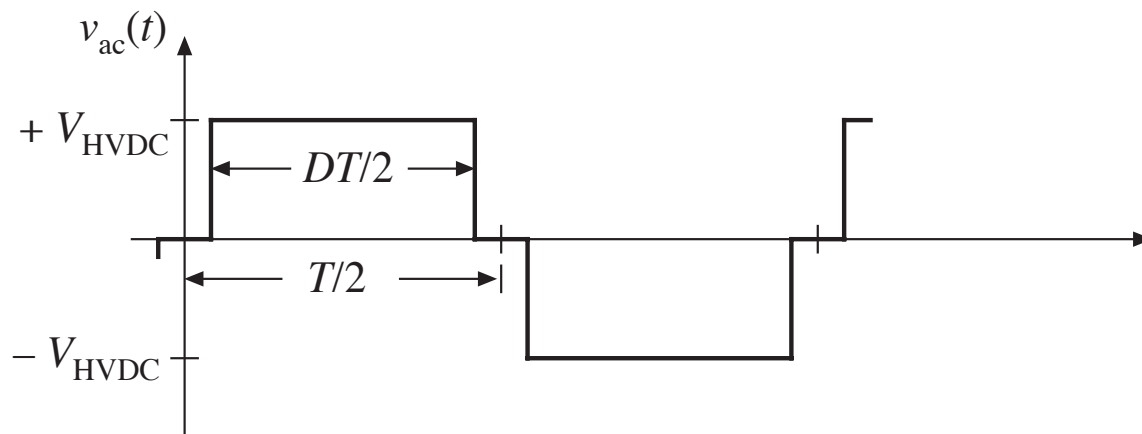
# “Modified Sine Wave” Inverter

$v_{ac}(t)$  has a rectangular waveform

Inverter transistors switch at 60 Hz,  
 $T = 16.66$  msec




RMS value of  $v_{ac}(t)$  is:

$$V_{ac,RMS} = \sqrt{\frac{1}{T} \int_0^T v_{ac}^2(t) dt} = \sqrt{D} V_{HVDC}$$

- Choose  $V_{HVDC}$  larger than desired  $V_{ac,RMS}$
- Can regulate value of  $V_{ac,RMS}$  by variation of  $D$
- Waveform is highly nonsinusoidal, with significant harmonics

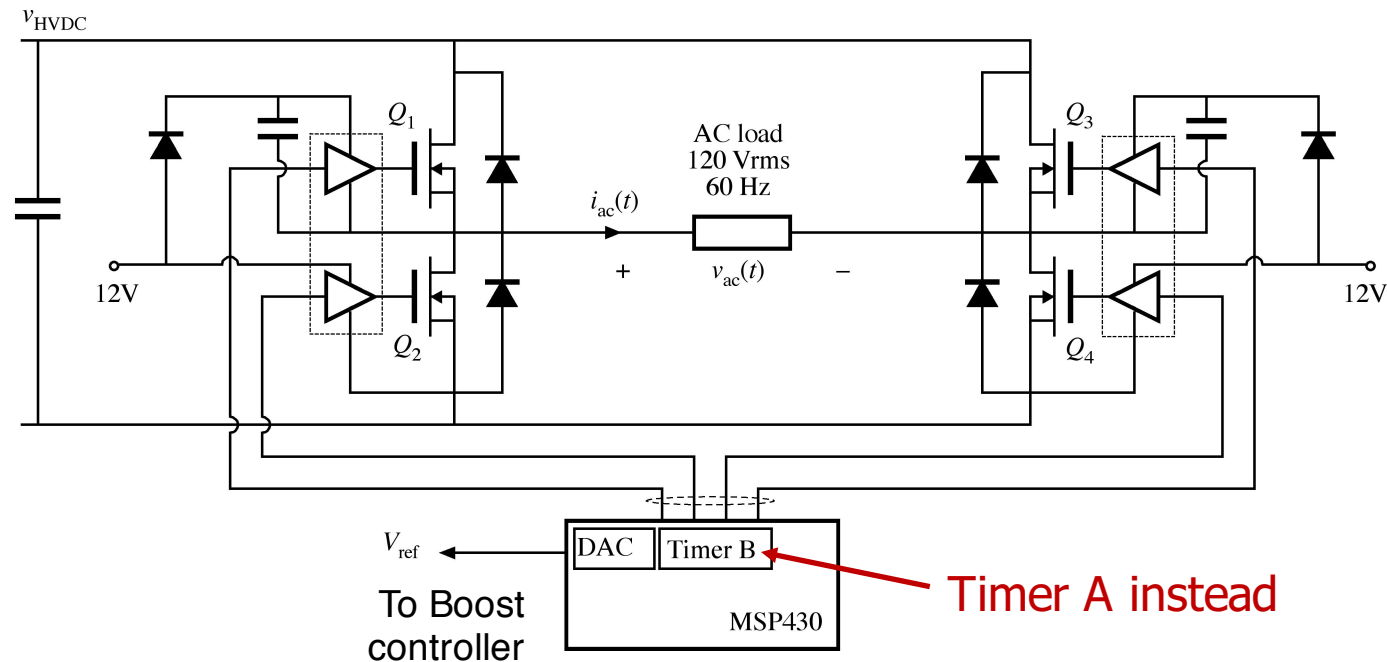
# Inverter Control

- Use MSP430 to control the MOSFET gate drivers
  - Can use Timer A (or logic outputs) to generate drive signals



- Your goal: adjust  $V_{ref}$  and inverter duty cycle to obtain  $V_{ac} = 120 \text{ V rms}$


# Gate Drive Timing

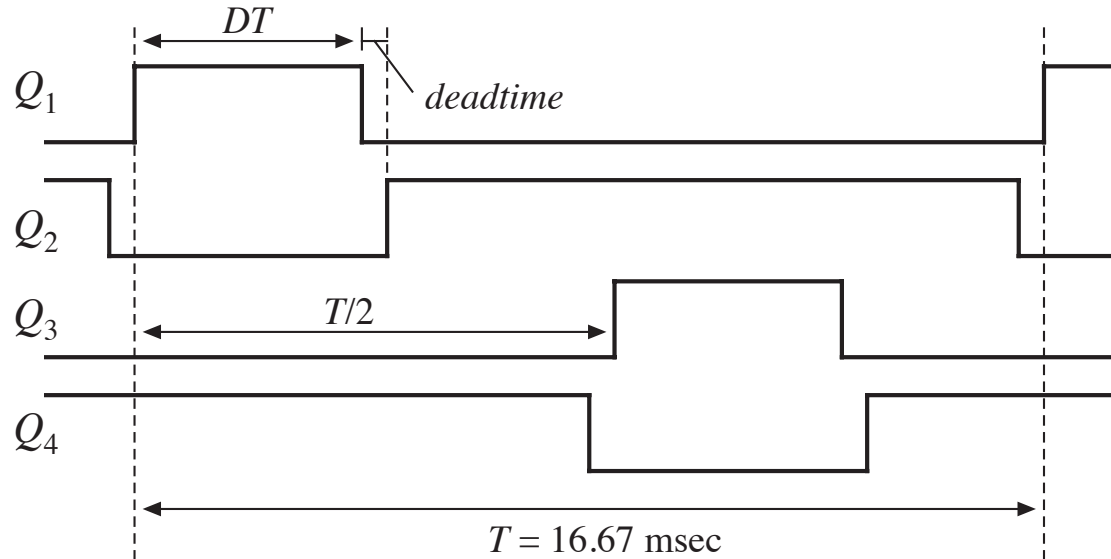

- For modified sine wave inverter: switch once per ac half cycle
- Adjust duty cycle to control rms voltage
- Require deadtime  $>$  (switching/delay times of MOSFETs plus gate drivers); otherwise, simultaneous conduction of  $Q_1$  and  $Q_2$  causes “shoot-through” current that can damage MOSFETs



# Half-Bridge Gate Drivers

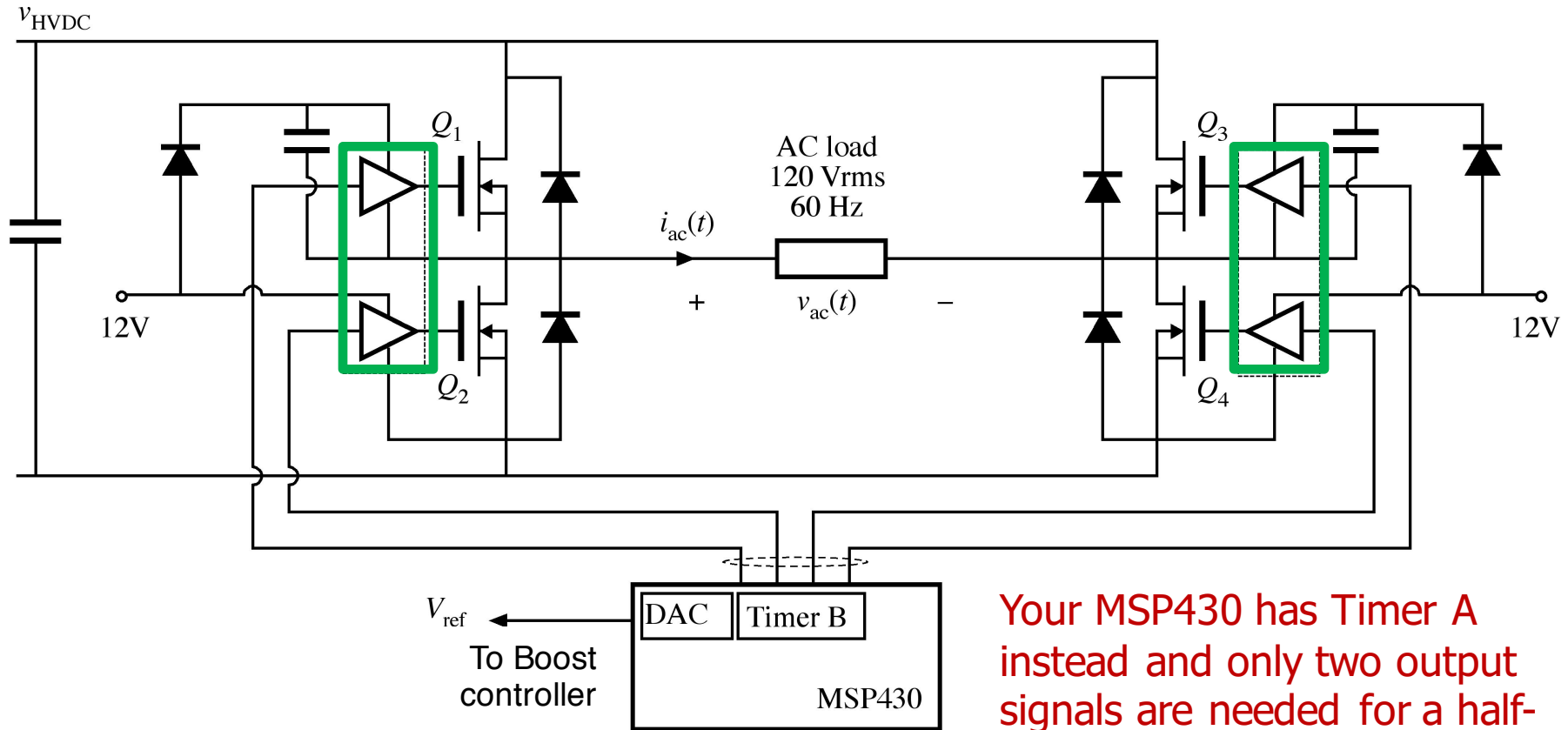

Your MSP430 has Timer A instead and only two output signals are needed for a half-bridge driver

Half-bridge gate driver examples: IR21094 and FAN 73832  
(your parts kit has IR21094)


# Half-Bridge Gate Driver Functionality

Contains two MOSFET drivers:

- Low side driver
- High side driver

High side driver includes

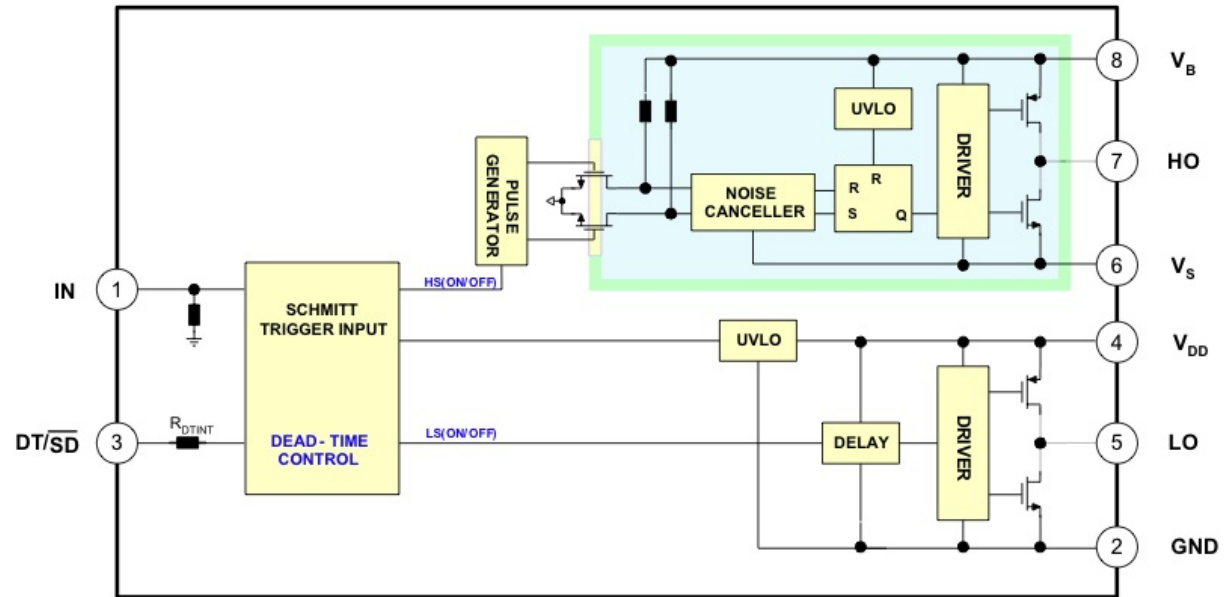- Level-shifting circuitry
- Provisions for bootstrap power supply




FAN73832 Rev:00


Figure 3. Functional Block Diagram of FAN73832

Undervoltage lockout circuitry holds MOSFETs off when driver power supply is below threshold


# Half-Bridge Gate Driver - IR21094

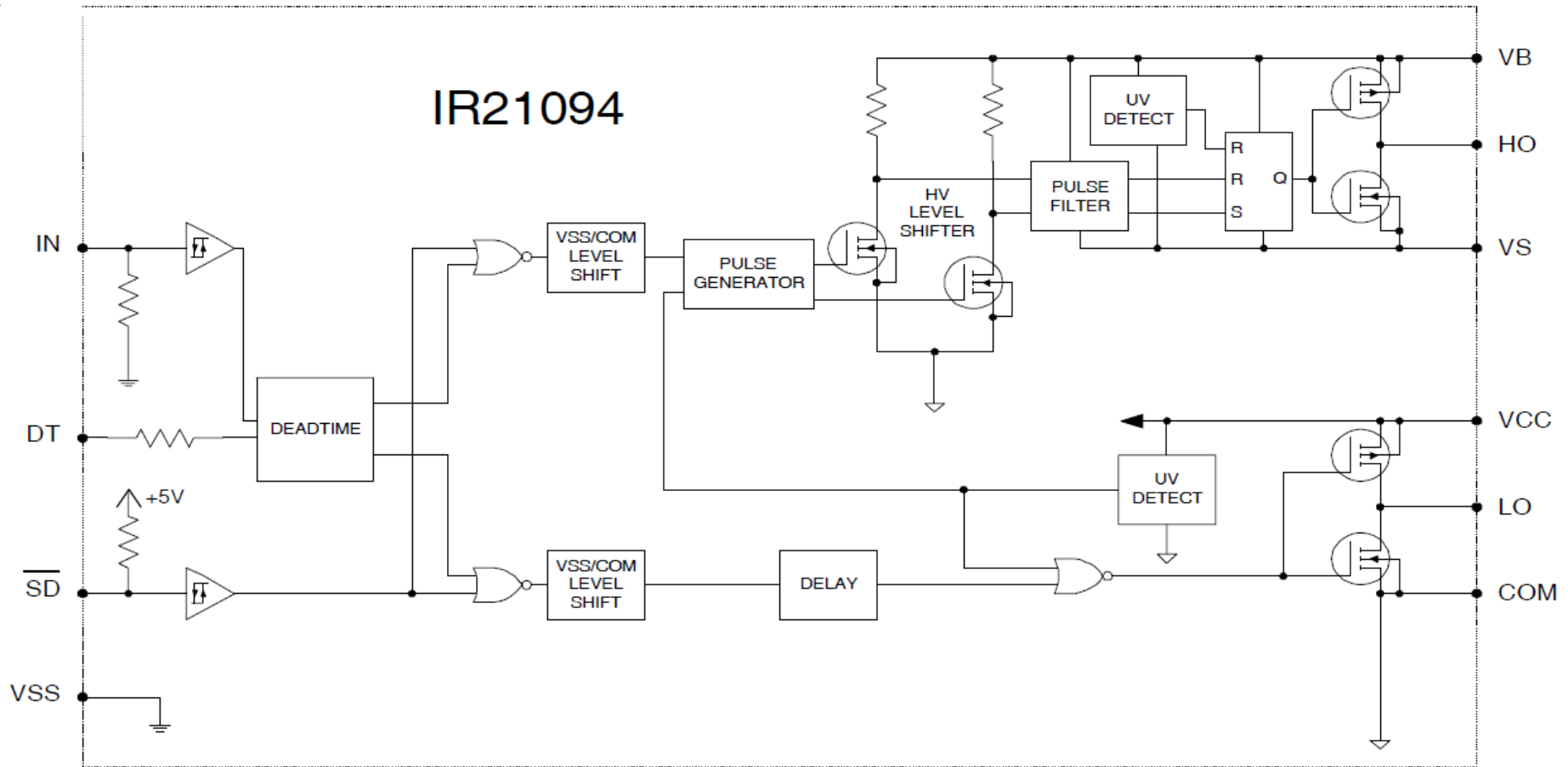
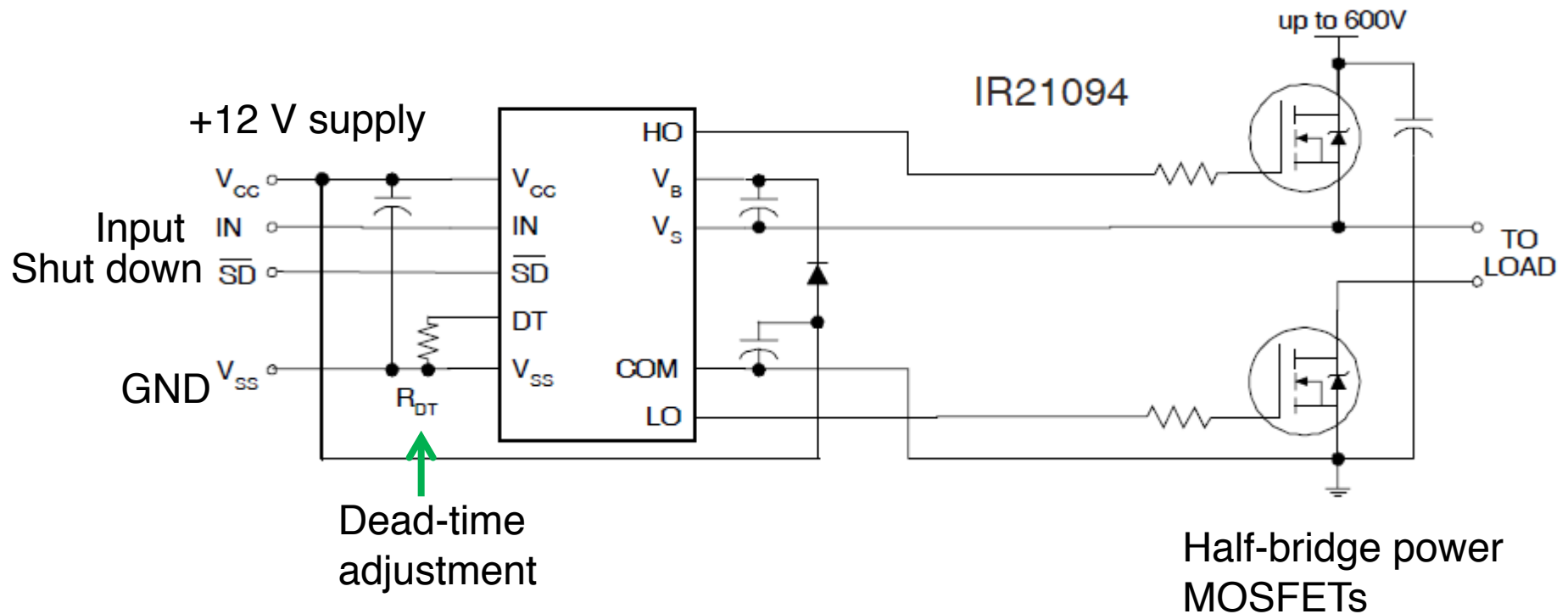
# Half-Bridge Gate Driver Circuit Example



# Half-Bridge Gate Driver Circuit Example

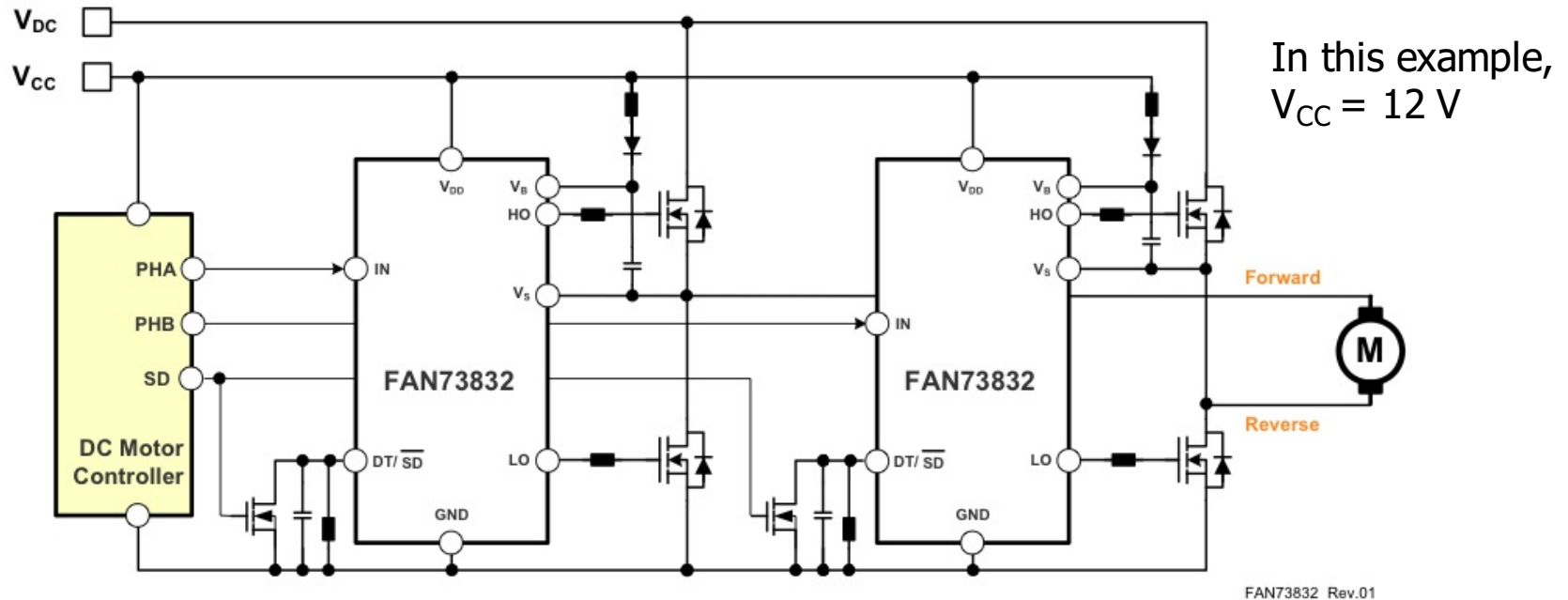


**Figure 2. Application Circuit for Full-Bridge DC Motor Driver**

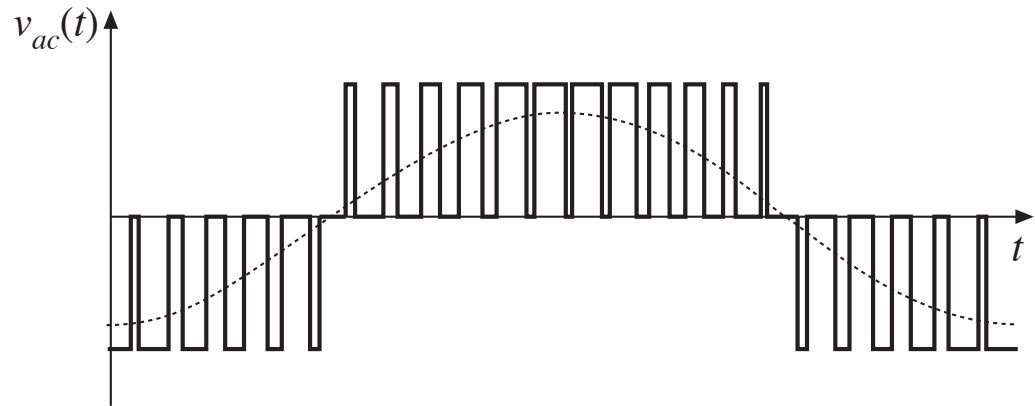- High side circuitry includes external diode and capacitor for bootstrap power supply
- To charge bootstrap capacitor, low side MOSFET must conduct


# PWM Inverter

- Average  $v_{ac}(t)$  has a sinusoidal waveform
- Inverter transistors switch at frequency substantially higher than 60 Hz




- Choose  $V_{HVDC}$  larger than desired  $V_{ac,peak}$
- Can regulate waveshape and value of  $V_{ac,RMS}$  by variation of  $d(t)$  (programming inside microcontroller)
- Can achieve sinusoidal waveform, with negligible harmonics
- Higher switching frequency leads to more switching loss and need to filter high-frequency switching harmonics and common-mode currents
- For the same  $V_{ac,RMS}$ , need larger  $V_{HVDC}$
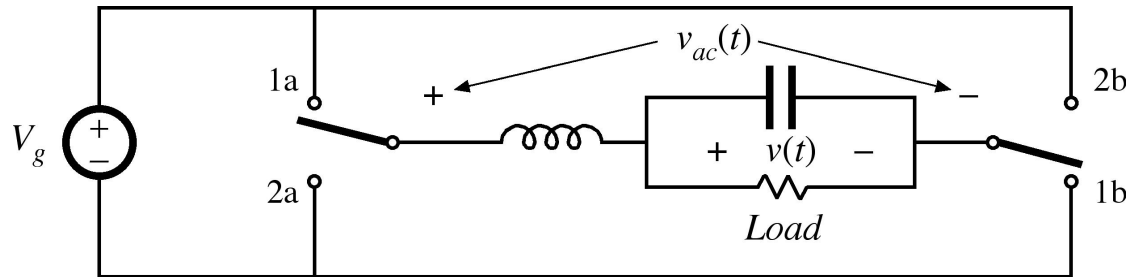
# Alternate Ways to Generate PWM Sinusoid




- (a) Operate left and right sides with same (complementary) gate drive signals

$$v(t) = (2d(t) - 1) V_g$$

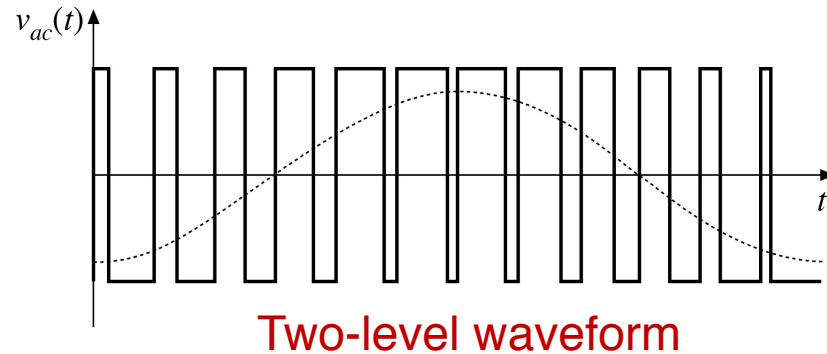


- (b) PWM one side, while other side switches at 60 Hz

$$v(t) = \pm d(t) V_g$$

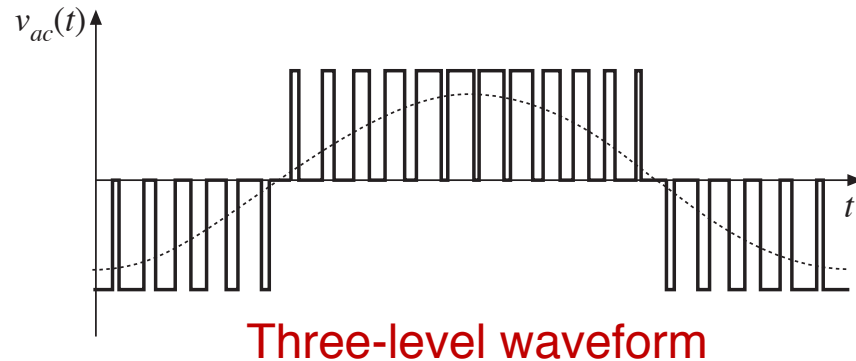

# Filtering the AC Output

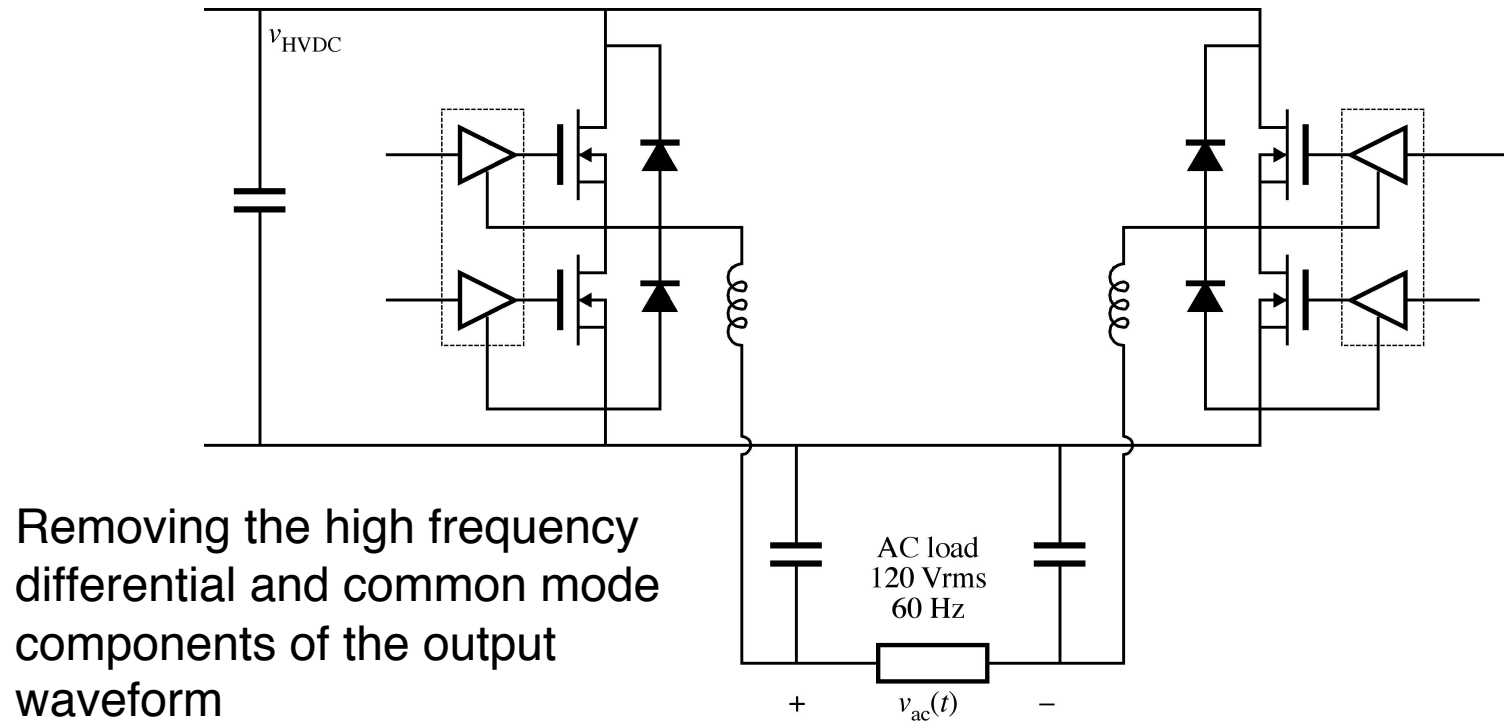

Note: the “Kill-a-Watt” power meters cannot tolerate high frequency components in the ac voltage waveform. Do not connect these meters to an unfiltered inverter output!



# Review of Fourier Series

- Any periodic waveform  $f(t)$  can be expressed in terms of harmonically related  $\sin()$  and  $\cos()$  terms

$$f(t) = \frac{b_0}{2} + \sum_{n=1}^{\infty} \left[ a_n \sin(n\omega_0 t) + b_n \cos(n\omega_0 t) \right]$$

where  $\omega_0 = \frac{2\pi}{T}$  and  $T$  is period of  $f(t)$

- The coefficients  $a_n$  and  $b_n$  can be calculated from:


$$a_n = \frac{2}{T} \int_T f(t) \sin(n\omega_0 t) dt$$

$$b_n = \frac{2}{T} \int_T f(t) \cos(n\omega_0 t) dt$$

# Classification of Waveforms

- Some waveforms have special characteristics

Even  $x(t) = x(-t)$

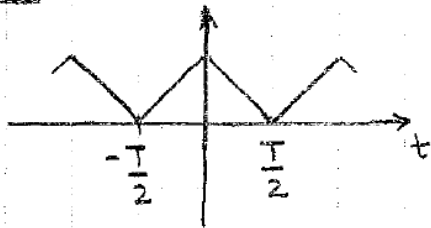


No Sin terms since Sin is Odd

$$a_n = 0 \text{ for all } n$$

$$\left[ \begin{array}{l} \text{Even func.} \times \text{Odd func.} = \text{Odd func.} \\ a_n = \frac{2}{T} \int_{-T/2}^{T/2} (\text{Odd func.}) dt = 0 \end{array} \right]$$

Odd  $x(t) = -x(-t)$

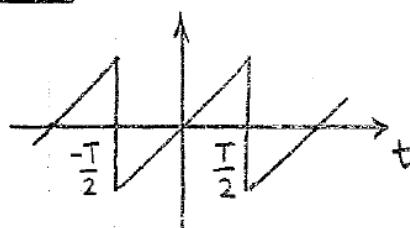


No Cos terms since Cos is Even

$$b_n = 0 \text{ for all } n$$

$$\left[ \begin{array}{l} \text{Odd func.} \times \text{Even func.} = \text{Odd func.} \\ b_n = \frac{2}{T} \int_{-T/2}^{T/2} (\text{Odd func.}) dt = 0 \end{array} \right]$$

Half-wave Symmetric

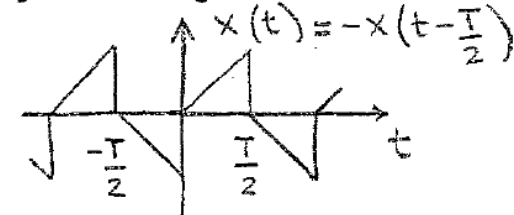



No Even Harmonics

$$a_{2k} = 0 \text{ \& } b_{2k} = 0 \text{ for all } k$$

$$\left[ \begin{array}{l} \text{For } n \text{ Even} \\ \int_{-T/2}^0 ( ) dt = - \int_0^{T/2} ( ) dt \\ \Rightarrow a_n = 0 \text{ \& } b_n = 0 \text{ for } n \text{ even} \end{array} \right]$$

$$f(t) = \frac{b_0}{2} + \sum_{n=1}^{\infty} \left[ a_n \sin(n\omega_0 t) + b_n \cos(n\omega_0 t) \right]$$

# Modified Sine-Wave Inverter

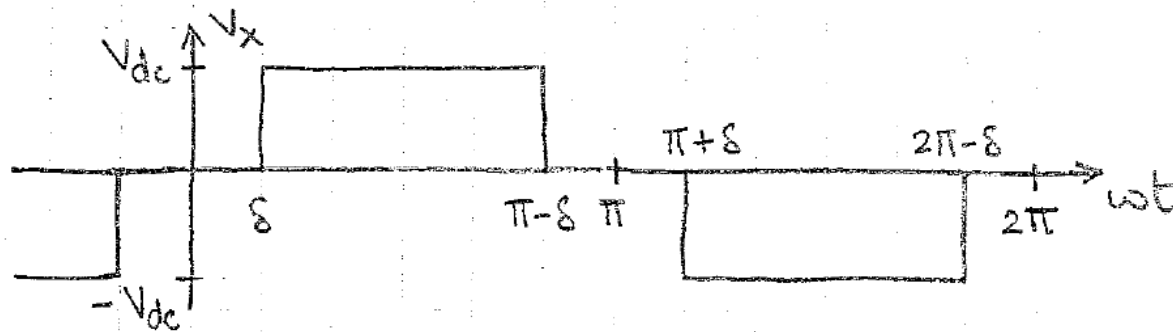
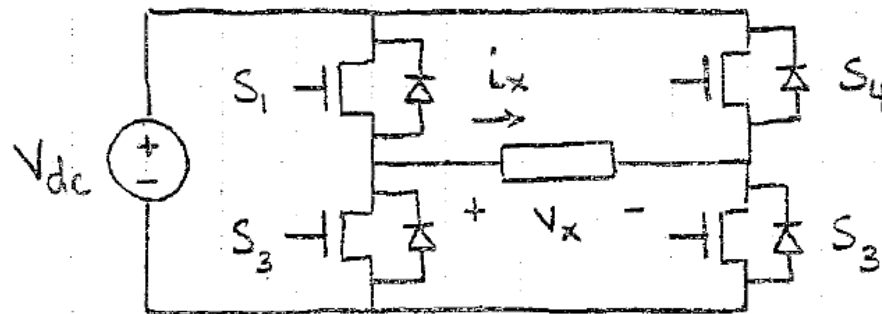


What is the frequency content of  $V_x$ ?


- $V_x$  waveform is Odd  $\rightarrow$  No cos terms, Only Sin terms
- $V_x$  waveform is Half-wave Symmetric  $\rightarrow$  No even harmonics

$$\therefore V_x(t) = \sum_{n \text{ odd}} V_n \sin(n\omega t)$$
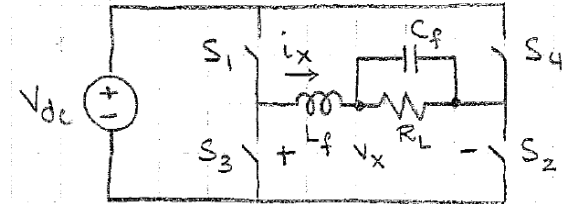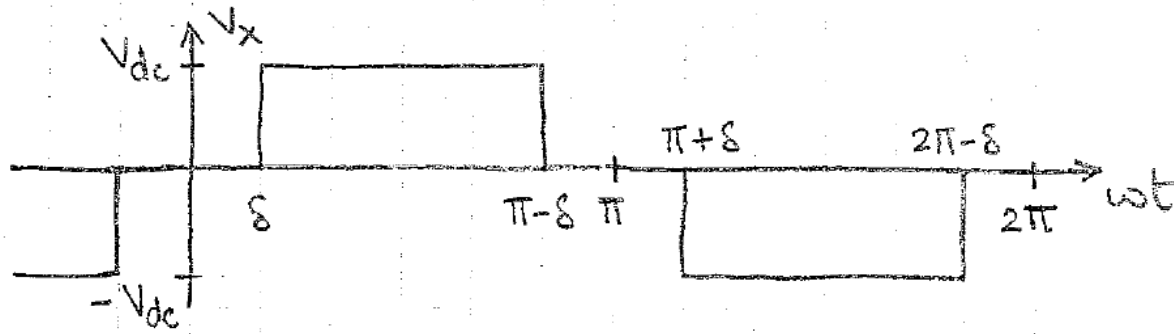
# Frequency Content of Modified Sine-Wave



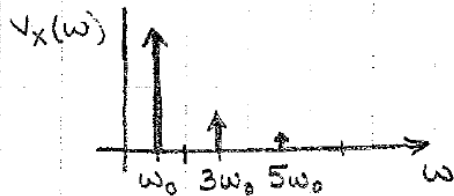If  $\delta = 0 \Rightarrow v_x$  is a square wave  $\Rightarrow v_x(t) = \sum_{n \text{ odd}} \frac{4 V_{dc}}{n\pi} \sin(n\omega t)$




Frequency content: Fundamental, 3<sup>rd</sup>, 5<sup>th</sup>, 7<sup>th</sup>, ...  
harmonics

- If we can filter out the harmonics, load voltage will be more sinusoidal than  $v_x$
- However, difficult to filter because the frequencies to be rejected ( $3\omega_0, 5\omega_0, \dots$ ) are close to the frequency we want to keep ( $\omega_0$ )
- Would like to find another way to eliminate harmonics

# Impact of Change of $\delta$

## (A) Control of Fundamental Magnitude

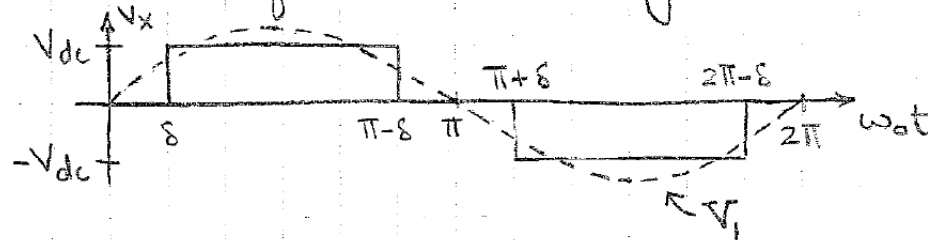

$$V_x(t) = \sum_{n \text{ odd}} V_n \sin(n\omega_0 t)$$

$$\omega_0 = \frac{2\pi}{T}$$

$$V_1 = \frac{2}{T} \int_T V_x(t) \sin(\omega_0 t) dt = \frac{2}{2\pi} \int_{2\pi} V_x(\omega_0 t) \sin(\omega_0 t) d(\omega_0 t)$$

$$V_1 = \frac{4}{2\pi} \int_{\delta}^{\pi-\delta} V_{dc} \sin(\omega_0 t) d(\omega_0 t) = \frac{4 V_{dc}}{2\pi} \left[ -\cos(\omega_0 t) \right]_{\delta}^{\pi-\delta}$$

$$V_1 = \frac{4 V_{dc}}{2\pi} \left[ -\overbrace{\cos(\pi-\delta)}^{-\cos \delta} + \cos(\delta) \right] \Rightarrow \boxed{V_1 = \frac{4 V_{dc}}{\pi} \cos(\delta)}$$

- Hence we can control the magnitude of the fundamental by controlling  $\delta$
- Can be useful if we want to regulate the output voltage of an inverter when the input voltage is changing (e.g., in a UPS when battery voltage is drooping as it discharges)

# Impact of Change of $\delta$ (Cont.)

## (B) Control of Harmonics' Magnitude

$$V_n = \frac{2}{T} \int_T v_x(t) \sin(n\omega_0 t) dt = \frac{2}{2\pi} \int_{2\pi} v_x(\omega_0 t) \sin(n\omega_0 t) d(\omega_0 t)$$


$$V_3 = \cancel{2} \cdot \frac{2}{2\pi} \int_{\delta}^{\pi-\delta} V_{dc} \sin(3\omega_0 t) d(\omega_0 t) = \frac{2}{\pi} \frac{V_{dc}}{3} \left[ -\cos(3\omega_0 t) \right]_{\delta}^{\pi-\delta}$$

$$V_3 = \frac{2 V_{dc}}{3\pi} \left[ -\overbrace{\cos(3\pi-3\delta)}^{-\cos(3\delta)} + \cos(3\delta) \right] \Rightarrow \boxed{V_3 = \frac{4 V_{dc}}{3\pi} \cos(3\delta)}$$

- So as we change  $\delta$ , the magnitude of the 3<sup>rd</sup> harmonic also changes
- If  $\delta = 30^\circ$   $\Rightarrow 3\delta = 90^\circ \Rightarrow V_3 = 0$   
Hence we can kill the 3<sup>rd</sup> harmonic by setting  $\boxed{\delta = 30^\circ}$
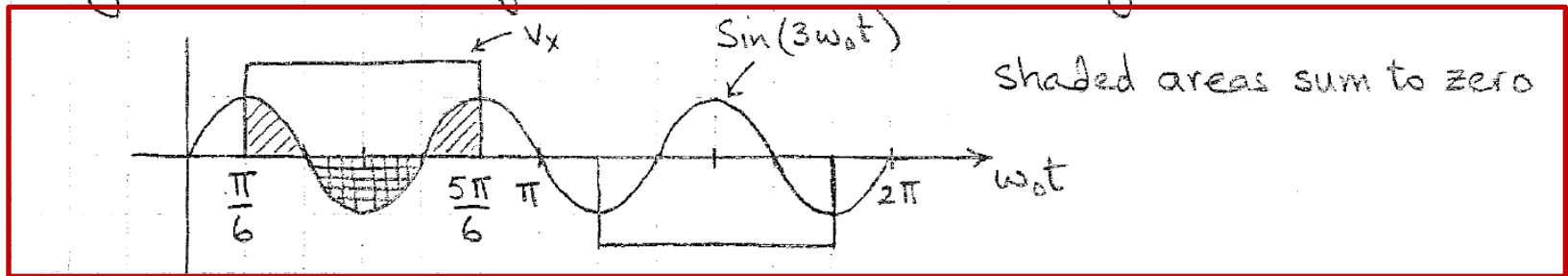
# Harmonic Elimination

- Easy to visualize why 3<sup>rd</sup> harmonic is killed by  $\delta = 30^\circ$




Can use same technique to see what happens to other harmonics


- Hence the lowest harmonic we are left with is the 5<sup>th</sup>, so filtering becomes easier
- Note  $\delta = 30^\circ$ , eliminates all triple- $n$  ( $3n$ ) harmonics (i.e., 9<sup>th</sup>, 15<sup>th</sup> are also killed).
- However, when we fix  $\delta$  to kill harmonics, we cannot use it to regulate the magnitude of the fundamental



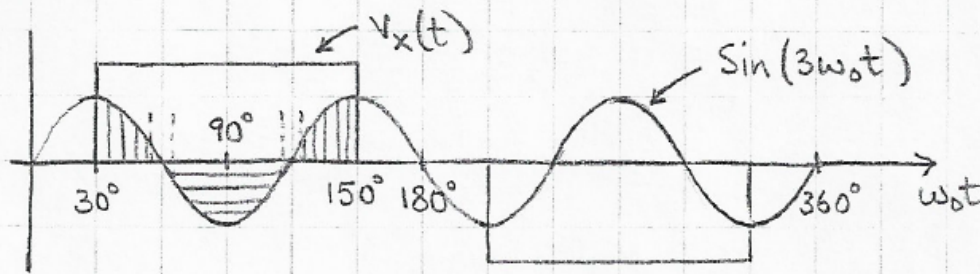
# Elimination of 3<sup>rd</sup> and 5<sup>th</sup> Harmonic



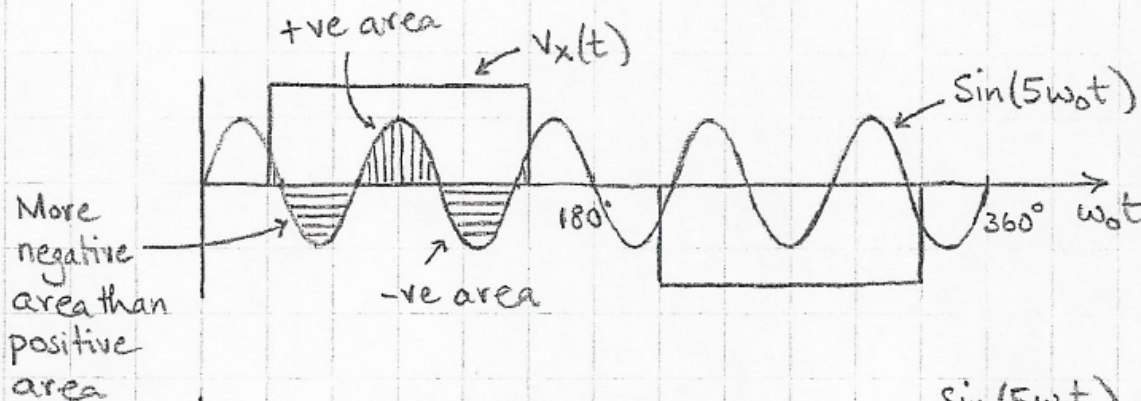3<sup>rd</sup> harmonic free  $v_x(t)$   
(+ve and -ve areas cancel)



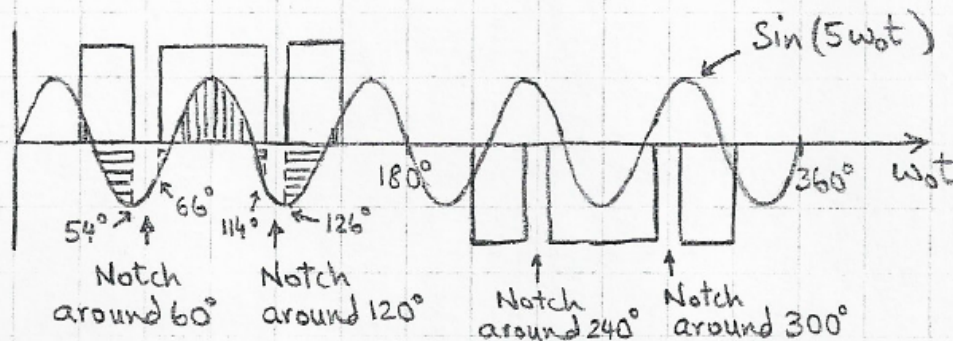Need to take a bite out of  
the negative area while keeping  
3<sup>rd</sup> harmonic areas in balance



5<sup>th</sup> & 3<sup>rd</sup> harmonic free  $v_x(t)$   
(+ve and -ve areas cancel)

These notches don't disturb the 3<sup>rd</sup>  
harmonic content as they take equal  
+ve & -ve area out the 3<sup>rd</sup> harmonic  
waveform