

Criteria ▼	Full credit ▼	Partial credit ▼	No credit ▼
Part 1: complete schematic of sensing circuitry. Include filtering, component values, header pin labels, overvoltage protection ▼	10 points	5 points	0 points
Part 1: write expressions for the ADC input voltages as functions of battery voltage and current ▼	5 points	3 points	0 points
Part 1: explain and document test data proving that you can capture the battery voltage and current within the MSP430 ▼	15 points	7 points	0 points
Part 2: Description of testing, debugging, and evaluation procedure ▼	15 points	8 points	0 points
Part 2: full schematic of Exp 3, including indication of which component is on each board and any twisted pair wiring ▼	10 points	5 points	0 points
Part 2: at MPP, capture oscilloscope waveform of PV panel voltage and MSP430 duty cycle output, showing operation (P&O or other) ▼	10 points	5 points	0 points
about MPP			
Part 2: Explain what measurements and data were collected to validate that PV system operated at max power point ▼	10 points	5 points	0 points
Part 2: Measured PV panel output power and input power. Calculated converter efficiency. ▼	7 points	4 points	0 points
Unshaded conditions: is more power captured with or without the converter? Compare experimental data. Explain why. ▼	9 points	4 points	0 points
With 4 cells shaded: does experimental system capture more power with or without converter? Give experimental data. Explain why. Suggest a way to improve this case. ▼	9 points	5 points	0 points